

# EECS 151/251A Homework 2

Due Monday, Feb 6<sup>th</sup>, 2023

## For this HW Assignment


You will be asked to write several Verilog modules as part of this HW assignment. You will need to test your modules by running them through a simulator. As shown in discussion 2, a highly suggested simulator is <https://www.edaplayground.com> which is a free, online, Verilog simulator.

For all problems except 2(b), turn in:

 1. Circuit diagram (neatly drawn by hand or with a tool). When drawing there are some rules we'd like you to follow:
  - Draw solder dots at wire junctions
  - Label bus widths for multi-bit wires
2. Verilog code
3. Testbench
4. Test result

**Warning:** We enforce no register inference policy in this class. You must use the register library in EECS151.v whenever using registers in your Verilog. EECS151.v is located at <https://inst.eecs.berkeley.edu/~eeecs151/sp23/files/lib/EECS151.v>. We will only accept solutions using this library!

To import the library on *EDA playground*, click the plus button shown below and upload the file. Then, add `include "EECS151.v" to your Verilog code (design.sv). You can import other modules (such as modules you designed before) in the same way.




## Problem 1: Binary Decoder and Encoder

In this problem except (a)3, you are not allowed to use any of the following operators:  $\{ !, \sim, \&, |, \sim\&, \sim|, *, \&\&, || \}$ .

- (a) Write five different Verilog implementations of a 2-bit binary decoder, based on the formats listed below. For the first one (structural Verilog), also draw a gate-level circuit diagram. Write a single testbench that exhaustively tests all of your implementations (put all of them in `design.sv` on *EDA playground*).
1. Structural Verilog
  2. Behavioral Verilog using continuous assignment (i.e. no `always` blocks)
  3. Behavioral Verilog using continuous assignment and bit-wise operators
  4. Behavioral Verilog using `if`
  5. Behavioral Verilog using `case`
- (b) Write the behavioral Verilog using continuous assignment and the ternary operator (?:), for a 2-bit binary *encoder*. (A encoder has the inverse function of a decoder.) The input is guaranteed to be one-hot. Write a testbench using one of the decoders you designed (import the decoder in the testbench).

Solution:

(a) Diagram:

 

Design:

1. Structural Verilog

```

module decoder1(
    input [1:0] s,
    output [3:0] x
);

    wire s0bar, s1bar;

```

```

    not(s0bar, s[0]);
    not(s1bar, s[1]);

    and(x[0], s0bar, s1bar);
    and(x[1], s[0], s1bar);
    and(x[2], s0bar, s[1]);
    and(x[3], s[0], s[1]);

```

**endmodule**

2. Behavioral Verilog using continuous assignment

```

module decoder2(
    input [1:0] s,
    output [3:0] x
);

    assign x[0] = (s == 2'b00);
    assign x[1] = (s == 2'b01);
    assign x[2] = (s == 2'b10);
    assign x[3] = (s == 2'b11);

```

**endmodule**

3. Behavioral Verilog using continuous assignment and bit-wise operators

```

module decoder3(
    input [1:0] s,
    output [3:0] x
);

    assign x[0] = ~s[1] & ~s[0];
    assign x[1] = ~s[1] & s[0];
    assign x[2] = s[1] & ~s[0];
    assign x[3] = s[1] & s[0];

```

**endmodule**

4. Behavioral Verilog using if

```

module decoder4(
    input [1:0] s,
    output reg [3:0] x
);

    always @(*) begin
        x = 4'b0;
        if(s == 2'b00)
            x[0] = 1;
        if(s == 2'b01)

```

```

        x[1] = 1;
    if(s == 2'b10)
        x[2] = 1;
    if(s == 2'b11)
        x[3] = 1;
end

endmodule
5. Behavioral Verilog using case
module decoder5(
    input [1:0] s,
    output reg [3:0] x
);

always @(*) begin
    case(s)
        2'b00: x = 4'b0001;
        2'b01: x = 4'b0010;
        2'b10: x = 4'b0100;
        2'b11: x = 4'b1000;
    endcase
end

endmodule
Testbench:
module decoder_tb;
    reg [1:0] s;
    reg [3:0] expected;
    wire [3:0] xs [0:4];

    // loop variables
    integer i, j;

    // instantiate duts
    decoder1 d1(.s(s), .x(xs[0]));
    decoder2 d2(.s(s), .x(xs[1]));
    decoder3 d3(.s(s), .x(xs[2]));
    decoder4 d4(.s(s), .x(xs[3]));
    decoder5 d5(.s(s), .x(xs[4]));

    // expected outputs
    always @(*) begin
        case (s)
            2'b00: expected = 4'b0001;
            2'b01: expected = 4'b0010;

```


```

    2'b10:   expected = 4'b0100;
    2'b11:   expected = 4'b1000;
    default: expected = 4'bxxxx;
  endcase
end

// begin test
initial begin
  $dumpfile("dump.vcd");
  $dumpvars;
  for(i = 0; i < 4; i = i + 1) begin
    s = i;
    #1;
    $display("s: %b, xs[0]: %b, xs[1]: %b, xs[2]: %b, xs[3]: %b,
    xs[4]: %b, expected: %b",
             s, xs[0], xs[1], xs[2], xs[3], xs[4], expected);
    // Break early if failed
    for(j = 0; j < 5; j = j + 1) begin
      if(xs[j] !== expected) begin
        $display("FAILED at decoder%1d, expected %b, got %b",
                 j + 1, expected, xs[j]);
        $finish();
      end
    end
  end
  $display("ALL TESTS PASSED FOR ALL DESIGNS!");
  $finish();
end
endmodule

```

(b) Diagram:

 

Design:

```

module encoder(
    input [3:0] x,
    output [1:0] s
);

assign s = (x[0] == 1'b1)? 2'b00:
           (x[1] == 1'b1)? 2'b01:

```

```
(x[2] == 1'b1)? 2'b10:  
                2'b11;
```


```
endmodule
```

Testbench:

```
`include "decoder.v"  
  
module encoder_tb;  
    reg [1:0] s;  
    reg [1:0] expected;  
    wire [3:0] x;  
    wire [1:0] out;  
  
    // loop variables  
    integer i, j;  
  
    // instantiate duts  
    decoder1 d1(.s(s), .x(x));  
    encoder enc(.x(x), .s(out));  
  
    // expected outputs  
    always @(*) begin  
        expected = s;  
    end  
  
    // begin test  
    initial begin  
        $dumpfile("dump.vcd");  
        $dumpvars;  
        for(i = 0; i < 4; i = i + 1) begin  
            s = i;  
            #1;  
            $display("s: %b, x: %b, out: %b, expected: %b",
                     s, x, out, expected);  
            // Break early if failed  
            if(out != expected) begin  
                $display("FAILED, expected %b, got %b",
                         expected, out);  
                $finish();  
            end  
        end  
        $display("ALL TESTS PASSED!");  
        $finish();  
    end  
endmodule
```


## Problem 2: Decoder-Based Multiplexer

 - (a) Design a 4-to-1 multiplexer using one of the decoders you designed above. The select signals must be input to the decoder and must not be used anywhere else. Provide an exhaustive test.
- (b) What could be a potential benefit of using this decoder-based multiplexer against the following design:



Solution:

(a) Diagram:

 

Design:

```

`include "decoder.v"

module multiplexer(
    input [1:0] s,
    input [3:0] in,
    output      out
);

    wire [3:0] x;
  
```

```

wire t0, t1, t2, t3;

decoder1 dc1(.s(s), .x(x));

and(t0, in[0], x[0]);
and(t1, in[1], x[1]);
and(t2, in[2], x[2]);
and(t3, in[3], x[3]);
or(out, t0, t1, t2, t3);

endmodule

Testbench:

module multiplexer_tb;
    reg [1:0] s;
    reg [3:0] in;
    reg expected;
    wire out;

    // loop variables
    integer i, j;

    // instantiate duts
    multiplexer mux1(.s(s), .in(in), .out(out));

    // expected outputs
    always @(*) begin
        case (s)
            2'b00: expected = in[0];
            2'b01: expected = in[1];
            2'b10: expected = in[2];
            2'b11: expected = in[3];
            default: expected = 1'bx;
        endcase
    end

    // begin test
    initial begin
        $dumpfile("dump.vcd");
        $dumpvars;
        for(j = 0; j < 16; j = j + 1) begin
            in = j;
            for(i = 0; i < 4; i = i + 1) begin
                s = i;
                #1;
                $display("s: %b, in: %b, out: %b, expected: %b",

```

```

        s, in, out, expected);
// Break early if failed
if(out !== expected) begin
    $display("FAILED, expected %b, got %b",
            expected, out);
    $finish();
end
end
$display("ALL TESTS PASSED!");
$finish();
end
endmodule

```


- (b) Smaller delay (fewer logic levels) from data input to output, trading off delay from select signals to output.

### Problem 3: Equality Comparator Generator

An equality comparator is a combinational logic circuit that takes as input two  $N$ -bit signals and outputs 1 iff the two signals match in every bit position. Design a generator for equality comparators of size  $N$  in the structural Verilog. Write a testbench that tests  $N = 1$  and  $N = 4$  exhaustively.

Solution:

Diagram:

 

Design:

```

module eq #(parameter N = 4)
    ) (

```

```

    input [N-1:0] a,
    input [N-1:0] b,
    output          eq
);

wire [N-1:0]           s;
wire [N-1:0]           t;

genvar                  i;

generate
    for(i = 0; i < N; i = i + 1)
        xor(s[i], a[i], b[i]);
endgenerate

buf(t[0], s[0]);
generate
    for(i = 1; i < N; i = i + 1)
        or(t[i], s[i], t[i-1]);
endgenerate

not(eq, t[N-1]);

endmodule

```

Testbench:

```

module eq_tb;
    reg a1, b1;
    reg [3:0] a4, b4;
    reg          expected1, expected4;
    wire         out1, out4;

    // loop variables
    integer   i, j;

    // instantiate duts
    eq #(N(1)) eq1 (.a(a1), .b(b1), .eq(out1));
    eq #(N(4)) eq4 (.a(a4), .b(b4), .eq(out4));

    // expected outputs
    always @(*) begin
        expected1 = (a1 == b1);
        expected4 = (a4 == b4);
    end

```

```

// begin test
initial begin
    $dumpfile("dump.vcd");
    $dumpvars;
    for(i = 0; i < 2; i = i + 1) begin
        for(j = 0; j < 2; j = j + 1) begin
            a1 = i;
            b1 = j;
            #1;
            $display("a: %b, b: %b, out: %b, expected: %b",
                     a1, b1, out1, expected1);
            if(out1 !== expected1) begin
                $display("FAILED, expected %b, got %b",
                         expected1, out1);
                $finish();
            end
        end
    end
    for(i = 0; i < 16; i = i + 1) begin
        for(j = 0; j < 16; j = j + 1) begin
            a4 = i;
            b4 = j;
            #1;
            $display("a: %b, b: %b, out: %b, expected: %b",
                     a4, b4, out4, expected4);
            if(out4 !== expected4) begin
                $display("FAILED, expected %b, got %b",
                         expected4, out4);
                $finish();
            end
        end
    end
    $display("ALL TESTS PASSED FOR ALL DESIGNS!");
    $finish();
end
endmodule

```

## Problem 4: Counter Generator

Write a Verilog implementation for an  $N$ -bit counter generator for counters with the following specification. Write a testbench for  $N = 4$ .

Specification:


- Counters have as input `clk` (the clock signal), `rst` (reset), and `en` (enable).
- Counters have an  $N$ -bit output named `cnt`.

- Counters hold the value of `cnt` constant when both `rst` and `en` are 0.
- Counters set `cnt` to 0 on a positive edge of `clk` if `rst` is 1.
- Counters increment `cnt` by 1 at a positive edge of `clk` if `rst` is 0 and `en` is 1.
- When `cnt` is the maximum possible value ( $2^N - 1$  in  $N$ -bit counters), `cnt` will become 0 next time it is incremented.

*Warning:* Use the register library in `EECS151.v`.

Solution:

Diagram:

 

Design:

```

`include "EECS151.v"

module counter #(
    parameter N = 4
) (
    input      clk, rst, en,
    output [N-1:0] cnt
);

wire [N-1:0] cnt_inc;

REGISTER_R_CE #(N) r(.q(cnt), .d(cnt_inc), .rst(rst), .ce(en),
                .clk(clk));

assign cnt_inc = cnt + 1;

endmodule

```

Testbench:

```
module counter_tb;
    reg clk, rst, en;
    reg [3:0] expected;
    wire [3:0] out;

    // loop variables
    integer i;

    // define clock
    initial clk = 0;
    always #1 clk = !clk;

    // instantiate dut
    counter #(N(4)) c1(.clk(clk), .rst(rst), .en(en), .cnt(out));

    // task to compare the output with its expected value
    task check;
        begin
            #2;
            // verify in the timestep clock is going down
            $display("rst: %b, en: %b, out: %b, expected: %b",
                     rst, en, out, expected);
            if(out !== expected) begin
                $display("FAILED, expected %b, got %b",
                         expected, out);
                $finish();
            end
        end
    endtask

    // begin test
    initial begin
        $dumpfile("dump.vcd");
        $dumpvars;
        // check reset works regardless enable
        rst = 1;
        en = 1'bx;
        expected = 4'b0;
        check;
        // check increment works
        rst = 0;
        en = 1;
        for(i = 0; i < 16; i = i + 1) begin
            expected = expected + 1;
            check;
        end
        // check enable works
```

```

for(i = 0; i < 16; i = i + 1) begin
    // count doesn't change if enable is 0
    en = 0;
    check;
    check;
    check;
    // count is incremented if enable is 1
    en = 1;
    expected = expected + 1;
    check;
end
$display("ALL TESTS PASSED!");
$finish();
end
endmodule

```

## Problem 5: Serial To Parallel Converter

Imagine a situation that you need to design an interface between two circuits *A* and *B*. *A* generates one-bit data at a time, while *B* receives 10-bit data in parallel. These circuits also partially implement the hand-shaking protocol. *A* raises **SerRdy** when the data starts coming out. On the other hand, *B* reads the data when **ParRdy** is on. Assume all circuits (including the one you are going to design) share the clock signal **clk**.


- Using the equality comparator generator and the counter generator you designed, design a saturating counter that saturates at 9 (it works the same as the original counter up to 9, but then it will get stuck at 9 until the reset signal is activated). Equip it with an extra output port that tells whether it is saturated (1) or not (0).
- Design a 10-bit shift-register with enable (it works as a shift-register if enable is 1, otherwise it just holds the current value).
- Design the interface circuit using the saturating counter and the shift-register. Its detailed specification is shown below. You may assume that **SerRdy** is 1 at the first positive edge.

Specification:

- Receives three binary inputs: **SerDat**, **SerRdy**, and **clk**.
- Generates two outputs: a 10-bit signal **ParDat** and a binary signal **ParRdy**.
- Stores a 10-bit sequence that **SerDat** takes at each positive edge of **clk** after **SerRdy** becomes 1.
- It is guaranteed that once **SerRdy** becomes 1, it will remain 1 until next positive edge of **clk**. Just after that, it will drop to 0 and remain 0 for at least 10 cycles.
- Turns on **ParRdy** when finished storing the 10-bit sequence, which is output as **ParDat**.
- Turns off **ParRdy** when next sequence comes in.

Solution:

(a) Diagram:

 

Design:

```

`include "counter.v"
`include "eq.v"

module sat_counter #(
    parameter N = 4,
    parameter M = 4'd9
) (
    input      clk, rst,
    output [N-1:0] cnt,
    output      sat
);

wire en;

counter #(N) c1(clk, rst, en, cnt);
eq #(N) eq1(cnt, M, sat);
not(en, sat);

endmodule

```

Testbench:

```

module sat_counter_tb;
    reg clk, rst;
    reg [3:0] expected;
    reg      expected_sat;
    wire [3:0] out;
    wire      sat;

    // loop variables
    integer i;

    // define clock
    initial clk = 0;

```

```
always #1 clk = !clk;

// instantiate duts
sat_counter #(N(4), .M(4'd9)) c1(.clk(clk), .rst(rst), .cnt(out),
→ .sat(sat));

task check;
begin
#2;
// verify in the timestep clock is going down
$display("rst: %b, out: %b, sat: %d, expected: %b, expected_sat:
→ %b",
rst, out, sat, expected, expected_sat);
if(out !== expected) begin
$display("FAILED at out, expected %b, got %b",
expected, out);
$finish();
end
if(sat !== expected_sat) begin
$display("FAILED at sat, expected %b, got %b",
expected_sat, sat);
$finish();
end
end
endtask


// begin test
initial begin
$dumpfile("dump.vcd");
$dumpvars;
// initial reset
rst = 1;
expected = 4'b0;
expected_sat = 0;
check;
// check increment works before saturation
rst = 0;
for(i = 0; i < 8; i = i + 1) begin
expected = expected + 1;
check;
end
// check it saturates
expected = expected + 1;
expected_sat = 1;
check;
check;
check;
```

```

    check;
    // check reset works after saturation
    rst = 1;
    expected = 4'b0;
    expected_sat = 0;
    check;
    $display("ALL TESTS PASSED!");
    $finish();
end
endmodule

```

(b) Diagram:

 

Design:

```

`include "EECS151.v"

module shift_reg #(
    parameter N = 10
) (
    input      clk, in, en,
    output [N-1:0] out
);

wire [N-1:0] d;

REGISTER_CE #(N(N)) r(.q(out), .d(d), .ce(en), .clk(clk));

assign d = {out, in};

endmodule

```

Testbench:

```

module sat_counter_tb;
reg clk, in, en;
reg [9:0] expected;
wire [9:0] out;

// loop variables

```

```
integer      i;

// define clock
initial clk = 0;
always #1 clk = !clk;

// instantiate dut
shift_reg #(N(10)) c1(.clk(clk), .in(in), .en(en), .out(out));

task check;
begin
#2;
// verify in the timestep clock is going down
$display("in: %b, en: %b, out: %b, expected: %b",
         in, en, out, expected);
if(out != expected) begin
    $display("FAILED, expected %b, got %b",
             expected, out);
    $finish();
end
end
endtask


// begin test
initial begin
$dumpfile("dump.vcd");
$dumpvars;
// fill register with random numbers
en = 1;
for(i = 0; i < 9; i = i + 1) begin
    in = $random % 2;
    expected = {expected[8:0], in};
    #2;
end
in = $random % 2;
expected = {expected[8:0], in};
check;
// check enable
en = 0;
check;
check;
check;
// check 10 more cycles with random numbers
en = 1;
for(i = 0; i < 10; i = i + 1) begin
    en = 1;
    in = $random % 2;
```

```

    expected = {expected[8:0], in};
    check;
  end
  $display("ALL TESTS PASSED!");
  $finish();
end
endmodule

```

(c) Diagram:

 

Design:

```

`include "shift_reg.v"
`include "sat_counter.v"

module parallelizer(
    input      clk,
    input      SerDat, SerRdy,
    output [9:0] ParDat,
    output      ParRdy
);

// shift-register to store the value of SerDat
wire          en;
shift_reg #(N(10)) sr(.clk(clk), .in(SerDat), .en(en), .out(ParDat));

// saturating counter to count 10 - 1 cycles after SerRdy becomes on
wire          sat;
sat_counter #(N(4), M(4'd9)) sc(.clk(clk), .rst(SerRdy), .sat(sat));

// if counter is saturated, ParDat is ready
assign ParRdy = sat;

// if SerRdy is on (first bit) or counter is not saturated (following
// bits), enable shift-register
assign en = SerRdy | !ParRdy;

endmodule

```

Testbench:

```

module parallelizer_tb;
    reg clk;
    reg SerDat, SerRdy;
    reg [9:0] expected;
    reg      expected_ParRdy;
    wire [9:0] ParDat;
    wire      ParRdy;

    // loop variables
    integer i;

    // define clock
    initial clk = 0;
    always #1 clk = !clk;

    // instantiate duts
    parallelizer p1(.clk(clk), .SerDat(SerDat), .SerRdy(SerRdy),
→ .ParDat(ParDat), .ParRdy(ParRdy));

    task check;
        begin
            #2;
            // verify in the timestep clock is going down
            $display("SerDat: %b, SerRdy: %b, ParDat: %b, ParRdy: %b",
→ expected: %b, expected_ParRdy: %b",
                    SerDat, SerRdy, ParDat, ParRdy, expected,
→ expected_ParRdy);
            // ParRdy must be always correct
            if(ParRdy !== expected_ParRdy) begin
                $display("FAILED at ParRdy, expected %b, got %b",
                        expected_ParRdy, ParRdy);
                $finish();
            end
            // ParDat must be correct if ParRdy
            if(ParRdy && ParDat !== expected) begin
                $display("FAILED at ParDat, expected %b, got %b",
                        expected, ParDat);
                $finish();
            end
        end
    endtask

    // begin test
    initial begin
        $dumpfile("dump.vcd");

```

```
$dumpvars;
// trigger SerRdy
SerRdy = 1;
SerDat = $random % 2;
expected = {expected[8:0], SerDat};
expected_ParRdy = 0;
check;
SerRdy = 0;
// check behavior after SerRdy before ParRdy
for(i = 0; i < 8; i = i + 1) begin
    SerDat = $random % 2;
    expected = {expected[8:0], SerDat};
    check;
end
// check behavior when turning on ParRdy
expected_ParRdy = 1;
SerDat = $random % 2;
expected = {expected[8:0], SerDat};
check;
// check behavior after ParRdy
for(i = 0; i < 20; i = i + 1) begin
    SerDat = $random % 2;
    check;
end
// trigger SerRdy again
SerRdy = 1;
SerDat = $random % 2;
expected = {expected[8:0], SerDat};
expected_ParRdy = 0;
check;
SerRdy = 0;
// check behavior after SerRdy before ParRdy
for(i = 0; i < 8; i = i + 1) begin
    SerDat = $random % 2;
    expected = {expected[8:0], SerDat};
    check;
end
// check behavior when turning on ParRdy
expected_ParRdy = 1;
SerDat = $random % 2;
expected = {expected[8:0], SerDat};
check;
$display("ALL TESTS PASSED!");
$finish();
end
endmodule
```