

EECS 151/251A Homework 4


Due Tuesday, Feb 21, 2023

In this homework, you will be asked to use binary-encoded or one-hot-encoded states. In binary encoding, state n corresponds to a state where the FFs hold n in a binary number. For example, in a 4-state machine, the FFs hold 00 in state 0, 01 in state 1, 10 in state 2, and 11 in state 3. On the other hand, in one-hot encoding, state n is a state where the n -th FF holds 1 and the other FFs hold 0. Using the same example, the value of FFs is 0001 in state 0, 0010 in state 1, 0100 in state 2, and 1000 in state 3 in one-hot encoding.

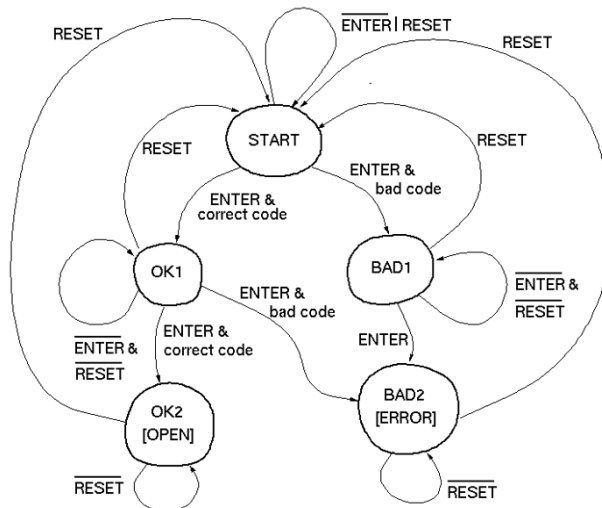Problem 1: Combinational Lock

IMPORTANT: Use a skeleton at https://inst.eecs.berkeley.edu/~eecs151/sp23/files/verilog/comb_lock.v for this problem.

Consider the following state transition diagram of a combinational lock.



The following is the additional specification of this combinational lock.

- It receives one 2-bit code at a time.
- The correct code sequence is $11 \rightarrow 10$.
- It outputs two signals: OPEN and ERROR. OPEN is 1 iff it is in OK2, whereas ERROR is 1 iff it is in BAD2.
- It is guaranteed that ENTER and RESET do not take 1 at the same time.

- It uses the following state assignment: {START = state 0, OK1 = state 1, OK2 = state 2, BAD1 = state 3, BAD2 = state 4}.
- (a) Write a Verilog module with binary-encoded states. (*Hint*: Use `case`.)
- (b) Write a Verilog module with one-hot-encoded states, without using `always` blocks. (*Hint*: Use continuous assignment.)

Solution:

```
(a) `include "EECS151.v"

module comb_lock_binary(
    input          CLK, ENTER, RESET,
    input [1:0]    CODE,
    output reg     OPEN, ERROR
);

    localparam START = 3'b000;
    localparam OK1   = 3'b001;
    localparam OK2   = 3'b010;
    localparam BAD1  = 3'b011;
    localparam BAD2  = 3'b100;

    localparam CODE1 = 2'b11;
    localparam CODE2 = 2'b10;

    wire [2:0] cur_state;
    reg [2:0] next_state;
    REGISTER #(.N(3)) r(.q(cur_state), .d(next_state), .clk(CLK));

    always @(*) begin
        OPEN = 0;
        ERROR = 0;
        next_state = cur_state;
        case(cur_state)
            START: begin
                if(ENTER) begin
                    if(CODE == CODE1) next_state = OK1;
                    else next_state = BAD1;
                end
            end
            OK1: begin
                if(RESET) next_state = START;
                if(ENTER) begin
                    if(CODE == CODE2) next_state = OK2;
                    else next_state = BAD2;
                end
            end
        endcase
    end
endmodule
```

```

    end
    OK2: begin
        OPEN = 1;
        if(RESET) next_state = START;
    end
    BAD1: begin
        if(RESET) next_state = START;
        if(ENTER) next_state = BAD2;
    end
    BAD2: begin
        ERROR = 1;
        if(RESET) next_state = START;
    end
endcase
end

endmodule

```

```

(b) module comb_lock_onehot(
        input        CLK, ENTER, RESET,
        input  [1:0] CODE,
        output       OPEN, ERROR
    );

    wire [4:0]          cur_state, next_state;
    REGISTER #(.N(5)) r(.q(cur_state), .d(next_state), .clk(CLK));

    assign OPEN = cur_state[2];
    assign ERROR = cur_state[4];

    assign next_state[0] = (cur_state[0] & ~ENTER) | RESET;
    assign next_state[1] = (cur_state[0] & ENTER & CODE[1] & CODE[0]) |
        (cur_state[1] & ~ENTER & ~RESET);
    assign next_state[2] = (cur_state[1] & ENTER & CODE[1] & ~CODE[0]) |
        (cur_state[2] & ~RESET);
    assign next_state[3] = (cur_state[0] & ENTER & (~CODE[1] | ~CODE[0])) |
        (cur_state[3] & ~ENTER & ~RESET);
    assign next_state[4] = (cur_state[1] & ENTER & (~CODE[1] | CODE[0])) |
        (cur_state[3] & ENTER) |
        (cur_state[4] & ~RESET);


endmodule

```

 Problem 2: STD to Gate-Level Circuits


Consider the following state transition diagram with input a, b and output o . Labels of the arrow specify the values of input and output as ab/o .

(No need to write Verilog for this problem.)



- Draw a gate-level circuit diagram with binary-encoded states. Use K-maps to simplify the circuit.
- Draw a gate-level circuit diagram with one-hot-encoded states.

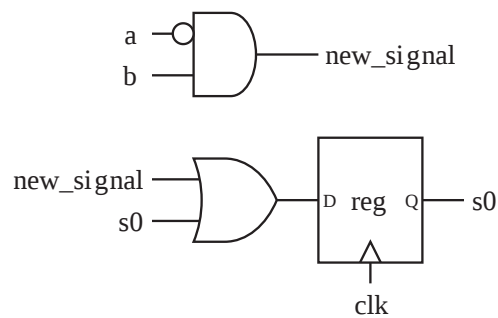(Note: You may omit wires as long as they are named. Example is shown below.)



Solution:

- Truth Table:

s_1	s_0	a	b	n_1	n_0	o
0	0	0	0	0	0	0
0	0	0	1	0	1	1
0	0	1	0	1	0	1
0	0	1	1	0	0	0
0	1	0	0	0	1	0
0	1	0	1	1	1	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	1
1	0	1	1	1	0	0
1	1	0	0	0	0	0
1	1	0	1	1	1	0
1	1	1	0	1	1	0
1	1	1	1	1	1	0

K-map for n_1 :

		ab			
		00	01	11	10
$s_1 s_0$	00	0	0	0	1
	01	0	1	0	0
	11	0	1	1	1
	10	1	1	1	1

K-map for n_0 :

		<i>ab</i>			
		00	01	11	10
<i>s₁s₀</i>	00	0	1	0	0
	01	1	1	1	1
	11	0	1	1	1
	10	0	0	0	1

K-map for *o*:

		<i>ab</i>			
		00	01	11	10
<i>s₁s₀</i>	00	0	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	0	0	0	1


SOPs:

$$n_1 = s_1s'_0 + s_1a + s'_0ab' + s_0a'b$$

$$n_0 = s'_1s_0 + s_0b + s'_1a'b + s_1ab'$$

$$o = s'_1a'b + s'_0ab'$$


Circuit Diagram:

 

(b) Boolean Expression:

$$\begin{aligned}
 n_0 &= s_0(a \oplus b)' + s_3a'b' \\
 n_1 &= s_0a'b + s_1(a'b)' \\
 n_2 &= s_0ab' + s_2(ab')' \\
 n_3 &= s_1a'b + s_2ab' + s_3(a + b) \\
 o &= (s_0 + s_1)a'b + (s_0 + s_2)ab'
 \end{aligned}$$

Circuit Diagram:

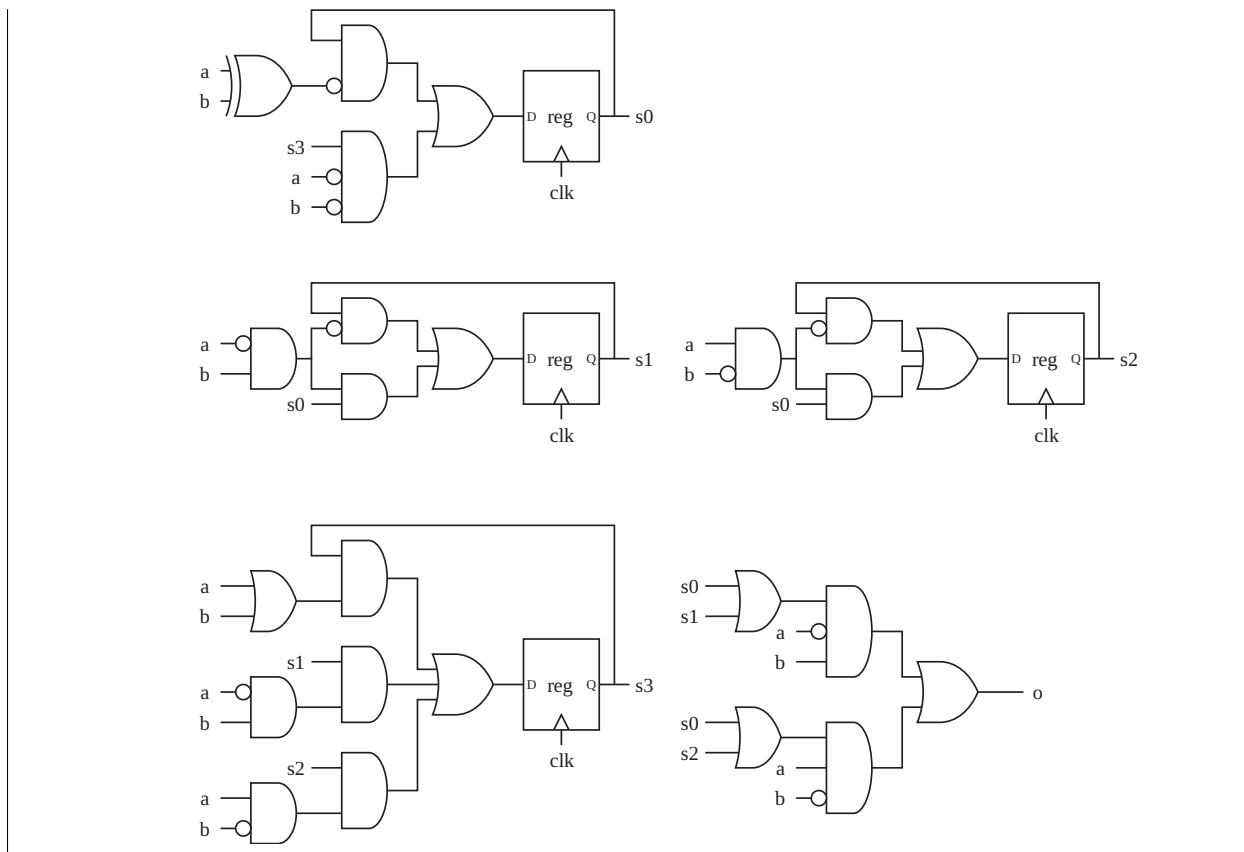

Problem 3: Alternative Counters

A 2-bit counter is a state machine with 4 states. It transitions from state n to state $(n + 1 \bmod 4)$ at each positive edge of the clock signal. Assume the states are binary-encoded.

- Write a Boolean expression of the input of each FF.
- Imagine a situation that we need to count 4 cycles but no need to know which cycle we are in of the 4 cycles. In this situation, we can use an alternative counter, which transitions among 4 states in an arbitrary order. For example, it may transition from state 0 to state 2, state 2 to state 1, state 1 to state 3, and state 3 to state 0. Find a best alternative counter in terms of number of 2-input gates, and write the order of states and the Boolean expressions of FF inputs. You cannot use more than two FFs and they are initialized to 0.

Solution:

(a)

$$n_0 = s'_0$$

$$n_1 = s_0 \oplus s_1$$

(b) Order: state 0 \rightarrow state 1 \rightarrow state 3 \rightarrow state 2.

Boolean Expression:

$$n_0 = s'_1$$

$$n_1 = s_0$$

Problem 4: Vending Machine

You are to design a control module in a vending machine. The items inside the machine cost \$15, and the machine accepts five dollar and ten dollar bills only. The control module receives two signals that indicate what kind of bill has been deposited.

The control module has three output signals. One signal causes the item to be delivered, while the other two signals cause a bill to be dispensed.

The vending machine has another module that counts the number of five dollar bills inside. The control module receives a signal from it that indicates whether it is out of change or not.

Whenever the amount of money received becomes \$15, the machine delivers the item and resets to its initial state. When it has received \$20, it delivers the item with a change, or returns two ten dollar bills if it is out of change. After that, it goes back to the initial state.

Identify your inputs and outputs, and draw a state transition diagram that implements the control module. (No need to write Verilog.)

Assume that only one bill can be deposited or dispensed at a time. No bills can be deposited when delivering the item.

Solution:

Inputs:

- FIVE (when a five dollar bill is deposited)
- TEN (when a ten dollar bill is deposited)
- OUT (when the machine is out of change)

Outputs:

- ITEM (deliver the item)
- RETURN5 (dispense a five dollar bill)
- RETURN10 (dispense a ten dollar bill)

STD:

