



EECS 151/251A

Spring 2023

**Digital Design and Integrated
Circuits**

Instructor:
Wawrzynek

**Lecture 3: Verilog 1:
Combinational Logic
Circuits**

Outline



- Hardware Description Language Overview
- Verilog Introduction

Announcements


- Problem Set one posted. Start soon!
 - Due next Monday (another out Friday)
- Contact me if you are still trying to get enrolled.



Hardware Description Languages

Design Entry

 - ❑ Schematic entry/editing used to be the standard method in industry and universities.
- ☺ Schematics are intuitive. They match our use of gate-level or block diagrams.
- ☺ Somewhat physical. They imply a physical implementation.
- ☹ Require a special tool (editor).
- ☹ Unless hierarchy is carefully designed, schematics can be confusing and difficult to follow on large designs.



- Hardware Description Languages (HDLs) are the new standard
 - except for PC board design, where schematics are still used.

Hardware Description Languages

Basic Idea:

- Language constructs describe circuits with two basic forms:
 - **Structural descriptions:** connections of components. Nearly one-to-one correspondence to with schematic diagram.
 - **Behavioral descriptions:** use high-level constructs (similar to conventional programming) to describe the circuit function.

Originally invented for simulation.

- “logic synthesis” tools exist to automatically convert to gate level representation.
- High-level constructs greatly improves designer productivity.
- However, this may lead you to falsely believe that hardware design can be reduced to writing programs*

“Structural” example:

```
Decoder(output x0,x1,x2,x3;  
inputs a,b)  
{  
    wire abar, bbar;  
    inv(bbar, b);  
    inv(abar, a);  
    and(x0, abar, bbar);  
    and(x1, abar, b );  
    and(x2, a, bbar);  
    and(x3, a, b );  
}
```

“Behavioral” example:


```
Decoder(output x0,x1,x2,x3;  
inputs a,b)  
{  
    switch [a b]  
        case 00: [x0 x1 x2 x3] = 0x8;  
        case 01: [x0 x1 x2 x3] = 0x4;  
        case 10: [x0 x1 x2 x3] = 0x2;  
        case 11: [x0 x1 x2 x3] = 0x1;  
    endswitch;  
}
```

Warning: this is a fake HDL!

*New tools and languages exist for this - called “high level synthesis”.

Sample Design Methodology

 Hierarchically defines structure and/or function of circuit.



Verification: Does the design behave as required with regards to function, timing, and power consumption?

Maps specification to resources of implementation platform (FPGA or ASIC).

Note: This is not the entire story. Other tools are useful for analyzing HDL specifications. More on this later.

Some Hardware Description Languages

Verilog:

- Simple C-like syntax for structural and behavior hardware constructs
- Mature set of commercial tools for synthesis and simulation
- Used in EECS 151 / 251A

VHDL:

- Semantically very close to Verilog
- More syntactic overhead
- Extensive type system for “synthesis time” checking

System Verilog:

- Enhances Verilog with strong typing along with other additions
- Somewhat less mature tool-flow

BlueSpec:

- Invented at MIT
- Originally built within the Haskell programming language
- Now available commercially: bluespec.com

Chisel:

- Developed at UC Berkeley
- Used in CS152, CS250
- Available at: www.chisel-lang.org



Verilog Introduction

Verilog Introduction

- ❑ A module definition describes a component in a circuit
- ❑ Two ways to describe module contents:
 - Structural Verilog
 - List of sub-components and how they are connected
 - Just like schematics, but using text
 - You get precise control over circuit details
 - May be necessary to map to special resources of the FPGA/ASIC
 - Behavioral Verilog
 - Describe what a component does, not how it does it
 - May be simpler to write than structural description
 - Synthesized into a circuit that has this behavior
 - Result is only as good as the tools
- ❑ Build up a hierarchy of modules. Top-level module is your entire design (or the environment to test your design).
- ❑ *Common approach is to use behavioral descriptions for “leaf cells” and structural to build hierarchy.*

Verilog Modules and Instantiation

- ❑ Modules define circuit components.
- ❑ Instantiation defines hierarchy of the design.

```

                                name           port list
                                -----
                                module addr_cell (a, b, cin, s, cout);
                                keywords
                                input      a, b, cin;
                                output    s, cout;
                                port declarations (input, output, or inout)
                                module body
                                -----
                                endmodule

                                module adder (A, B, S);
                                -----
                                Instance of addr_cell
                                addr_cell ac1 ( ... connections ... );
                                -----
                                endmodule

```

Note: A module is not a function in the C sense. There is no call and return mechanism. Think of it more like a hierarchical data structure.

Note: Verilog syntax allows port declarations in port list.

Structural Model - XOR example

module name

```
module xor_gate ( out, a, b );
```

port list

```
  input  a, b;
```

port declarations

```
  output out;
```

```
  wire  aBar, bBar, t1, t2;
```

internal signal declarations

Built-in gates

```
  not invA (aBar, a);
```

instances

```
  not invB (bBar, b);
```

```
  and and1 (t1, a, bBar);
```


```
  and and2 (t2, b, aBar);
```

```
  or  or1 (out, t1, t2);
```

```
endmodule
```

Instance name


Interconnections (note output is first)

 


■ Notes:

- The instantiated gates are not “executed”. They are active always.
- xor gate already exists as a built-in (so really no need to define it).

Structural Example: 2-to1 mux

 

a) 2-input mux symbol

 

b) 2-input mux gate-level circuit diagram

```
/* 2-input multiplexor in gates */  
module mux2 (in0, in1, select, out);  
  input in0,in1,select;  
  output out;  
  wire s0,w0,w1;  
  
  not (s0, select);  
  and (w0, s0, in0),  
      (w1, select, in1);  
  or  (out, w0, w1);  
  
endmodule // mux2
```


**Built-ins don't need
Instance names**

**C++ style
comments**


**Multiple instances can
share the same
"master" name.**

**Built-ins gates can
have > 2 inputs. Ex:
and (w0, a, b, c, d);**

Instantiation, Signal Array, Named ports

 

a) 4-input mux symbol

 

b) 4-input mux implemented with 2-input muxes

```

/* 2-input multiplexor in gates */
module mux2 (in0, in1, select, out);
    input in0,in1,select;
    output out;
    wire s0,w0,w1;
    not (s0, select);
    and (w0, s0, in0),
        (w1, select, in1);
    or (out, w0, w1);
endmodule // mux2
    
```

```

module mux4 (in0, in1, in2, in3, select, out);
input in0,in1,in2,in3;
input [1:0] select;
output out;
wire w0,w1;
mux2
    m0 (.select(select[0]), .in0(in0), .in1(in1), .out(w0)),
    m1 (.select(select[0]), .in0(in2), .in1(in3), .out(w1)),
    m3 (.select(select[1]), .in0(w0), .in1(w1), .out(out));
endmodule // mux4
    
```

Signal array. Declares select[1], select[0]

Named ports. Highly recommended.

Simple Behavioral Model

```
module foo (out, in1, in2);  
  input      in1, in2;  
  output     out;
```

```
  assign out = in1 & in2;
```

```
endmodule
```

“continuous assignment”


**Connects out to be the logical
“and” of in1 and in2.**

The assignment continuously happens, therefore any change on the rhs is reflected in out immediately (except for the small delay associated with the implementation of the &).


Not like an assignment in C that takes place when the program counter gets to that place in the program.

Example - Ripple Adder

```
module FullAdder(a, b, ci, r, co);  
  input a, b, ci;  
  output r, co;  
  
  assign r = a ^ b ^ ci;  
  assign co = a&ci | a&b | b&cin;  
  
endmodule
```

 
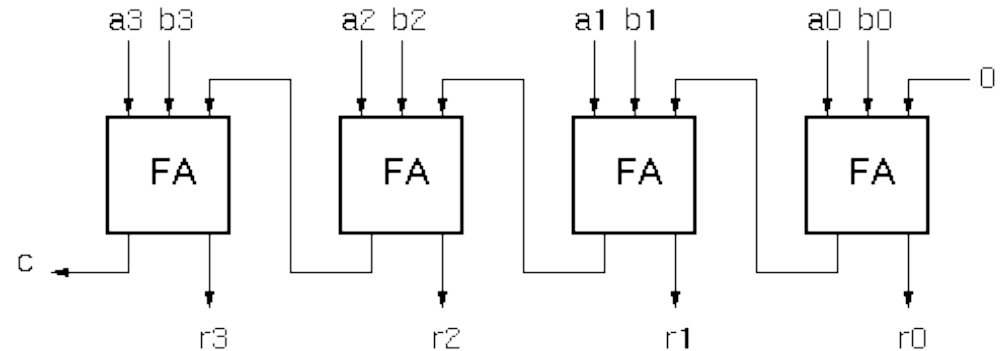
```
module Adder(A, B, R);  
  input [3:0] A;  
  input [3:0] B;  
  output [4:0] R;  
  
  wire c1, c2, c3;  
  FullAdder  
  add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),  
  add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),  
  add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),  
  add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );  
  
endmodule
```



Verilog Operators

Verilog Operator	Name	Functional Group
()	bit-select or part-select	
()	parenthesis	
! ~ & ~& ~ ^ ~^ or ^~	logical negation negation reduction AND reduction OR reduction NAND reduction NOR reduction XOR reduction XNOR	Logical Bit-wise Reduction Reduction Reduction Reduction Reduction Reduction
+ -	unary (sign) plus unary (sign) minus	Arithmetic Arithmetic
{}	concatenation	Concatenation
{{}}	replication	Replication
* / %	multiply divide modulus	Arithmetic Arithmetic Arithmetic
+ -	binary plus binary minus	Arithmetic Arithmetic
<< >>	shift left shift right	Shift Shift

> >= < <=	greater than greater than or equal to less than less than or equal to	Relational Relational Relational Relational
== !=	logical equality logical inequality	Equality Equality
=== !==	case equality case inequality	Equality Equality
&	bit-wise AND	Bit-wise
^ ^~ or ~^	bit-wise XOR bit-wise XNOR	Bit-wise Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional

Verilog Numbers

Constants:

14 ordinary decimal number

-14 2's complement representation

12'b0000_0100_0110 binary number (“_” is ignored)

12'h046 hexadecimal number with 12 bits

Signal Values:

By default, Values are unsigned

e.g., `C[4:0] = A[3:0] + B[3:0];`

if A = 0110 (6) and B = 1010 (treated as 10 not -6)

C = 10000 not 00000

i.e., B is zero-padded, not sign-extended

`wire signed [31:0] x;`

Declares a signed (2's complement) signal array.



Verilog Assignment Types

Continuous Assignment Examples

```
wire [3:0] A, X, Y, R, Z;  
wire [7:0] P;  
wire r, a, cout, cin;
```

```
assign R = X | (Y & ~Z);
```

use of bit-wise Boolean operators

```
assign r = &X;
```

example
reduction
operator

```
assign R = (a == 1'b0) ? X : Y;
```

conditional operator

```
assign P = 8'hff;
```

example constants

```
assign P = X * Y;
```

arithmetic operators (use with care!)

```
assign P[7:0] = {4{X[3]}, X[3:0]};
```

(ex: sign-extension)

```
assign {cout, R} = X + Y + cin;
```

bit field concatenation

```
assign Y = A << 2;
```

bit shift operator

```
assign Y = {A[1], A[0], 1'b0, 1'b0};
```

equivalent bit shift

Non-continuous Assignments

A bit strange from a hardware specification point of view.
Shows off Verilog roots as a simulation language.

“always” block example:

```
module and_or_gate (out, in1, in2, in3);  
  input      in1, in2, in3;  
  output     out;  
  reg       out;
```

“reg” type declaration, needed for always block assignment. Not really a register in this case. Just a Verilog idiosyncrasy.

```
  always @(in1 or in2 or in3) begin  
    out = (in1 & in2) | in3;  
  end
```

“sensitivity” list, triggers the action in the body.

keyword

brackets multiple statements (not necessary in this example).

```
endmodule
```

Isn't this just: `assign out = (in1 & in2) | in3;?`

Why bother?

Always Blocks

Always blocks give us some constructs that are impossible or awkward in continuous assignments.

case statement example:

```
module mux4 (in0, in1, in2, in3, select, out);  
  input in0,in1,in2,in3;  
  input [1:0] select;  
  output      out;  
  reg         out;
```

```
  always @ (in0 in1 in2 in3 select)  
    case (select)  
      2'b00: out=in0;  
      2'b01: out=in1;  
      2'b10: out=in2;  
      2'b11: out=in3;  
    endcase  
endmodule // mux4
```

keyword

The statement(s) corresponding to whichever constant matches "select", get applied.

Couldn't we just do this with nested "if"s?

Well yes and no!

Always Blocks

Nested if-else example:


```
module mux4 (in0, in1, in2, in3, select, out);  
    input in0,in1,in2,in3;  
    input [1:0] select;  
    output      out;  
    reg         out;  
  
    always @ (in0 in1 in2 in3 select)  
        if (select == 2'b00) out=in0;  
        else if (select == 2'b01) out=in1;  
            else if (select == 2'b10) out=in2;  
                else out=in3;  
endmodule // mux4
```

Nested if structure leads to “priority logic” structure, with different delays for different inputs (in3 to out delay > than in0 to out delay).
Case version treats all inputs the same.

Defining Processor ALU in 5 mins

- Modularity is essential to the success of large designs
- High-level primitives enable direct synthesis of behavioral descriptions (functions such as additions, subtractions, shifts (<< and >>), etc.

Example: A 32-bit ALU

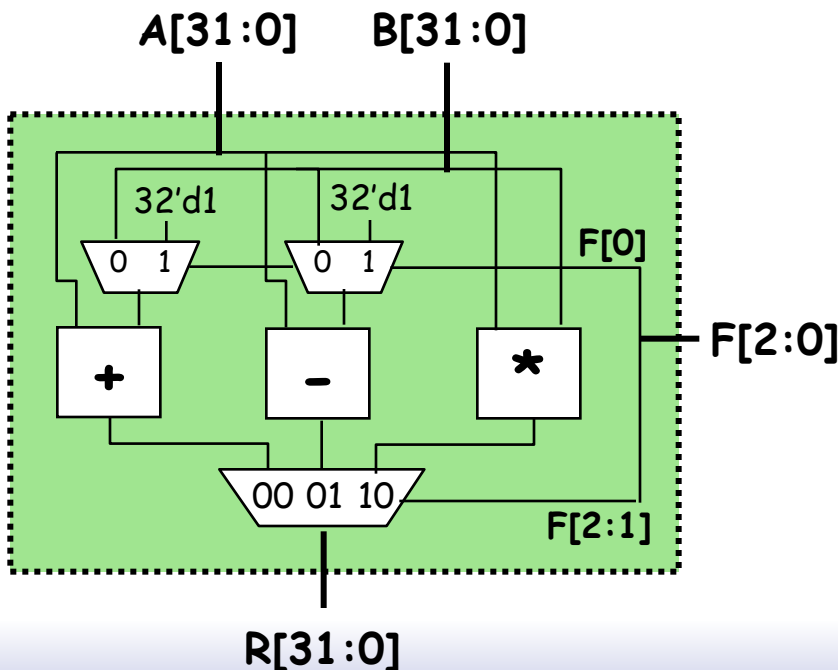

Function Table

F2	F1	F0	Function
0	0	0	A + B
0	0	1	A + 1
0	1	0	A - B
0	1	1	A - 1
1	0	X	A * B

Module Definitions

2-to-1 MUX

```
module mux32two(i0,i1,sel,out);  
input [31:0] i0,i1;  
input sel;  
output [31:0] out;  
  
assign out = sel ? i1 : i0;  
  
endmodule
```

32-bit Adder

```
module add32(i0,i1,sum);  
input [31:0] i0,i1;  
output [31:0] sum;  
  
assign sum = i0 + i1;
```

32-bit Subtractor

```
endmodule  
module sub32(i0,i1,diff);  
input [31:0] i0,i1;  
output [31:0] diff;  
  
assign diff = i0 - i1;  
  
endmodule
```

3-to-1 MUX

```
module mux32three(i0,i1,i2,sel,out);  
input [31:0] i0,i1,i2;  
input [1:0] sel;  
output [31:0] out;  
reg [31:0] out;  
  
always @ (i0 or i1 or i2 or sel)  
begin  
    case (sel)  
        2'b00: out = i0;  
        2'b01: out = i1;  
        2'b10: out = i2;  
        default: out = 32'bx;  
    endcase  
end  
endmodule
```

16-bit Multiplier

```
module mul16(i0,i1,prod);  
input [15:0] i0,i1;  
output [31:0] prod;  
  
// this is a magnitude multiplier  
// signed arithmetic later  
assign prod = i0 * i1;  
  
endmodule
```

Top-Level ALU Declaration

Given submodules:

```

module mux32two(i0,i1,sel,out);
module mux32three(i0,i1,i2,sel,out);
module add32(i0,i1,sum);
module sub32(i0,i1,diff);
module mul16(i0,i1,prod);

```

Declaration of the ALU Module:

```

module alu(a, b, f, r);
input [31:0] a, b;
input [2:0] f;
output [31:0] r;

```

```

wire [31:0] addmux_out, submux_out;
wire [31:0] add_out, sub_out, mul_out;

```

```


mux32two    adder_mux(.io(b), .i1(32'd1), .sel(f[0]), .out(addmux_out));
mux32two    sub_mux(.io(b), .i1(32'd1), .sel(f[0]), .out(submux_out));
add32       our_adder(.i0(a), .i1(addmux_out), .sum(add_out));
sub32       our_subtractor(.i0(a), .i1(submux_out), .diff(sub_out));
mul16       our_multiplier(.i0(a[15:0]), .i1(b[15:0]), .prod(mul_out));
mux32three output_mux(.i0(add_out), .i1(sub_out), .i2(mul_out), .sel(f[2:1]), .out(r));
endmodule

```

module names

(unique) instance names

corresponding wires/regs in module alu

 


intermediate output nodes ●

Top-Level ALU Declaration, take 2

- ❑ No Hierarchy:
- ❑ Declaration of the ALU Module:

 
```
module a1u(a, b, f, r);  
  input [31:0] a, b;  
  input [2:0] f;  
  output [31:0] r;  
  always @ (a or b or f)  
    case (f)  
      3'b000: r = a + b;  
      3'b001: r = a + 1'b1;  
      3'b010: r = a - b;  
      3'b011: r = a - 1'b1;  
      3'b100: r = a * b;  
      default: r = 32'bx;  
    endcase  
endmodule
```




Will this synthesize into 2 adders and 2 subtractors or 1 of each?

Review - Ripple Adder Example
 
```
module FullAdder(a, b, ci, r, co);  
  input a, b, ci;  
  output r, co;  
  
  assign r = a ^ b ^ ci;  
  assign co = a&ci + a&b + b&cin;  
  
endmodule
```


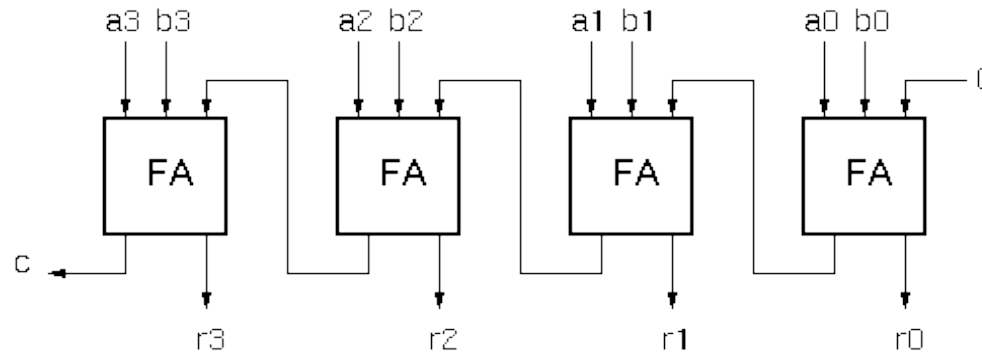
```
module Adder(A, B, R);  
  input [3:0] A;  
  input [3:0] B;  
  output [4:0] R;  
  
  wire c1, c2, c3;  
  FullAdder  
  add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),  
  add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),  
  add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),  
  add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );  
  
endmodule
```



Example - Ripple Adder Generator

Parameters give us a way to generalize our designs. A module becomes a “generator” for different variations. Enables design/module reuse. Can simplify testing.

```
module Adder(A, B, R);  
  parameter N = 4;  
  input [N-1:0] A;  
  input [N-1:0] B;  
  output [N:0] R;  
  wire [N:0] C;
```

Declare a parameter with default value.

Note: this is not a port. Acts like a “synthesis-time” constant.

Replace all occurrences of “4” with “N”.

variable exists only in the specification - not in the final circuit.

```
  genvar i;
```

Keyword that denotes synthesis-time operations

For-loop creates instances (with unique names)

```
  generate
```

```
    for (i=0; i<N; i=i+1) begin:bit
```

```
      FullAdder add(.a(A[i], .b(B[i]), .ci(C[i]), .co(C[i+1]), .r(R[i]));
```

```
    end
```

```
  endgenerate
```

```
  assign C[0] = 1'b0;
```

```
  assign R[N] = C[N];
```

```
endmodule
```

```
Adder adder4 ( ... );
```

```
Adder #(.N(64))
```

```
adder64 ( ... );
```

**Overwrite parameter
N at instantiation.**

More on Generate Loop

Permits variable declarations, modules, user defined primitives, gate primitives, continuous assignments, initial blocks and always blocks to be instantiated multiple times using a for-loop.

```
// Gray-code to binary-code converter
```

```
module gray2bin1 (bin, gray);
```

```
parameter SIZE = 8;
```

```
output [SIZE-1:0] bin;
```

```
input [SIZE-1:0] gray;
```

```
genvar i;
```

```
generate for (i=0; i<SIZE; i=i+1) begin:bit
```

```
assign bin[i] = ^gray[SIZE-1:i];
```

```
end endgenerate
```

```
endmodule
```

variable exists only in the specification - not in the final circuit.

Keywords that denotes synthesis-time operations

For-loop creates instances of assignments

Loop must have constant bounds

generate if-else-if based on an expression that is deterministic at the time the design is synthesized.

generate case : selecting case expression must be deterministic at the time the design is synthesized.

Verilog in EECS 151/251A

- ❑ We use behavioral modeling at the bottom of the hierarchy
- ❑ Use instantiation to 1) build hierarchy and, 2) map to FPGA and ASIC resources not supported by synthesis.
- ❑ Favor continuous assign and avoid always blocks unless:
 - no other alternative: ex: state elements, case
 - helps readability and clarity of code: ex: large nested if else
- ❑ Use named ports.
- ❑ Verilog is a big language. This is only an introduction.
 - Complete IEEE Verilog-Standard document (1364-2005) linked to class website.
 - Harris & Harris book chapter 4 is a good source.
 - ***Be careful of what you read on the web.*** Many bad examples out there.
 - We will be introducing more useful constructs throughout the semester. Stay tuned!