



EECS 151/251A
Spring 2023
Digital Design and
Integrated Circuits

Instructor:
John Wawrzynek

Lecture 7:
Combinational Logic
part 2, FSMs part 1

Announcements

- HW2 being graded.
- HW 3 posted.
- *Wawrzynek office hours moving to Thursday 12:30 starting this week.*

Outline





Combinational Logic:

- ❑ *Boolean Simplification*
- ❑ *Multi-level Logic,*
- ❑ *NAND/NOR*
- ❑ *XOR*


Finite State Machines:

Karnaugh Map Method

  - K-map is a method of representing the TT leading to simplification.



Note: "gray code" labeling.

 

5 & 6 variable k-maps possible

K-map Simplification

1. Draw K-map of the appropriate number of variables (between 2 and 6)
2. Fill in map with function values from truth table.
3. Form groups of 1's.
 - ✓ Dimensions of groups must be even powers of two (1x1, 1x2, 1x4, ..., 2x2, 2x4, ...)
 - ✓ Form as large as possible groups and as few groups as possible.
 - ✓ Groups can overlap (this helps make larger groups)
 - ✓ Remember K-map is periodical in all dimensions (groups can cross over edges of map and continue on other side)
4. For each group write a product term.
 - the term includes the “constant” variables (use the uncomplemented variable for a constant 1 and complemented variable for constant 0)
5. Form Boolean expression as sum-of-products.

Product-of-Sums K-map

1. Form groups of 0's instead of 1's.
2. For each group write a sum term.
 - the term includes the “constant” variables (use the uncomplemented variable for a constant 0 and complemented variable for constant 1)
3. Form Boolean expression as product-of-sums.

		ab			
		00	01	11	10
cd	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1

$$f = (b' + c + d)(a' + c + d')(b + c + d')$$


BCD incrementer example

Binary Coded Decimal

	<i>a b c d</i>	<i>w x y z</i>
0	0000	0001
1	0001	0010
2	0010	0011
3	0011	0100
4	0100	0101
5	0101	0110
6	0110	0111
7	0111	1000
8	1000	1001
9	1001	0000
	1010	- - - -
	1011	- - - -
	1100	- - - -
	1101	- - - -
	1110	- - - -
	1111	- - - -

$\{a,b,c,d\}$

4 ↓

 

4 ↓

$\{w,x,y,z\}$

BCD Incrementer Example

- ❑ Note one map for each output variable.
- ❑ Function includes “don’t cares” (shown as “-” in the table).
 - These correspond to places in the function where we don’t care about its value, because we don’t expect some particular input patterns.
 - We are free to assign either 0 or 1 to each don’t care in the function, as a means to increase group sizes.
- ❑ In general, you might choose to write product-of-sums or sum-of-products according to which one leads to a simpler expression.

BCD incrementer example

W

		ab			
cd		00	01	11	10
	00	0	0	-	1
	01	0	0	-	0
	11	0	1	-	-
	10	0	0	-	-

X

		ab			
cd		00	01	11	10
	00	0	1	-	0
	01	0	1	-	0
	11	1	0	-	-
	10	0	1	-	-

w =

x =

y

		ab			
cd		00	01	11	10
	00	0	0	-	0
	01	1	1	-	0
	11	0	0	-	-
	10	1	1	-	-



Z

		ab			
cd		00	01	11	10
	00	1	1	-	1
	01	0	0	-	0
	11	0	0	-	-
	10	1	1	-	-

y =

z =

Higher Dimensional K-maps

  





Boolean Simplification – Multi-level Logic

Multi-level Combinational Logic

 - Example: reduced sum-of-products form
 $x = adf + aef + bdf + bef + cdf + cef + g$
- Implementation in 2-levels with gates:
cost: 1 7-input OR, 6 3-input AND
=> ~50 transistors
delay: 3-input AND gate delay + 7-input OR gate delay



 - Factored form:
 $x = (a + b + c)(d + e)f + g$
cost: 1 3-input OR, 2 2-input OR, 1 3-input AND
=> ~20 transistors
delay: 3-input OR + 3-input AND + 2-input OR




Footnote: NAND would be used in place of all ANDs and ORs.

Which is faster?

*In general: Using multiple levels (more than 2) will reduce the cost. Sometimes also delay.
Sometimes a tradeoff between cost and delay.*


Multi-level Combinational Logic

 Another Example: $F = abc + abd + a'c'd' + b'c'd'$



$$\text{let } x = ab \quad y = c+d$$

$$f = xy + x'y'$$

 

Incorporates fanout.

No convenient hand methods exist for multi-level logic simplification:

a) CAD Tools use sophisticated algorithms and heuristics

Guess what? These problems tend to be NP-complete

b) Humans and tools often exploit some special structure (example adder)

NAND-NAND & NOR-NOR Networks





DeMorgan's Law Review:

$$(a + b)' = a' b'$$

$$a + b = (a' b')'$$

$$(a b)' = a' + b'$$

$$(a b) = (a' + b')'$$

    


push bubbles or introduce in pairs or remove pairs:

$$(x')' = x.$$

NAND-NAND & NOR-NOR Networks


- Mapping from AND/OR to NAND/NAND

 

Multi-level Networks

Convert to NANDs:

$$F = a(b + cd) + bc'$$


 


EXOR Function Implementations



Parity, addition mod 2

$$x \oplus y = x'y + xy'$$

x	y	xor	xnor
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

  

Another approach:

  

if $x=0$ then y else y'





Finite State Machines



Finite State Machines (FSMs)

FSMs:

  - Can model behavior of any sequential circuit
- Useful representation for designing sequential circuits
- As with all sequential circuits: output depends on present *and* past inputs
 - effect of past inputs represented by the current *state*
- Behavior is represented by **State Transition Diagram**:
 - traverse one edge per clock cycle.



FSM Implementation

  


- ❑ Flip-flops form *state register*
- ❑ number of states $\leq 2^{\text{number of flip-flops}}$
- ❑ CL (combinational logic) calculates next state and output
- ❑ **Remember: The FSM follows exactly one edge per cycle.**

Later we will learn how to implement in Verilog. Now we learn how to design “by hand” to the gate level.


FSM Example: Parity Checker

A string of bits has “even parity” if the number of 1's in the string is even.

 - Design a circuit that accepts a infinite serial stream of bits, and outputs a 0 if the parity thus far is even and outputs a 1 if odd:





 example: 0 0 1 1 1 0 1
 even even odd even odd odd even




Next we take this example through the “formal design process”. But first, can you guess a circuit that performs this function?

By-hand Design Process (a)

  

“State Transition Diagram”

 
- circuit is in one of two “states”.
- transition on each cycle with each new input, over exactly one arc (edge).
- Output depends on which state the circuit is in.



By-hand Design Process (b)

State Transition Table:

<i>present state</i>	<i>OUT</i>	<i>IN</i>	<i>next state</i>
<i>EVEN</i>	<i>0</i>	<i>0</i>	<i>EVEN</i>
<i>EVEN</i>	<i>0</i>	<i>1</i>	<i>ODD</i>
<i>ODD</i>	<i>1</i>	<i>0</i>	<i>ODD</i>
<i>ODD</i>	<i>1</i>	<i>1</i>	<i>EVEN</i>

 

Invent a code to represent states:

Let 0 = EVEN state, 1 = ODD state

<i>present state (ps)</i>	<i>OUT</i>	<i>IN</i>	<i>next state (ns)</i>
0	0	0	0
0	0	1	1
1	1	0	1
1	1	1	0

Derive logic equations from table (how?):

$$OUT = PS$$

$$NS = PS \text{ xor } IN$$

By-hand Design Process (c)


Logic equations from table:

$$OUT = PS$$

$$NS = PS \text{ xor } IN$$

□ Circuit Diagram:

 - XOR gate for NS calculation
- Flip-Flop to hold present state
- no logic needed for output in this example.



“Formal” By-hand Design Process

Review of Design Steps:

1. Specify **circuit function** (English)
2. Draw **state transition diagram**
3. Write down **symbolic state transition table**
4. Write down **encoded state transition table**
5. Derive **logic equations**
6. Derive **circuit diagram**


Register to hold state

Combinational Logic for Next State and Outputs



Another FSM Design Example


Combination Lock Example

 

- Used to allow entry to a locked room:
2-bit serial combination. Example 01,11:
 1. Set switches to 01, press ENTER
 2. Set switches to 11, press ENTER
 3. OPEN is asserted (OPEN=1).

If wrong code, ERROR is asserted (after second combo word entry).
Press Reset at anytime to try again.

Combinational Lock STD

 


Assume the ENTER button when pressed generates a pulse for only one clock cycle.

Symbolic State Transition Table

RESET	ENTER	COM1	COM2	Preset State	Next State	OPEN	ERROR
0	0	*	*	START	START	0	0
0	1	0	*	START	BAD1	0	0
0	1	1	*	START	OK1	0	0
0	0	*	*	OK1	OK1	0	0
0	1	*	0	OK1	BAD2	0	0
0	1	*	1	OK1	OK2	0	0
0	*	*	*	OK2	OK2	1	0
0	0	*	*	BAD1	BAD1	0	0
0	1	*	*	BAD1	BAD2	0	0
0	*	*	*	BAD2	BAD2	0	1
1	*	*	*	*	START	0	0

 Decoder logic for checking combination (01,11):




* represents "wild card" - expands to all combinations

Encoded ST Table

ENTER	COM1	COM2	PS2	PS1	PS0	NS2	NS1	NS0
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0
1	0	0	0	0	0	1	0	0
1	0	1	0	0	0	1	0	0
1	1	0	0	0	0	0	0	1
1	1	1	0	0	0	0	0	1
0	0	0	0	0	1	0	0	1
0	0	1	0	0	1	0	0	1
0	1	0	0	0	1	0	0	1
0	1	1	0	0	1	0	0	1
1	0	0	0	0	1	1	0	1
1	1	0	0	0	1	1	0	1
1	0	1	0	0	1	0	1	1
1	1	1	0	0	1	0	1	1
0	0	0	0	1	1	0	1	1
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	0	1	1	0	1	1
1	0	0	0	1	1	0	1	1
1	0	1	0	1	1	0	1	1
1	1	0	0	1	1	0	1	1
1	1	1	0	1	1	0	1	1
0	0	0	1	0	0	1	0	0
0	0	1	1	0	0	1	0	0
0	1	0	1	0	0	1	0	0
0	1	1	1	0	0	1	0	0
1	0	0	1	0	0	1	0	1
1	0	1	1	0	0	1	0	1
1	1	1	1	0	0	1	0	1
0	0	0	1	0	1	1	0	1
0	0	1	1	0	1	1	0	1
0	1	0	1	0	1	1	0	1
0	1	1	1	0	1	1	0	1
1	0	0	1	0	1	1	0	1
1	0	1	1	0	1	1	0	1
1	1	0	1	0	1	1	0	1
1	1	1	1	0	1	1	0	1

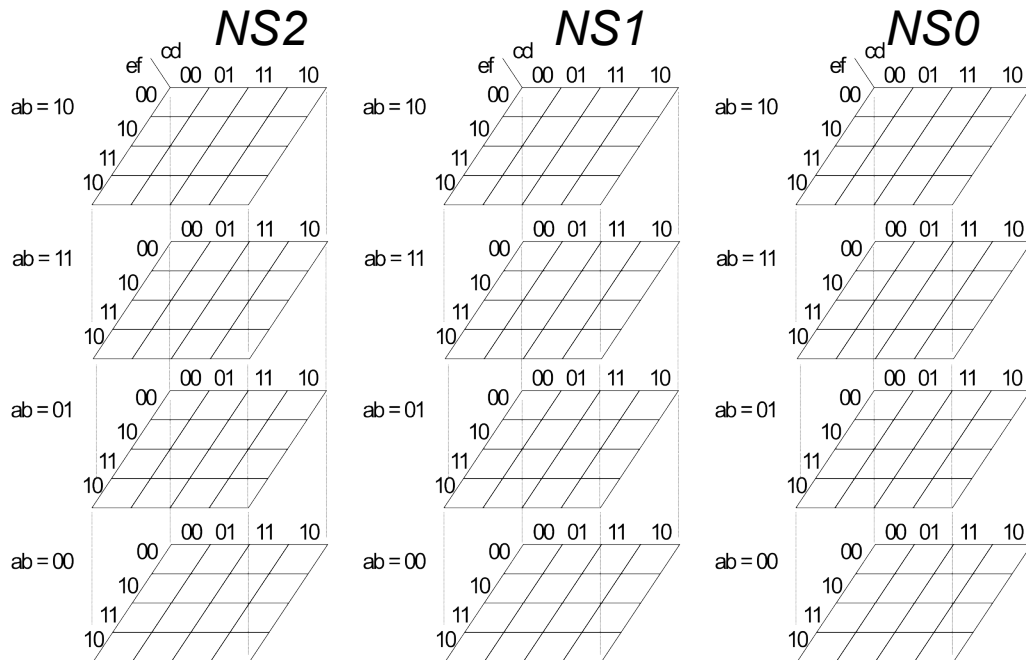- **Assign states:**
START=000, OK1=001, OK2=011
BAD1=100, BAD2=101
- **Omit reset.** Assume that primitive flip-flops has reset input.
- **Rows not shown have don't cares in output.**
Correspond to invalid PS values.



- **What are the output functions for OPEN and ERROR?**