

Introduction to Formal Verification and Logic Synthesis

Yukio Miyasaka

Contents

Formal Verification

- Equivalence Checking
 - Binary Decision Diagram
 - Boolean Satisfiability Problem

Logic Synthesis

- Two-Level Logic Synthesis
- Two-Level Logic to Multi-Level Logic
- Multi-Level Logic Optimization

Formal Verification

- Prove that a given logic circuit meets some given properties
- Often compared to random simulation, here are some tradeoffs:

	Formal Verification	Random Simulation
Coverage	100%	#test patterns / #all possible patterns
Time	$\sim O(\exp(\text{circuit size}))$	$O(\text{\#test patterns} * \text{circuit size})$

Note: coverage has a different meaning for bounded model checking




Equivalence Checking

- Given two implementations, prove they are functionally equivalent
 - For simplicity, assume the implementations are combinational logic circuits
 - Optimized implementation v.s. Golden model (Spec)
- Exhaustive simulation is enough to prove this property
- However, it takes an exponential amount of time
 - N inputs $\rightarrow 2^N$ patterns to simulate
 - $O(\exp(\#\text{inputs}))$
- Can we do it better?

Binary Decision Diagram (BDD)

- Binary tree
- Redundant nodes (equivalent cofactors) are removed
- Each node has a unique function


x_1	x_2	x_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

   


Randal E. Bryant, "Symbolic Boolean manipulation with ordered binary-decision diagrams," in ACM Computing Surveys, vol. 24, no. 3, pp. 293–318, 1992.

BDD Operations


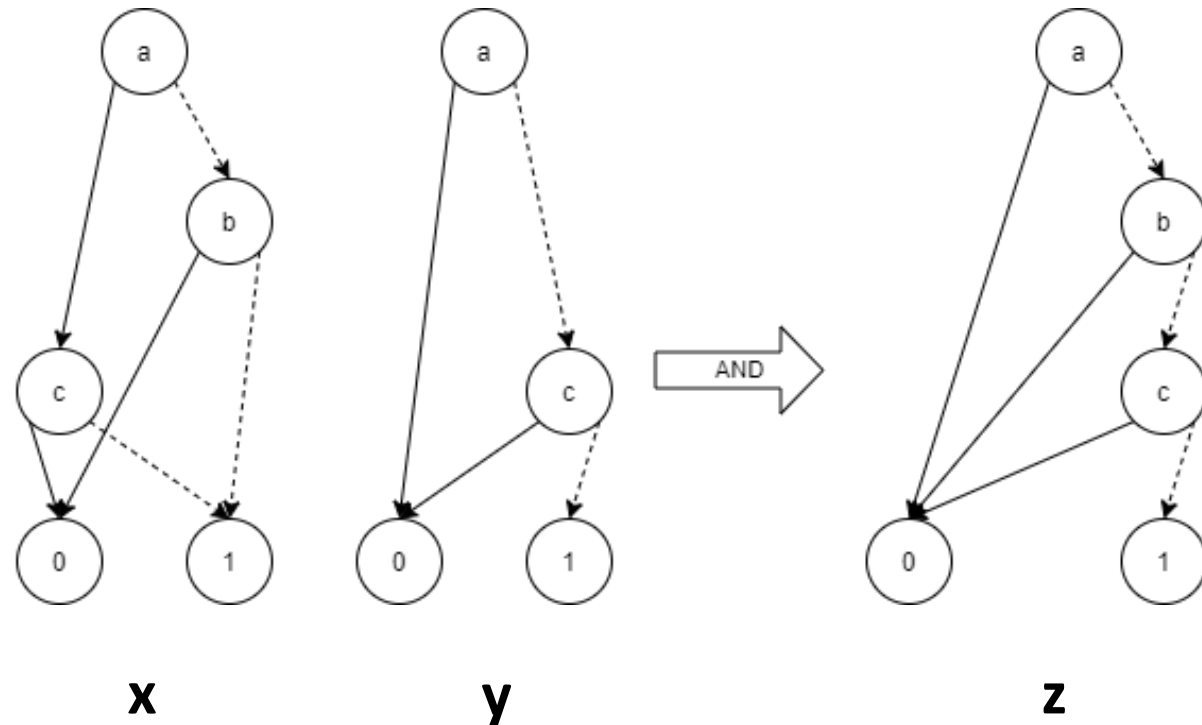
- We can construct a BDD for the result of operation by a recursive procedure
 - e.g. $\text{BDD } z = \text{AND}(\text{BDD } x, \text{BDD } y);$
- Runtime is bounded by $O(\#\text{BDD nodes})$ while $\#\text{BDD nodes}$ is usually smaller than $\exp(\#\text{inputs})$



Symbolic Simulation

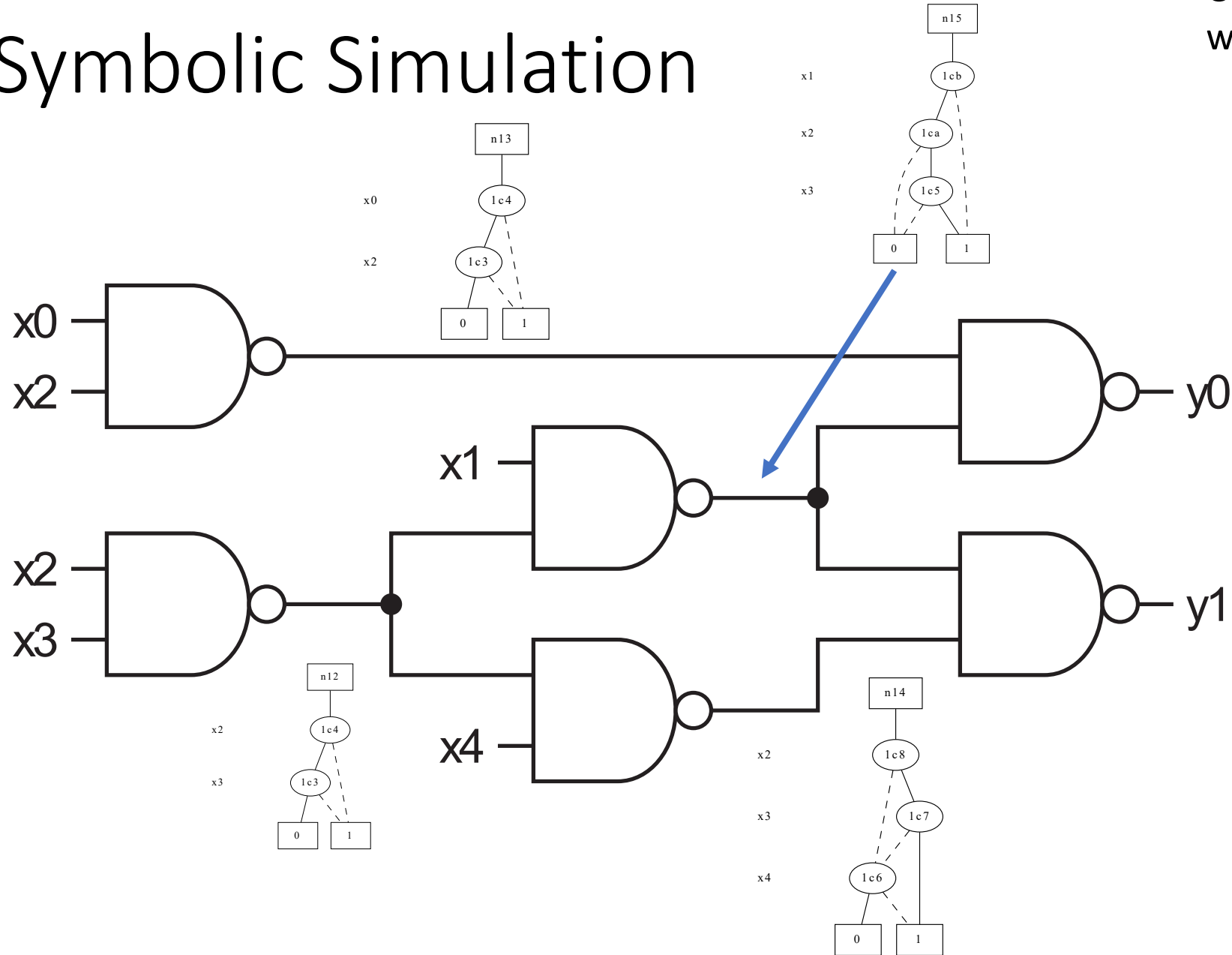

  
Output BDDs to be compared with the golden model



Boolean Satisfiability Problem


- Problem definition $\exists \vec{x}. f(\vec{x}) = 1.$
- One of the most famous NP-complete problems
- $f(\vec{x})$ is usually given as CNF (Conjunctive Normal Form) a.k.a. POS
 - Variable x_1, x_2, \dots
 - Literal $x_1, x'_1, x_2, x'_2, \dots$
 - Clause $x_1 + x'_2 + x_3, \dots$
 - CNF $(Clause A) \cdot (Clause B) \cdot \dots$
- Many heuristics have been proposed
- Can be solved much faster than the other NP-complete problems

History of SAT Solver Improvement

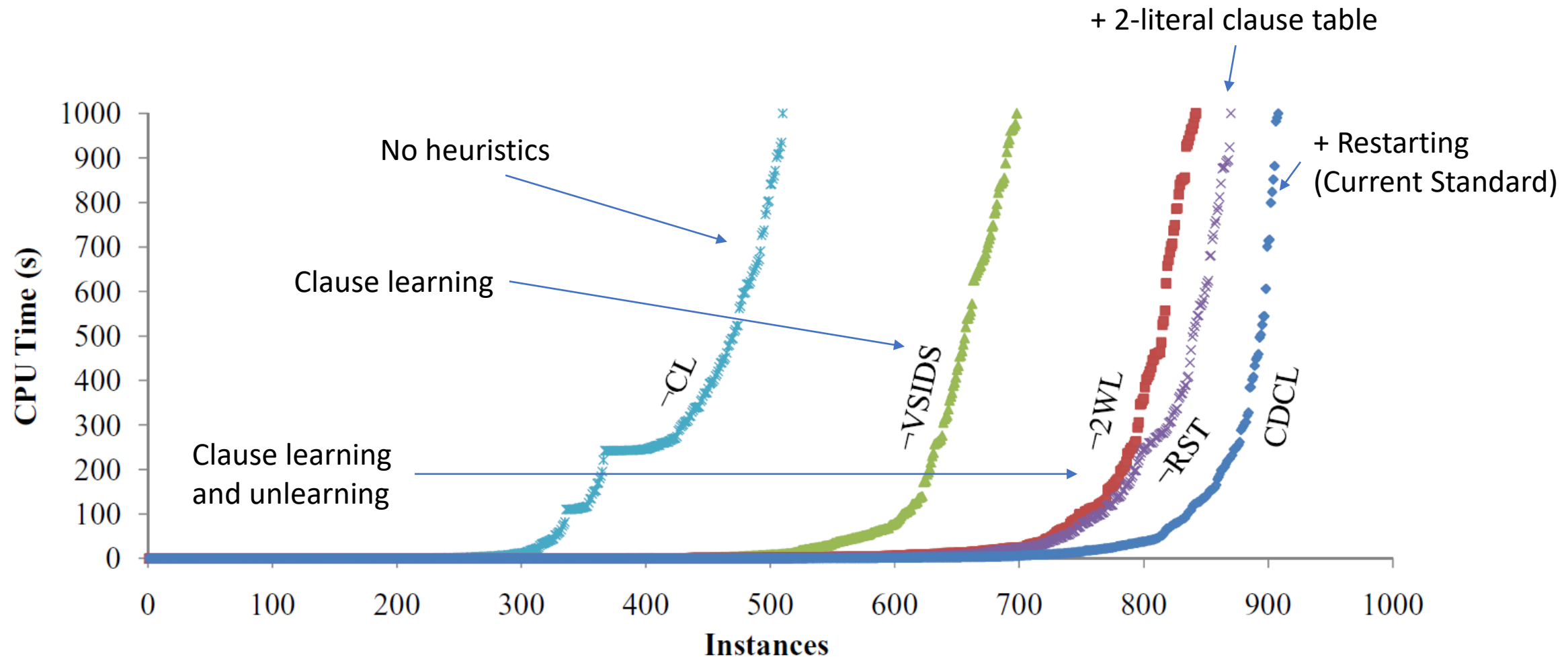


H. Katebi, K. A. Sakallah, and J. P. Marques-Silva, "Empirical study of the anatomy of modern sat solvers," in Proc. 14th SAT, 2011, pp.343-356.

SAT-based Equivalence Checking

 
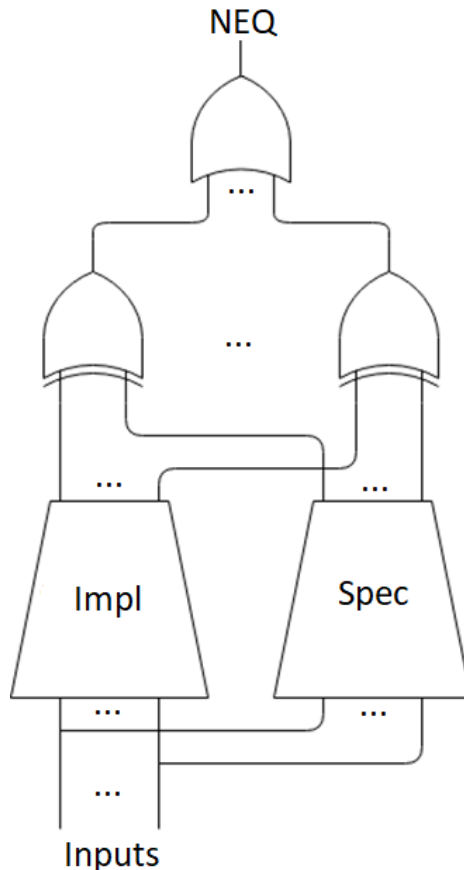
$$f_{AND} = (a' + b' + c)(a + c')(b + c')$$



MITER Circuit

Solve

$$\exists \overrightarrow{Inputs}, \overrightarrow{Internal}. \\ f_{MITER}(\overrightarrow{Inputs}, \overrightarrow{Internal}, NEQ) \cdot NEQ.$$

If satisfiable, there exists a pattern where two circuits output different values.

If unsatisfiable, two circuits are equivalent.

Performance Comparison

- For i10 benchmark (257 inputs, 224 outputs, about 2000 gates)
 - Exhaustive simulation: Never ends ($2^{257} > 10^{25}$ patterns)
 - Symbolic simulation: 0.65 sec
 - SAT-based: 0.43 sec
- SAT-based method is usually faster than symbolic simulation
- Exceptions are arithmetic circuits like multipliers

Logic Synthesis

Logic Synthesis

- Generates a logic circuit from various kinds of descriptions such as truth table, Boolean expression, etc.
- Important metrics: area (#gates) and depth (#levels)

Two-Level Logic


- AND gates in the first level, OR gates in the second level
- Direct representation of SOP
- The basic strategy is the same as Karnaugh map
- However, for more than one output, we have to care logic sharing
 - $x = a + a'bc, \quad y = b'c + a'bc$ is better than
 - $x = a + bc, \quad y = b'c + a'c$
- ESPRESSO heuristic logic minimizer:
 - Developed by Robert K. Brayton (emeritus professor at UC Berkeley)
 - <https://ptolemy.berkeley.edu/projects/embedded/pubs/downloads/espresso/index.htm>
 - Incompatible with modern C compilers, while you can find a patched version on GitHub or other websites

ESPRESSO: Example

test.pla

```
.i 3  
.o 2  
.p 8  
000 00  
001 01  
010 00  
011 11  
100 10  
101 11  
110 10  
111 10  
.e
```

espresso test.pla > out.pla

 

out.pla

```
.i 3  
.o 2  
.p 3  
-01 01  
011 11  
1-- 10  
.e
```

Two-Level Logic to Multi-Level Logic

- We can reduce #gates by factoring
 - $y = b'c + a'c = (b' + a')c$
- **Fast Extract** is a greedy algorithm for factoring
 - For each pair of products, calculate divisors
 - $(abc, a'bc') \rightarrow \text{divisors} = \{ac + a'c', b\}$
 - For each divisor, count how many literals it can save
 - Factor out the divisor that can save the most
 - Repeat until no more factoring is possible
 - (Some details are omitted)

Fast Extract: Example

- 5-input majority function: $abc + abd + abe + acd + \dots$
 - Factoring out a single variable can save 5 literals, while sum of two variables can save 10 literals
- Factor out $a + b$
 - $(a + b)(cd + ce + de) + abc + abd + abe + cde$
- Factor out ab
 - $(a + b)(cd + ce + de) + ab(c + d + e) + cde$
- Factor out $c + d$
 - $(a + b)(cd + (c + d)e) + ab((c + d) + e) + cde$
- After handling trivial cases where cd is shared, we get 12 gate implementation:
 - First level: $n_0 = a + b, n_1 = ab, n_2 = c + d, n_3 = cd$
 - Second level: $n_4 = n_2e, n_5 = n_2 + e, n_6 = n_3e$
 - Third level: $n_7 = n_3 + n_4, n_8 = n_1n_5$
 - Forth level: $n_9 = n_0n_7, n_{10} = n_8 + n_6$
 - Fifth level: $n_{11} = n_9 + n_{10}$

Multi-Level Logic Optimization

- Fast Extract is not optimal
 - Quality depends on the initial SOP
 - What if multiple divisors can save the same number of literals?
 - One of them might lead to a better result in the end
- Rewriting is one of the most popular optimization methods
 - Extract a subcircuit (4-5 inputs) iteratively
 - Replace it with an equivalent precomputed minimum circuit
 - How can we precompute the minimum circuit?


Exact Synthesis

- Encode all possible circuits of N gates into a CNF
- Let a SAT solver find one that is equivalent to the specification


- If the solver cannot find one with $N-1$ gates but one with N gates, the latter one is proven to be minimum

- There are many encoding methods


Exact Synthesis Encoding

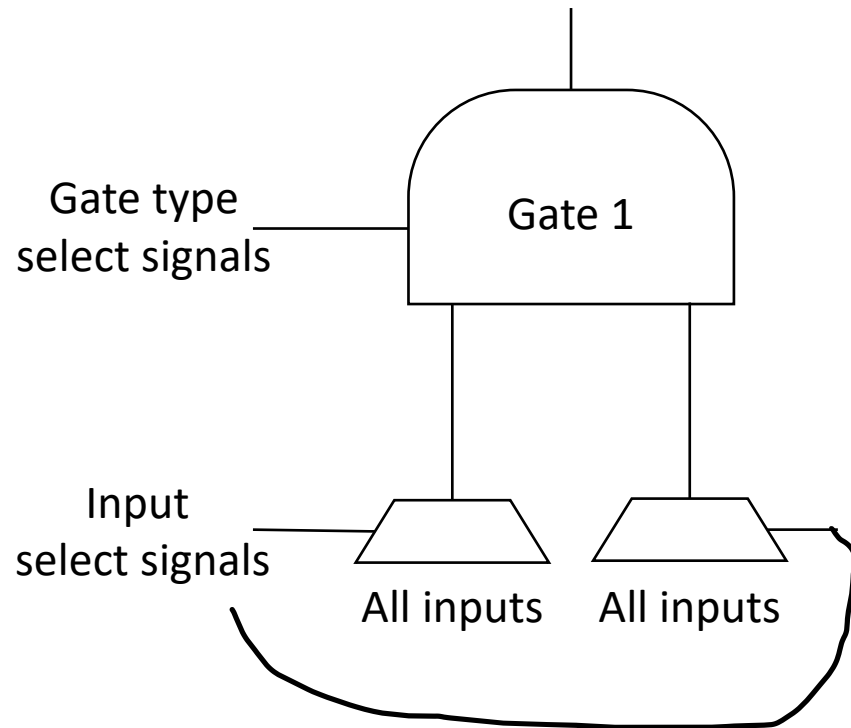

Exact Synthesis Encoding

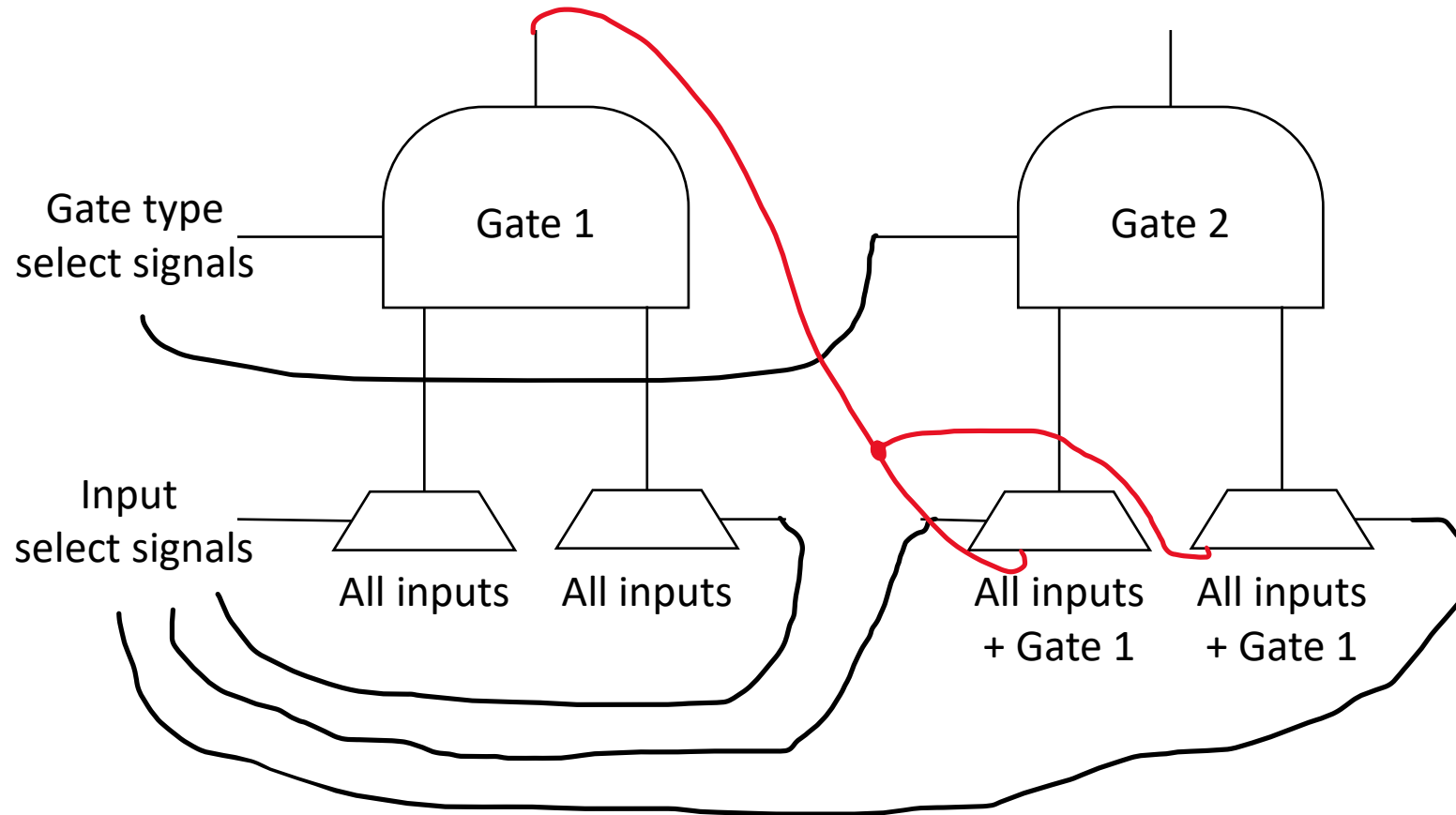


Exact Synthesis Encoding

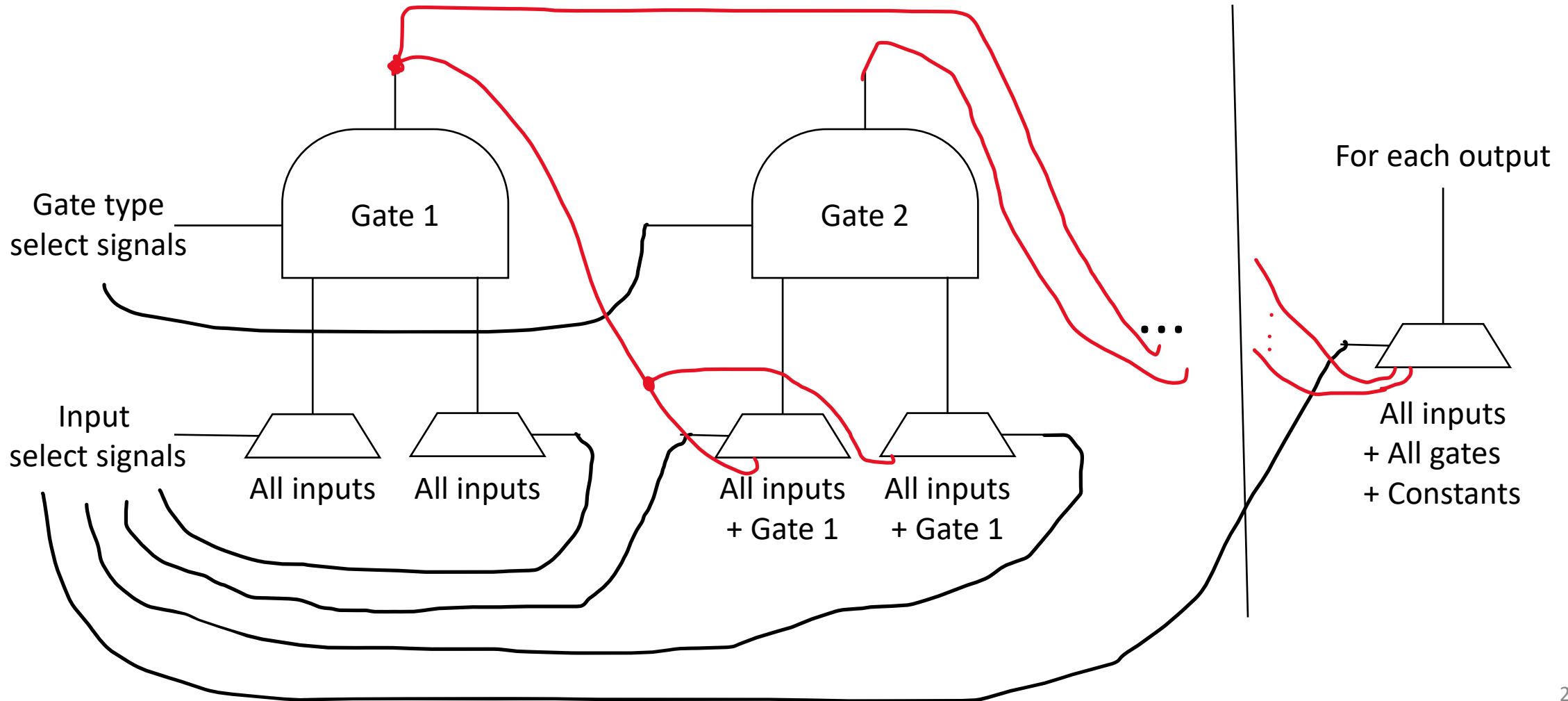

Exact Synthesis Encoding

Solve
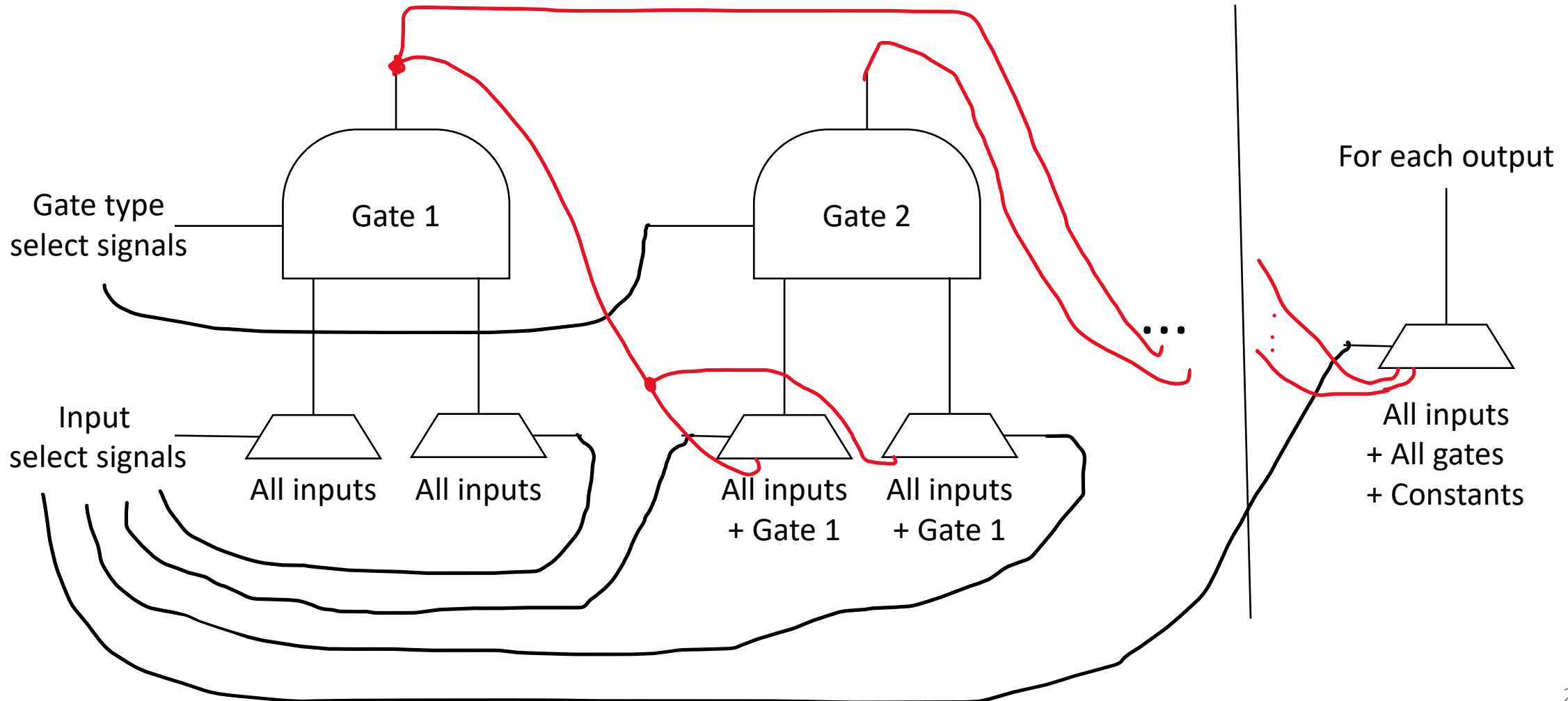
$$f(\overrightarrow{Inputs}, \overrightarrow{Select\ signals}) = Spec(\overrightarrow{Inputs}).$$



More About Logic Optimization

- Exact synthesis works up to 5 gates.
- Rewriting is local optimization, does not necessarily lead to the global optimal
- There are many other optimization methods
 - Merge equivalent internal nodes
 - Substitute one node with a new subcircuit
 - Compute internal don't-cares using BDD, and perform equivalent transformation
- Phase ordering problem
 - Once you apply one optimization, some other optimizations may be no longer effective
 - The effective order varies by circuits
 - Machine learning to find a good optimization order?