

UNIVERSITY OF CALIFORNIA
College of Engineering
Department of Electrical Engineering and Computer Sciences
NTU IC-776CA

B. E. BOSER

Homework 1
Due Thursday, Sep 22, 2005

EECS 247
Fall 2005


Note: You need to show zoom-in plots of your filter response around the passband and stopband corners, for both MATLAB and SPICE results, to demonstrate that you meet the specs.

Design a 2nd order (i.e. single biquad) bandpass filter with 1MHz center frequency and 250kHz 3dB-bandwidth.

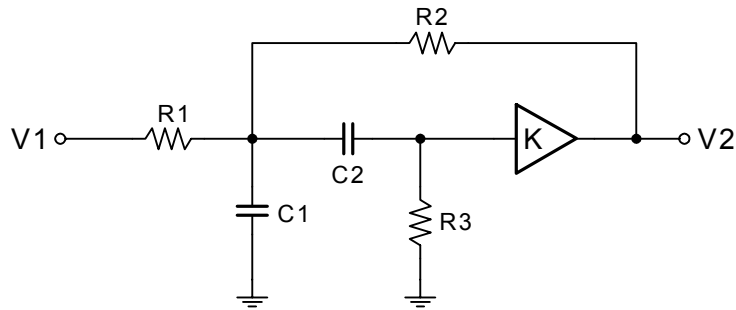- a) Calculate ω_P and Q_P .
- b) Plot a 3D perspective view of the magnitude response of the filter.
- c) Implement the filter with a 2nd order Sallen-Key section (see next page). Calculate all element values and the amplifier gain K . For simplicity make all capacitors 1pF and choose all resistors equal size. Calculate also the resulting filter gain G .
- d) Verify the transfer function with SPICE for nominal values and with a 5% variation of K . By how much are ω_P and Q_P changing?
- e) Calculate the sensitivity $S_K^{Q_P}$ and compare the analytical and simulation results.
- f) Return to nominal component values but add two 5% shunt capacitors from both terminals of C_2 to ground. By how much are ω_P and Q_P changing?

(The Sallen-Key bandpass filter design equations are shown on the next page)

Second-order Sallen-Key bandpass section:



Design equations:

Transfer function
$$H_{BP}(s) = \frac{G \frac{\omega_0}{Q} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

Center frequency
$$\omega_0 = \sqrt{\frac{R_1 + R_2}{R_1 R_2 R_3 C_1 C_2}}$$

Quality factor
$$Q = \frac{\omega_0}{\frac{1}{R_1 C_1} + \frac{1}{R_3 C_2} + \frac{1}{R_3 C_1} + \frac{1-K}{R_2 C_1}}$$

Gain
$$G = \frac{\frac{K}{R_1 C_1}}{\frac{1}{R_1 C_1} + \frac{1}{R_3 C_2} + \frac{1}{R_3 C_1} + \frac{1-K}{R_2 C_1}}$$