

UNIVERSITY OF CALIFORNIA  
 College of Engineering  
 Department of Electrical Engineering and Computer Sciences  
 NTU IC-776CA

Homework 3

EECS 247

B. E. BOSER



Due Thursday, Oct 20, 2005

□ Fall 2005

1. A full-scale sine wave with frequency  $f_x=7\text{MHz}$  is input to a DAC clocked at  $f_s=20\text{MHz}$ . Calculate the frequency and amplitude (relative to full-scale input) of all tones in the DAC output up to  $f=50\text{MHz}$ . Assume the DAC output for each sample is held for  $30\text{ns}$  and returned to zero for  $20\text{ns}$ . Ignore quantization noise and other non-idealities.

2. For the differential switched-capacitor integrator below, find the z-domain output/input transfer function assuming:

- a) Output is sampled in  $\Phi_1$
- b) Output is sampled in  $\Phi_2$
- c) For output sampled in  $\Phi_2$ , find the continuous-time equivalent for the integrator time-constant using the output expression derived. Assume  $f_{\text{signal}}/f_{\text{sampling}} \ll 1$ .

