

Overview

- Building behavioral models in stages
- A 5th-order, 1-Bit $\Sigma\Delta$ modulator
 - Noise shaping
 - Complex loop filters
 - Stability
 - Voltage scaling



Building Models in Stages

- When modeling a complex system like a 5th-order $\Sigma\Delta$ modulator, model development proceeds in stages
 - Each stage builds on its predecessor
- The design goal is to detect and eliminate problems at the highest possible level of abstraction
 - Each successive stage consumes progressively more engineering time



Building Models in Stages

- Rework and reverification of early stage models because of problems found in later stages is expensive
 - Defective silicon is much more expensive (and often fatal)
- Don't launch a multistage rework cycle every time you find a single bug

Building Models in Stages

- Our $\Sigma\Delta$ model development proceeds in stages:
 - Stage 0 gets to the starting line
 - Stage 1 develops a practical system built with ideal subcircuits
 - Stage 2 models key subcircuit nonidealities and translates the results into real-world subcircuit performance specifications

Building Models in Stages

- Real-world model development includes a critical stage 3:
 - Adding elements to earlier stages (hopefully only stage 2) to model significant surprises found in silicon
- The previous lecture introduced much of the stage 0 $\Sigma\Delta$ model and 1-Bit quantization background
 - What other steps are needed to arrive at a successful design?



Stage 0

- Collect references
 - Important references
 - Readable references
 - Talk to veterans to find them and sort them
- Understand the readable references
 - Build a simple model of what you think you understand
 - Start building diagnostic infrastructure



Stage 0 Models

- You can't just talk about stage 0 models with veterans and look at their stage 0 simulations
 - You've got to exercise and think with the model until you can begin to explain surprises by yourself
 - Then, in stage 1, you can ask a veteran more intelligent questions
- Stage 0 model code (download code used for last lecture) is 20% modulator loop code, 80% diagnostics
 - This ratio holds for all stages of modeling



Stage 1

- In stage 1, we'll study a model for a practical $\Sigma\Delta$ modulator topology built with ideal blocks
- Stage 1 model focus
 - Signal amplitudes
 - Stability
 - Worst-case inputs
 - Unstable systems can't graduate to stage 2
 - Quantization noise shaping



Stage 1 Models

Building the infrastructure to generate worst-case inputs and analyze model responses is of critical importance in stage 1

- You must tap into your organization's technical wisdom to learn what those worst-case real world inputs are

Models can only tell you the right answers if you ask them the right questions!



$\Delta\Sigma$ Modulator Filter Design

- Procedure
 - Establish requirements
 - Design noise-transfer function, NTF
 - Determine loop-filter, H
 - Synthesize filter
 - Evaluate performance, stability

Ref: R. W. Adams and R. Schreier, "Stability Theory for $\Delta\Sigma$ Modulators," in Delta-Sigma Data Converters, S. Norsworthy et al. (eds), IEEE Press, 1997, pp. 141-164.




Modulator Specification

- Example: Audio ADC
 - Dynamic range DR 16 Bits
 - Signal bandwidth B 20 kHz
 - Nyquist frequency f_N 44.1 kHz
 - Modulator order L 5
 - Oversampling ratio $M = f_s/f_N$ 64
 - Sampling frequency f_s 2.822 MHz
- The oversampling ratio M chosen based on
 - SQNR > 120dB (20dB below thermal noise)
 - Experience (e.g. Figure 4.14 in Adams & Schreier)




Modulator Block Diagram

 


Noise Transfer Function, NTF(z)
 
```
% stop-band attenuation ...  
% reduce if design is not stable  
  
Rstop = 80;  
[b,a] = cheby2(L, Rstop, 1/M, 'high');  
  
% normalize (for causality)  
b = b/b(1);  
NTF = filt(b, a, 1/fs);  
  
% check stability (mag < 1.5)  
[mag] = bode(NTF, pi*fs)  
  
>> mag = 1.32
```




Loop-Filter, H(z)
 
```
H = inv(NTF) - filt(1, 1, 1/fs);  
  
% check causality ... y(1) should be 0  
y = impulse(H);  
y = y(1)  
  
>> y = 0
```



Filter Topology

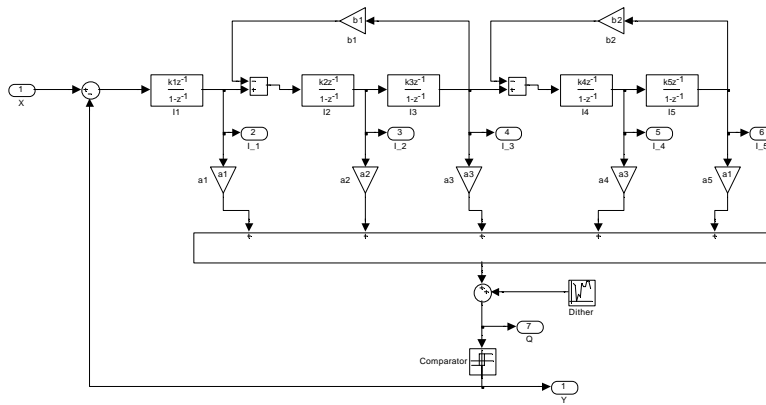


Rounded Filter Coefficients


$$\begin{aligned}
 a_1 &= 1; & k_1 &= 1; & b_1 &= 1/1024; \\
 a_2 &= 1/2; & k_2 &= 1; & b_2 &= 1/16 - 1/64; \\
 a_3 &= 1/4; & k_3 &= 1/2; \\
 a_4 &= 1/8; & k_4 &= 1/4; \\
 a_5 &= 1/8; & k_5 &= 1/8;
 \end{aligned}$$


Ref: Nav Sooch, Don Kerth, Eric Swanson, and Tetsuro Sugimoto, "Phase Equalization System for a Digital-to-Analog Converter Using Separate Digital and Analog Sections", U.S. Patent 5061925, 1990, figure 3 and table 1.

5th-Order Noise Shaping

 

5th-Order Noise Shaping

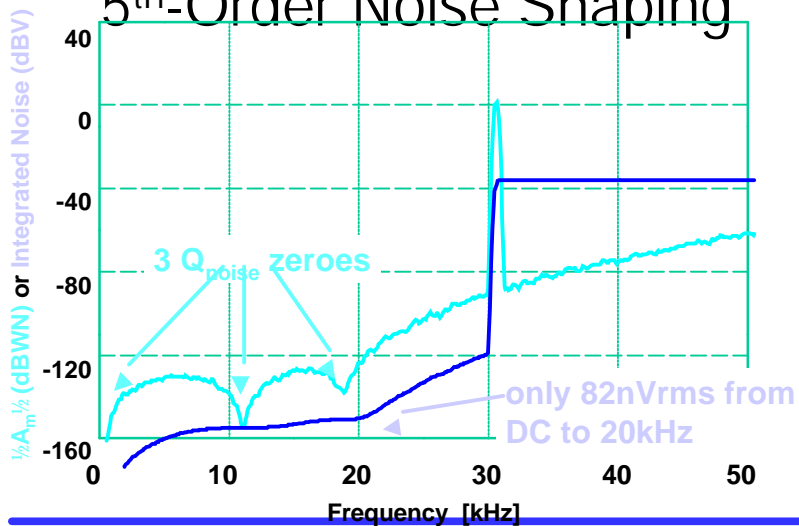


 


5th-Order Noise Shaping

- The 1Vrms 1-Bit quantization noise is shaped to sum to only 82nVrms in the audio band
 - That's over 140dB of dynamic range
- $\Sigma\Delta$ modulators are usually designed so that their quantization noise is negligible in the frequency band of interest
 - Thermal noise sources dominate
- Let's look at the loop filter transfer function...


5th-Order Loop Filter

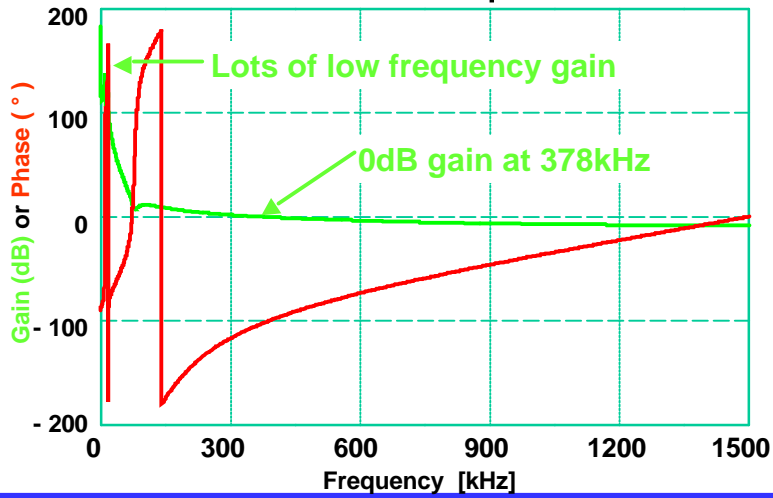

5th-Order Loop Filter

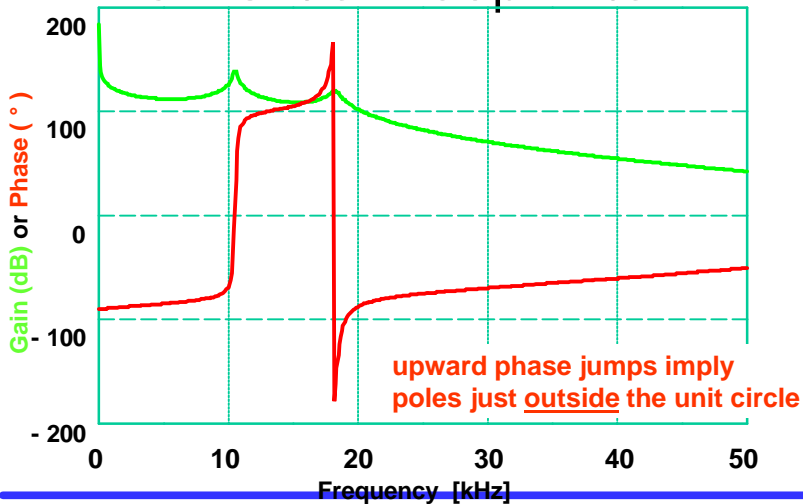

5th-Order Loop Filter

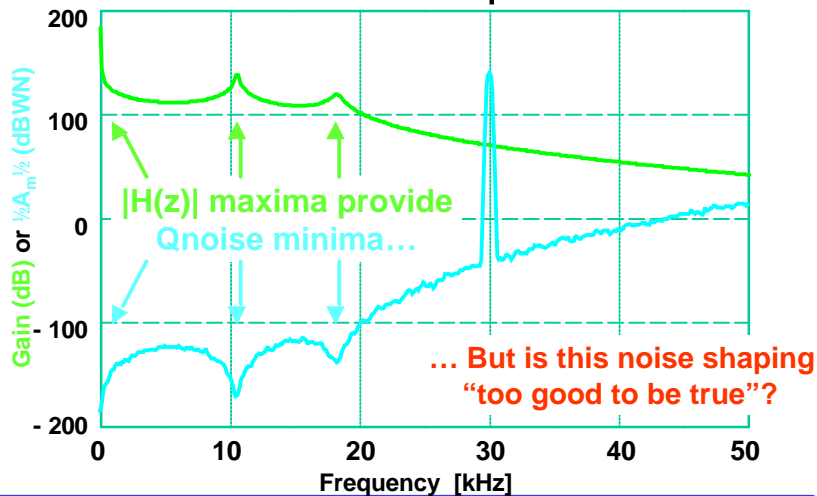


5th-Order Loop Filter

- The fact that $H(z)$ has poles outside the unit circle doesn't mean that the entire $\Sigma\Delta$ modulator is unstable
 - The modulator's stability depends on its closed loop poles
- All loop variables ($\int_1, \int_2, \int_3, \int_4, \int_5$) have the same closed loop poles
 - If one is stable, they all are

Modulator Root-Locus

 The nonlinear modulator system operates at some effective gain G between points A and B:




Modulator Root-Locus

- G may be a function of both v_{IN} and g
- The modulator closed loop poles are the zeroes of the function $1+HG$:


$$\frac{D_{OUT}(z)}{V_{IN}(z)} = \frac{HG/g}{1 + HG}$$

- We'll plot closed loop poles in the z -plane as G varies from 0.1 to 10 in equal log steps ...

Modulator Root-Locus

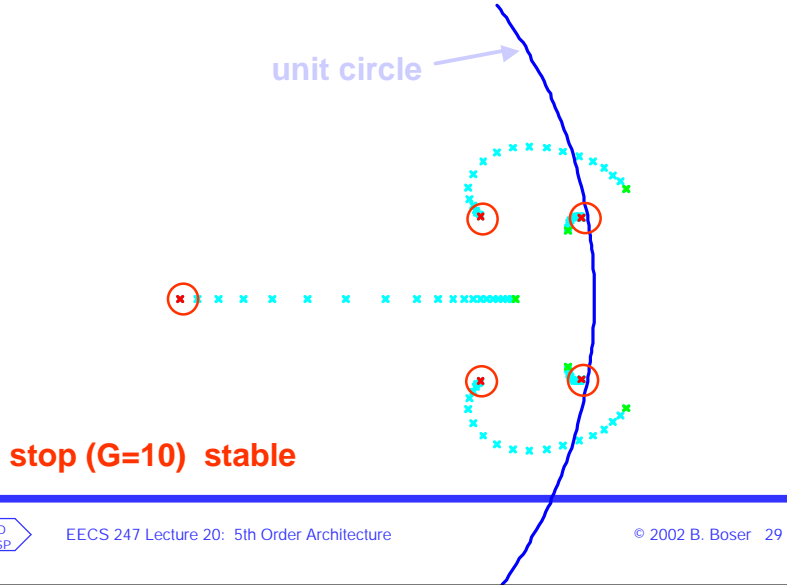


Modulator Root-Locus

 

Effective Gain

- If our linearized model is valid (a big if)
 - For $G > 0.4$, the modulator system is stable
 - For $G < 0.4$, it's unstable
- Presumably, the noise shapes in slides 18 and 23 were produced by a stable system
 - We'll evaluate G for 5kHz and 20kHz sinusoidal inputs varying in amplitude from -30dBV to $+5\text{dBV}$...
 - While we're at it, we'll capture minimum and maximum signal levels throughout the modulator

Sinewave Input Effective Gain

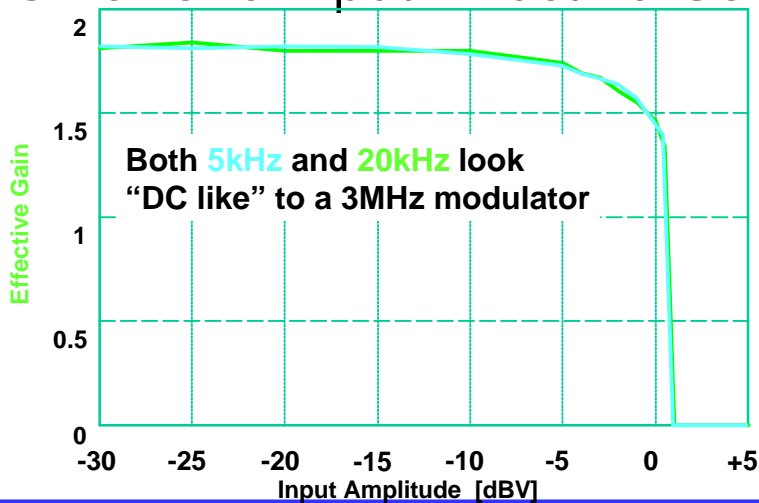


Effective Gain

- As the input amplitude increases, the signal at the quantizer input grows, and G falls
- Just over $1V_{rms}$, G falls to below 0.4, and
 - The system becomes unstable
 - Loop variables grow without bound (opamps in a real analog circuit will just run up to power supply rails)
 - Noise shaping is lost

Effective Gain

- It's highly unlikely that audio sinewaves provide the worst case inputs for stability
 - To evaluate any model, you've got to know what the worst case inputs are
- Let's look at inputs that aren't "dc-like" and aren't sinusoidal (square waves)...

300kHz Input Effective Gain

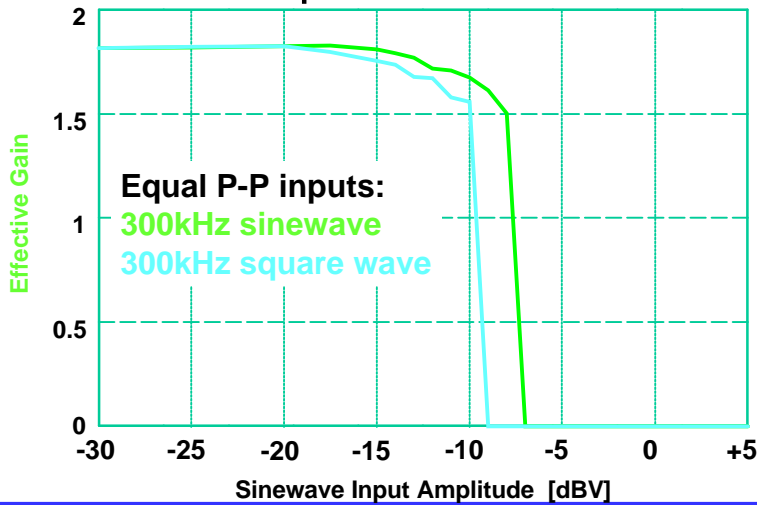

Modulator Stability

- The sensitivity of $\Sigma\Delta$ modulators to high frequency square wave inputs was first discovered on breadboards
 - No one thought to provide such inputs to early modulator simulations
- Worst-case square wave frequencies are roughly equal to the frequency of the highest Q pole in the noise shape
 - A key job of the antialiasing filters used in front of $\Sigma\Delta$ modulators is to reduce out-of-band signals to safe levels


Modulator Stability

- 5000 point simulations such as those in the previous slides don't guarantee stability
 - Sometimes millions of time points are required before an unstable modulator blows up
 - When it explodes, G falls very quickly
- Square wave tolerance is a fast, effective basis for comparing the relative stability of different modulator topologies


Voltage Scaling

- Given that the modulator is stable for 1Vrms inputs, let's move on to look at the state variable voltages under various input conditions
 - Loop state variables and the filter output are labeled green on the next slide
- Peak signal levels and signal standard deviations are easy to obtain in MATLAB
 - We'll examine voltages for a 5kHz sinusoidal input ...


5th-Order Loop Filter

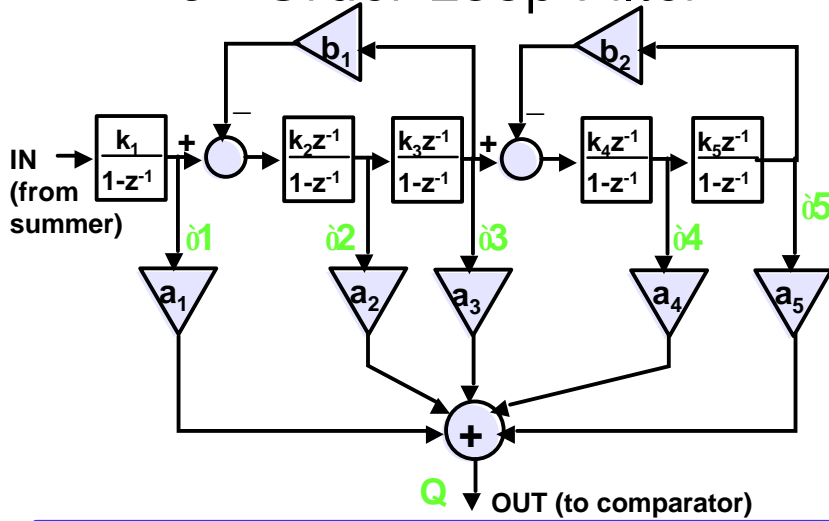

5kHz Input Loop Voltages

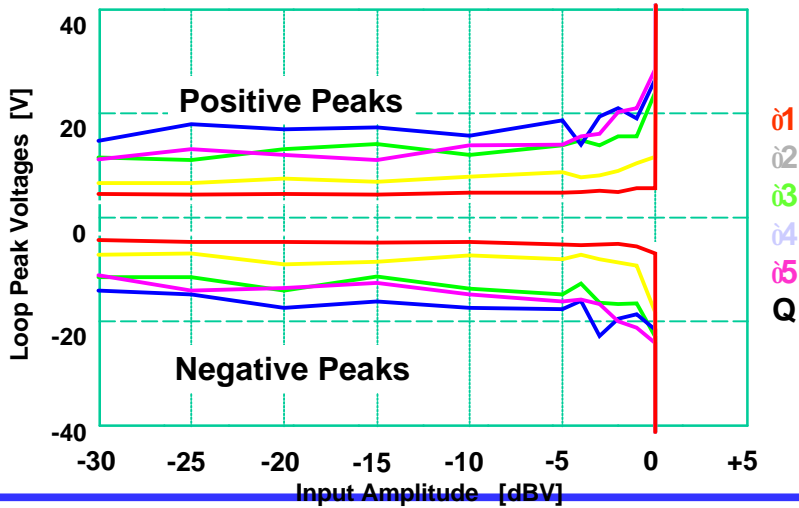


5th-Order Loop Filter

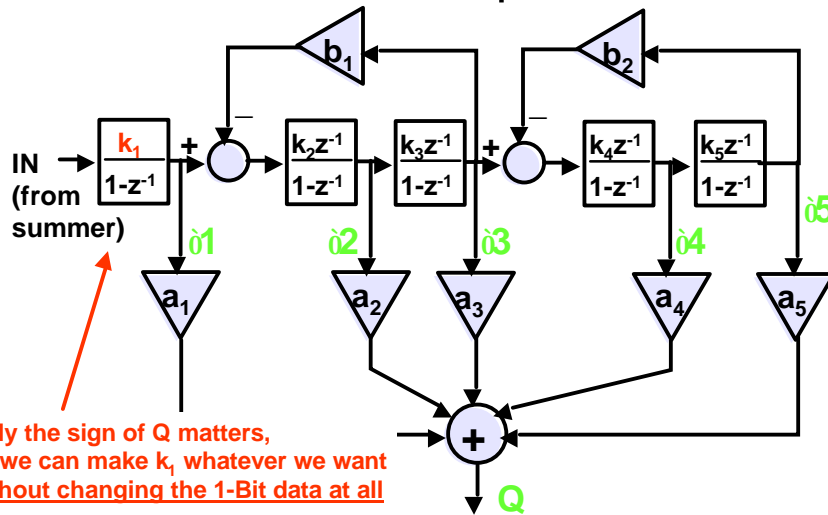


5kHz Input Loop Voltages

- If we scale k_1 by 0.1,
 - All state variables and Q scale by 0.1
 - But since the comparator output is fixed, G increases 10X
- The change in k_1 doesn't change the shape of the root locus, either
 - The effective gain for each root position is increased 10X
 - $G > 4$ is now required for stability

5kHz, $k_1=0.1$ Effective Gain

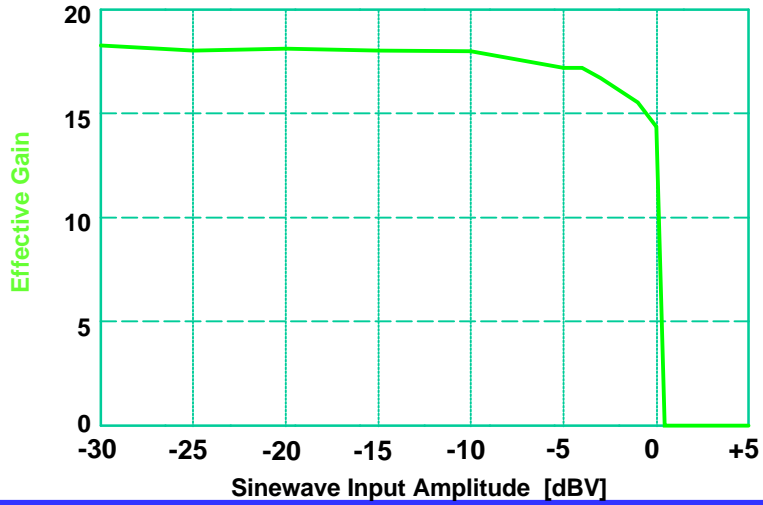


$k_1=0.1$ Loop Voltages

 

Loop Voltage Scaling

- Before we scale k_1 down any lower, we note that \int_3 , \int_4 , and \int_5 have substantially larger swings than \int_1 and \int_2
- Just about any filter topology allows scaling tricks which change internal state variable amplitudes without changing the filter output
 - The next slide shows an example

Scaling Example

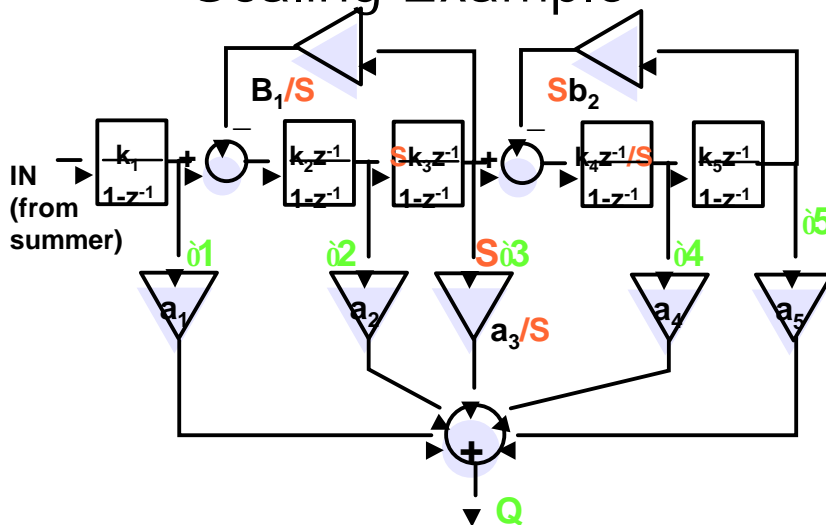


Input Range Scaling

- Slides 40 and 44 indicate inadequate stability margins for 1V_{rms} sinewave inputs
- Scaling the DAC output levels adjusts the modulator input range
 - If V_{IN} and the DAC outputs are scaled up by the same factor g , the 1-Bit data is completely unchanged
 - Of course, increasing the range also increases the quantization noise ... the dynamic range and peak SQNR stay the same!
 - If the DAC output levels are increased and the analog full scale is held constant, the stability margin improves ... at the expense of reduced SQNR

Input Range Scaling

Increasing the DAC levels by g reduces the analog to digital conversion gain:
 
$$\frac{D_{OUT}(z)}{V_{IN}(z)} = \frac{H}{1+gH} \gg \frac{1}{g}$$




increasing v_{IN} , g by the same factor leaves 1-Bit data unchanged

Stage 1 Modulator

- We'll increase g from 2.5 to 3.0 to provide a 2dB increase in stability margin for a 1V_{rms} full scale input
- We'll also implement the loop voltage scaling changes suggested in slide 45
- The result is our first-pass stage 1 modulator, and its performance appears on the following slides ...

Modulator Effective Gain

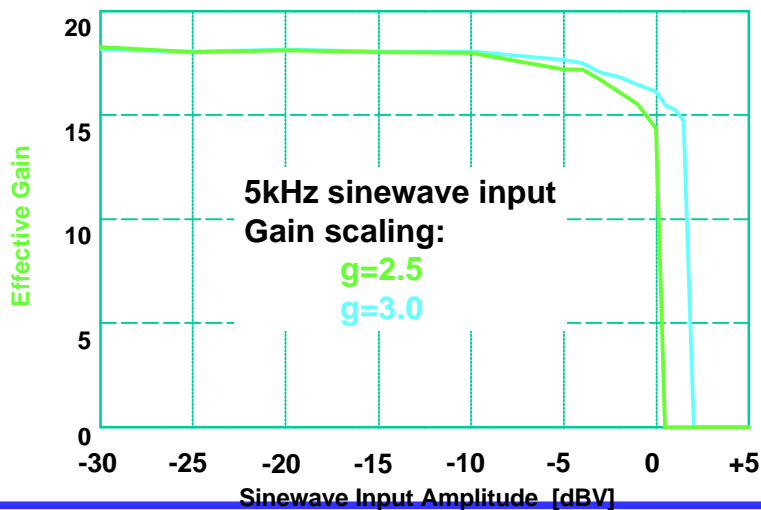

Loop Voltages

