

# Modeling $\Sigma\Delta$ Nonlinearities

- Many component nonlinearities contribute negligible errors
  - Don't waste CPU cycles modeling the voltage coefficient of every capacitor in the loop
  - Unnecessarily complex models reduce the chance to find relevant problems, and, perhaps, solutions
  - As with all nonidealities, model one at a time
- Expect errors from the 2<sup>nd</sup> integrator to be reduced by the gain of the 1<sup>st</sup> integrator
  - Errors further downstream are even less significant



# Capacitor Voltage Coefficient

- Ideal capacitor
- Practical capacitor (1<sup>st</sup> order model)

$$Q = CV$$


with

$$Q(V) = C_o(1 + \mathbf{a}V + \dots)V$$


- Typical voltage coefficients
  - Poly-poly capacitors 10 ppm/V
  - Metal-metal capacitors 1 ... 10 ppm/V




# Integrator 1

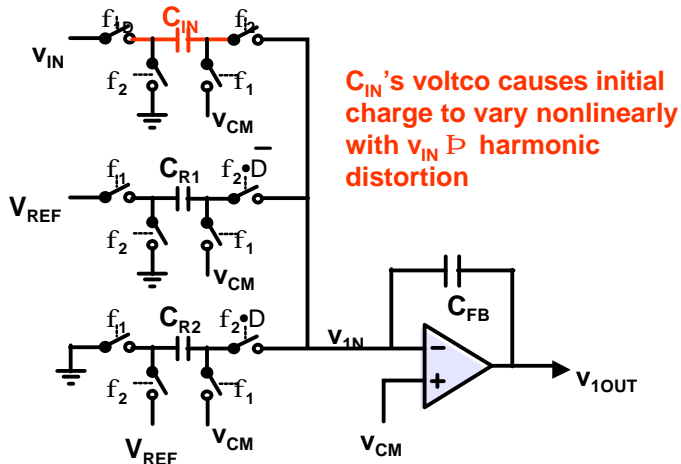

# Integrator 1

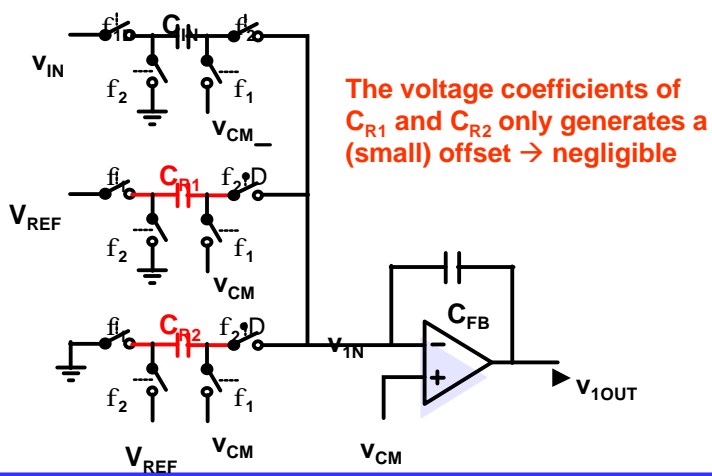

# Integrator 1

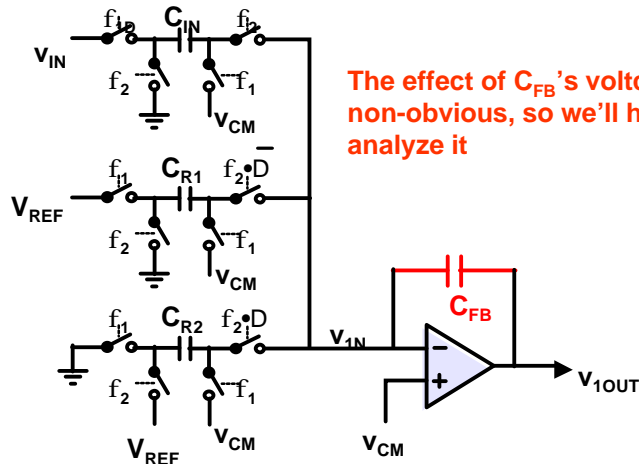


The effect of  $C_{FB}$ 's voltco is non-obvious, so we'll have to analyze it

## $C_{IN}$ Voltage Coefficient

- From charge conservation ( $V_{CM}=0, C_{R1}=C_{R2}=C_R$ ):


$$\begin{aligned}
 V_{1OUT}(k) = & \underbrace{V_{1OUT}(k-1)}_{\text{integration}} \\
 & + \underbrace{\frac{C_{IN}}{C_{FB}} V_{IN}(k-1) + a \frac{C_{IN}}{C_{FB}} V_{IN}^2(k-1)}_{\text{converter input}} \\
 & - \underbrace{D \frac{C_R}{C_{FB}} V_{REF}}_{\text{1-bit feedback}}
 \end{aligned}$$

# $C_{IN}$ Voltage Coefficient

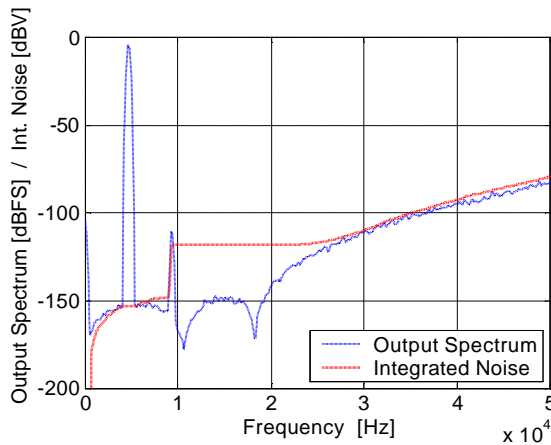


- $V_{in} = V_{FS} = 1V$
- Spectrum scaled for  $V_{FS} \rightarrow 0dB$   
(window lowers peak)
- Noise integral excludes DC, fundamental
- $\alpha = 10 \text{ ppm/V}$
- **2<sup>nd</sup> harmonic at -103dB dominates noise!**
- Let's characterize it ...

# $C_{IN}$ Voltage Coefficient

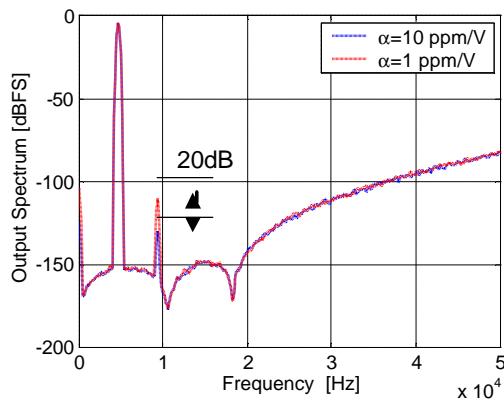

2<sup>nd</sup> harmonic increases  
1dB per 1dB increase of  $\alpha$

## $C_{IN}$ Voltage Coefficient

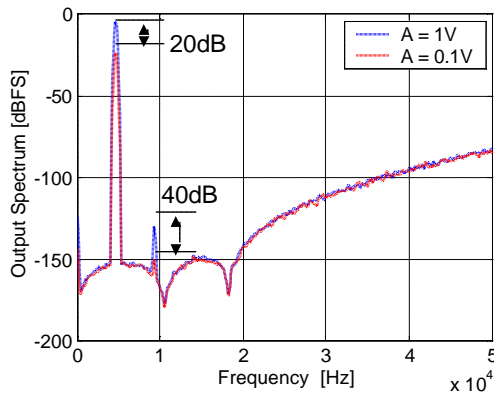

2<sup>nd</sup> harmonic increases  
2dB per 1dB increase of  
the input signal amplitude

## $C_{FB}$ Voltage Coefficient

- Let's look next at the voltage coefficient of the feedback capacitor in the 1<sup>st</sup> integrator
- We "turn off" all other nonidealities –  $C_{IN}$  voltage coefficients, noise, etc.
  - Makes it easier to find the effect of  $C_{FB}$  on the modulator
  - Downside: we miss potential interactions between nonidealities
  - Often they are negligible: nonidealities (like voltage coefficients) produce small errors ... linear superposition applies
  - Of course it's a good idea to run a complete verification at the end
  - And we'll get to diagnose the "real thing" soon enough ... without the insight gained from such idealized simulations it's next to impossible to diagnose a complex chip
- Evaluating the effect of the  $C_{FB}$  voltage coefficient requires solving a quadratic equation, see next slide ...

# $C_{FB}$ Voltage Coefficient



$$V_{OUT1} = \frac{Q_{FB}}{C_{FB1}(V_{OUT1})}$$

$$= \frac{-1 + \sqrt{1 + \frac{4aQ_{FB}}{C_{FB1}}}}{2a}$$


$$Q_{FB}(k) = Q_{FB}(k-1) + C_{IN}V_{IN} + DC_R V_{REF}$$

(same as output from linear integrator)

# $C_{FB}$ Voltage Coefficient

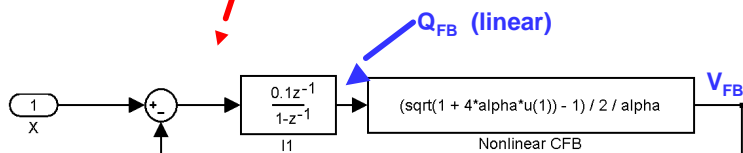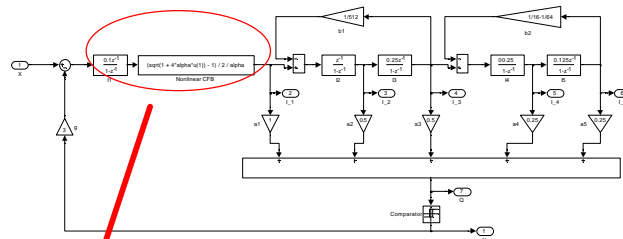


# $C_{FB}$ Voltage Coefficient

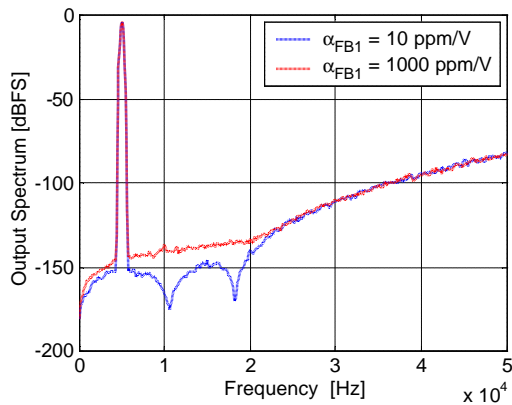


- Effect less pronounced than for  $C_{IN}$
- Noise remains zero at DC
- First order noise for large  $\alpha$
- Nonlinearities operating on shaped noise change the shape of the noise ...
  - No linear model can predict this
- No harmonics ... why?

# 1<sup>st</sup> Integrator Output

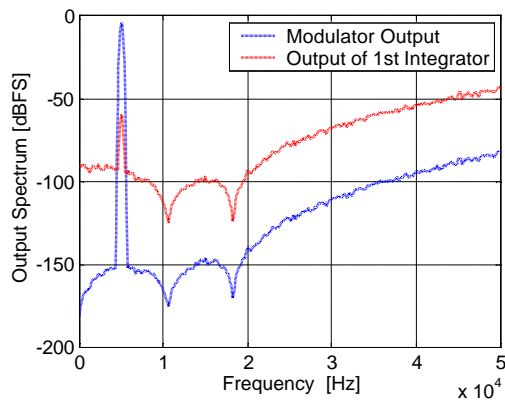


- The input signal appears much attenuated at the output of the 1<sup>st</sup> Integrator (by its gain)
- This signal appears across  $C_{FB}$  ... and since it contains no strong tones it produces no harmonics
- Or does it?

# DC Input

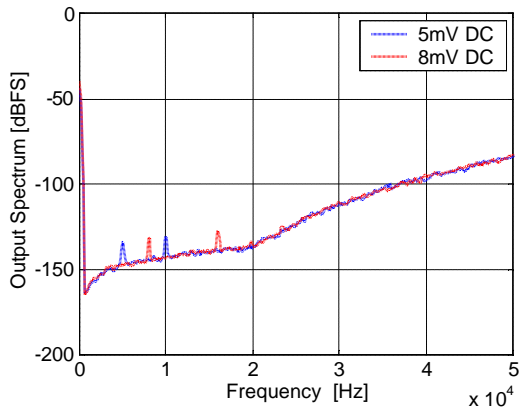

- For  $\alpha = 1000$  ppm/V, tones produced by  $C_{FB}$  are **much larger than native tones**, but move with the same velocity as native tones (1kHz/mV)
- Where are these tones coming from?

# $C_{FB}$ Voltage Coefficient

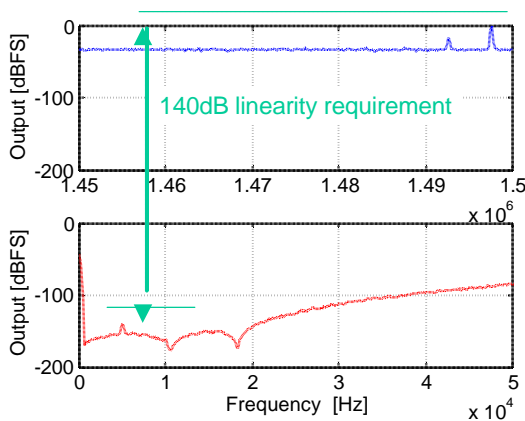

- Tones appear near  $f_s/2$ , as expected
- Apparently these are "folded" to the base-band
- How?

$\alpha = 10$  ppm/V



# Quantization Noise Nonlinearity

- Native tones at a frequency  $f_D$  close to  $f_s/2$  have much higher power than in-band tones

$$f_D = \frac{f_s}{2} - \frac{f_d}{2}$$

- When this tone passes a nonlinearity in the modulator loop filter, it produces distortion

$$\sin^2(2\mathbf{p}f_D t) = \frac{1}{2} - \frac{1}{2} \cos[2\mathbf{p}(2f_D)t]$$

# Quantization Noise Nonlinearity

$$\sin^2(2\mathbf{p}f_D t) = \frac{1}{2} - \frac{1}{2} \cos[2\mathbf{p}(2f_D)t]$$

- In the sampled data system,

$$2f_D = f_s - f_d$$

maps to  $f_d$

- Small nonlinearities applied to aggressively shaped quantization noise can produce big tone problems ...

# Out-of-Band Tones

- “In principle”, the digital filter removes out-of-band tones
  - Except their distortion components, caused by nonlinearities in the modulator loop filter
  - Except components that are mixed down to DC due to noise in the DAC reference
- The  $C_{FB1}$  voltage coefficient adds only a small nonlinearity to the quantization noise path
  - Fortunately this nonlinearity is applied to the integral of the quantization noise and sees only a small signal component
  - Nonlinearities in the amplifier are much more serious
  - Including those in the model is left as an exercise ...
- **Maintaining extremely high levels of linearity in  $H(z)$  is the biggest transistor-level design challenge of  $\Sigma\Delta$  modulators**