

Chapter #9: Finite State Machine Optimization

Contemporary Logic Design

**Randy H. Katz
University of California, Berkeley**

July 1993

Outline

- *Procedures for optimizing implementation of an FSM*

State Reduction

State Assignment

Motivation

Basic FSM Design Procedure:

- (1) Understand the problem
- (2) Obtain a formal description
- (3) Minimize number of states
- (4) Encode the states
- (5) Choose FFs to implement state register
- (6) Implement the FSM




**This
Chapter!**

Next Chapter

Motivation

State Reduction

 

Odd Parity Checker: two alternative state diagrams

- Identical output behavior on all input strings
- FSMs are *equivalent*, but require different implementations
- Design state diagram without concern for # of states, Reduce later

Motivation

State Reduction (continued)

Implement FSM with fewest possible states

- **Least number of flipflops**
- **Boundaries are power of two number of states**
- **Fewest states usually leads to more opportunities for don't cares**
- **Reduce the number of gates needed for implementation**

State Reduction

Goal

Identify and combine states that have equivalent behavior

Equivalent States: for all input combinations, states transition to the same or equivalent states

Odd Parity Checker: S0, S2 are equivalent states

Both output a 0

Both transition to S1 on a 1 and self-loop on a 0

Algorithmic Approach

- Start with state transition table
- Identify states with same output behavior
- If such states transition to the same next state, they are equivalent
- Combine into a single new renamed state
- Repeat until no new states are combined

State Reduction

Row Matching Method

Example FSM Specification:

Single input X, output Z

Taking inputs grouped four at a time, output 1 if last four inputs were the string 1010 or 0110

Example I/O Behavior:

X = 0010 0110 1100 1010 0011 ...
Z = 0000 0001 0000 0001 0000 ...

Upper bound on FSM complexity:

Fifteen states (1 + 2 + 4 + 8)


Thirty transitions (2 + 4 + 8 + 16)

sufficient to recognize any binary string of length four!

State Reduction

Row Matching Method

State Diagram for Example FSM:

 

State Reduction

Row Matching Method

Initial State Transition Table:

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S ₀	S ₁	S ₂	0	0
0	S ₁	S ₃	S ₄	0	0
1	S ₂	S ₅	S ₆	0	0
00	S ₃	S ₇	S ₈	0	0
01	S ₄	S ₉	S ₁₀	0	0
10	S ₅	S ₁₁	S ₁₂	0	0
11	S ₆	S ₁₃	S ₁₄	0	0
000	S ₇	S ₀	S ₀	0	0
001	S ₈	S ₀	S ₀	0	0
010	S ₉	S ₀	S ₀	0	0
011	S ₁₀	S ₀	S ₀	1	0
100	S ₁₁	S ₀	S ₀	0	0
101	S ₁₂	S ₀	S ₀	1	0
110	S ₁₃	S ₀	S ₀	0	0
111	S ₁₄	S ₀	S ₀	0	0

State Reduction

Row Matching Method

Initial State Transition Table:

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S ₀	S ₁	S ₂	0	0
0	S ₁	S ₃	S ₄	0	0
1	S ₂	S ₅	S ₆	0	0
00	S ₃	S ₇	S ₈	0	0
01	S ₄	S ₉	S ₁₀	0	0
10	S ₅	S ₁₁	S ₁₂	0	0
11	S ₆	S ₁₃	S ₁₄	0	0
000	S ₇	S ₀	S ₀	0	0
001	S ₈	S ₀	S ₀	0	0
010	S ₉	S ₀	S ₀	0	0
011	S ₁₀	S ₀	S ₀	1	0
100	S ₁₁	S ₀	S ₀	0	0
101	S ₁₂	S ₀	S ₀	1	0
110	S ₁₃	S ₀	S ₀	0	0
111	S ₁₄	S ₀	S ₀	0	0

State Reduction

Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_7	S_8	0	0
01	S_4	S_9	S'_{10}	0	0
10	S_5	S_{11}	S'_{10}	0	0
11	S_6	S_{13}	S_{14}	0	0
000	S_7	S_0	S_0	0	0
001	S_8	S_0	S_0	0	0
010	S_9	S_0	S_0	0	0
011 or 101	S'_{10}	S_0	S_0	1	0
100	S_{11}	S_0	S_0	0	0
110	S_{13}	S_0	S_0	0	0
111	S_{14}	S_0	S_0	0	0

State Reduction

Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S ₀	S ₁	S ₂	0	0
0	S ₁	S ₃	S ₄	0	0
1	S ₂	S ₅	S ₆	0	0
00	S ₃	S ₇	S ₈	0	0
01	S ₄	S ₉	S' ₁₀	0	0
10	S ₅	S ₁₁	S' ₁₀	0	0
11	S ₆	S ₁₃	S ₁₄	0	0
000	S ₇	S ₀	S ₀	0	0
001	S ₈	S ₀	S ₀	0	0
010	S ₉	S ₀	S ₀	0	0
011 or 101	S' ₁₀	S ₀	S ₀	1	0
100	S ₁₁	S ₀	S ₀	0	0
110	S ₁₃	S ₀	S ₀	0	0
111	S ₁₄	S ₀	S ₀	0	0

State Reduction

Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_7'	S_7'	0	0
01	S_4	S_7'	S_{10}'	0	0
10	S_5	S_7'	S_{10}'	0	0
11	S_6	S_7'	S_7'	0	0
not (011 or 101)	S_7'	S_0	S_0	0	0
011 or 101	S_{10}'	S_0	S_0	1	0

State Reduction

Row Matching Method

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1	S_2	0	0
0	S_1	S_3	S_4	0	0
1	S_2	S_5	S_6	0	0
00	S_3	S_7	S_7	0	0
01	S_4	S_7	S_{10}	0	0
10	S_5	S_7	S_{10}	0	0
11	S_6	S_7	S_7	0	0
not (011 or 101)	S_7	S_0	S_0	0	0
011 or 101	S_{10}	S_0	S_0	1	0


State Reduction

Row Matching Method

**Final Reduced
State Transition Table**

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3'	S4'	0	0
1	S2	S4'	S3'	0	0
00 or 11	S3'	S7'	S7'	0	0
01 or 10	S4'	S7'	S10'	0	0
not (011 or 101)	S7'	S0	S0	0	0
011 or 101	S10'	S0	S0	1	0

**Corresponding State
Diagram**

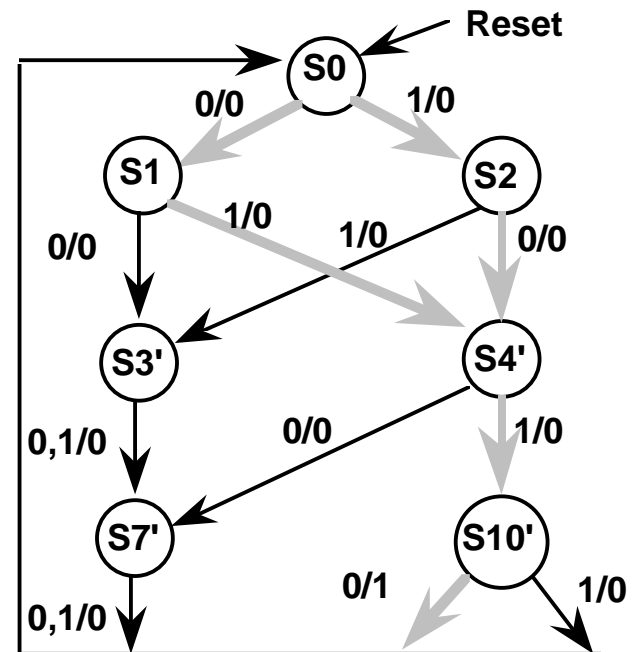

State Reduction

Row Matching Method

- Straightforward to understand and easy to implement
- Problem: does not allow yield the most reduced state table!

Example: 3 State Odd Parity Checker

Present State	Next State		Output
	X=0	X=1	
S ₀	S ₀	S ₁	0
S ₁	S ₁	S ₂	1
S ₂	S ₂	S ₁	0

**No way to combine states S₀ and S₂
based on Next State Criterion!**

State Reduction

Implication Chart Method

New example FSM:

Single input X, Single output Z

Output a 1 whenever the serial sequence 010 or 110 has been observed at the inputs

State transition table:


Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S ₀	S ₁	S ₂	0	0
0	S ₁	S ₃	S ₄	0	0
1	S ₂	S ₅	S ₆	0	0
00	S ₃	S ₀	S ₀	0	0
01	S ₄	S ₀	S ₀	1	0
10	S ₅	S ₀	S ₀	0	0
11	S ₆	S ₀	S ₀	1	0

State Reduction


Implication Chart Method

Enumerate all possible combinations of states taken two at a time

Next States
Under all
Input
Combinations

 

 Naive Data Structure:
X_{ij} will be the same as X_{ji}
Also, can eliminate the diagonal



Implication Chart

State Reduction

Implication Chart

Filling in the Implication Chart

Entry X_{ij} — Row is S_i , Column is S_j

S_i is equivalent to S_j if outputs are the same and next states are equivalent


X_{ij} contains the next states of S_i , S_j which must be equivalent if S_i and S_j are equivalent

If S_i , S_j have different output behavior, then X_{ij} is crossed out

 Example:


S_0 transitions to S_1 on 0, S_2 on 1;
 S_1 transitions to S_3 on 0, S_4 on 1;

So square $X_{\langle 0,1 \rangle}$ contains entries S_1 - S_3 (transition on zero)
 S_2 - S_4 (transition on one)



State Reduction

Implication Chart Method

 

**S2 and S4
have different
I/O behavior**

**This implies that
S1 and S0 cannot
be combined**

Starting Implication Chart

State Reduction

Implication Chart Method


Results of First Marking Pass

Second Pass Adds No New Information

S3 and S5 are equivalent

S4 and S6 are equivalent

This implies that S1 and S2 are too!

 


**Reduced State
Transition Table**

Input Sequence	Present State	Next State		Output	
		X=0	X=1	X=0	X=1
Reset	S_0	S_1'	S_1'	0	0
0 or 1	S_1'	S_3'	S_4'	0	0
00 or 10	S_3'	S_0	S_0	0	0
01 or 11	S_4'	S_0	S_0	1	0

State Reduction

Multiple Input State Diagram Example

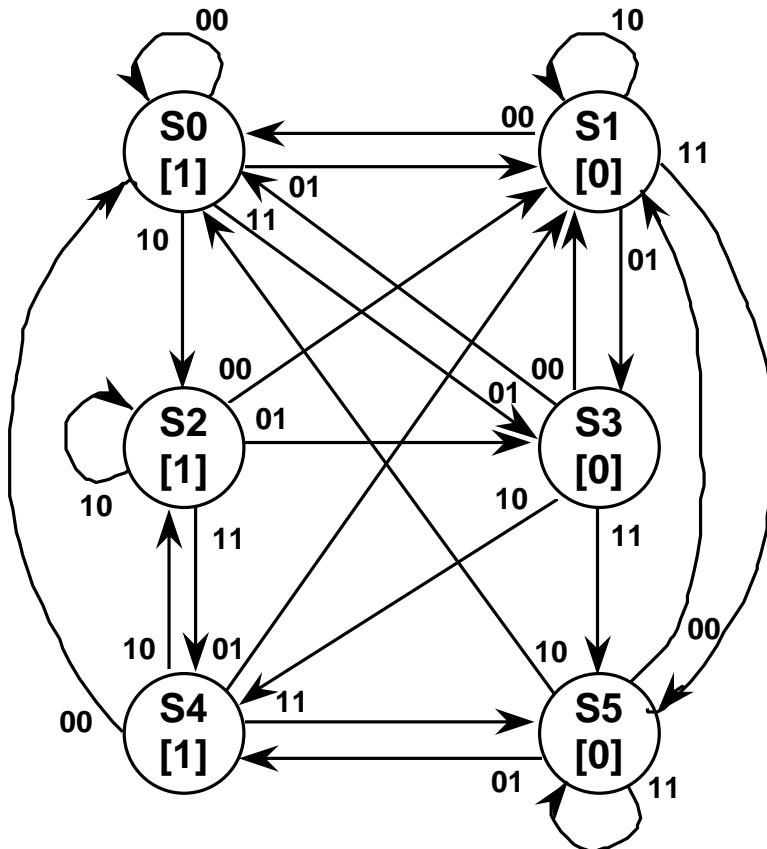


State Diagram

Present State	Next State				Output
	00	01	10	11	
S ₀	S ₀	S ₁	S ₂	S ₃	1
S ₁	S ₀	S ₃	S ₁	S ₅	0
S ₂	S ₁	S ₃	S ₂	S ₄	1
S ₃	S ₁	S ₀	S ₄	S ₅	0
S ₄	S ₀	S ₁	S ₂	S ₅	1
S ₅	S ₁	S ₄	S ₀	S ₅	0

Symbolic State Diagram

State Reduction

Multiple Input Example

 

Implication Chart

Present State	Next State				Output
	00	01	10	11	
S_0'	S_0'	S_1'	S_2'	S_3'	1
S_1'	S_0'	S_3'	S_1'	S_3'	0
S_2'	S_1'	S_3'	S_2'	S_0'	1
S_3'	S_1'	S_0'	S_0'	S_3'	0


Minimized State Table

State Reduction

Implication Chart Method

Does the method solve the problem with the odd parity checker?

Implication Chart

 

**S_0 is equivalent to S_2
since nothing contradicts this assertion!**

State Reduction

Implication Chart Method

The detailed algorithm:

1. Construct implication chart, one square for each combination of states taken two at a time
2. Square labeled S_i, S_j , if outputs differ than square gets "X". Otherwise write down implied state pairs for all input combinations
3. Advance through chart top-to-bottom and left-to-right. If square S_i, S_j contains next state pair S_m, S_n and that pair labels a square already labeled "X", then S_i, S_j is labeled "X".
4. Continue executing Step 3 until no new squares are marked with "X".
5. For each remaining unmarked square S_i, S_j , then S_i and S_j are equivalent.

State Assignment

When FSM implemented with gate logic, number of gates will depend on mapping between symbolic state names and binary encodings

4 states = 4 choices for first state, 3 for second, 2 for third, 1 for last
= 24 different encodings (4!)

Example for State Assignment: Traffic Light Controller

HG HY FG FY				HG HY FG FY				Inputs			Present State		Next State		Outputs				
00	01	10	11	10	00	01	11	C	TL	TS	Q ₁	Q ₀	P ₁	P ₀	ST	H ₁	H ₀	F ₁	F ₀
00	01	10	11	10	00	01	11	0	X	X	HG		HG		0	00		10	
00	01	11	10	10	00	11	01	X	0	X	HG		HG		0	00		10	
00	10	01	11	10	01	00	11	1	1	X	HG		HY		1	00		10	
00	10	11	01	10	01	11	00	X	X	0	HY		HY		0	01		10	
00	11	01	10	10	11	00	01	X	X	1	HY		FG		1	01		10	
00	11	10	01	10	11	01	00	1	0	X	FG		FG		0	10		00	
01	00	10	11	11	00	01	10	0	X	X	FG		FY		1	10		00	
01	00	11	10	11	00	10	01	X	1	X	FG		FY		1	10		00	
01	10	00	11	11	01	00	10	X	X	0	FY		FY		0	10		01	
01	10	11	00	11	01	10	00	X	X	1	FY		HG		1	10		01	
01	11	00	10	11	10	00	01												
01	11	10	00	11	10	01	00												

**24 state assignments
for the traffic light
controller**


Symbolic State Names: HG, HY, FG, FY

State Assignment

Pencil & Paper Heuristic Methods

State Maps: similar in concept to K-maps

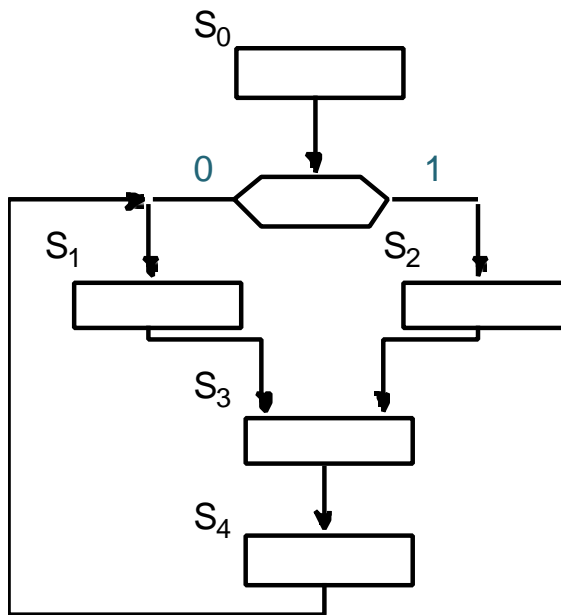If state X transitions to state Y, then assign "close" assignments to X and Y




State Name	Assignment		
	Q ₂	Q ₁	Q ₀
S ₀	0	0	0
S ₁	1	0	1
S ₂	1	1	1
S ₃	0	1	0
S ₄	0	1	1


Assignment

State Name	Assignment		
	Q ₂	Q ₁	Q ₀
S ₀	0	0	0
S ₁	0	0	1
S ₂	0	1	0
S ₃	0	1	1
S ₄	1	1	1

Assignment

 

State Map

 

State Map

State Assignment

Paper and Pencil Methods

Minimum Bit Distance Criterion


<i>Transition</i>	<i>First Assignment Bit Changes</i>	<i>Second Assignment Bit Changes</i>
S0 to S1:	2	1
S0 to S2:	3	1
S1 to S3:	3	1
S2 to S3:	2	1
S3 to S4:	1	1
S4 to S1:	2	2
	13	7

**Traffic light controller: HG = 00, HY = 01, FG = 11, FY = 10
 yields minimum distance encoding but not best assignment!**


State Assignment

Paper & Pencil Methods

 
Alternative heuristics based on input and output behavior as well as transitions:



Highest Priority

 

Medium Priority

 

Lowest Priority

Adjacent assignments to:

states that share a common next state
(group 1's in next state map)


states that share a common ancestor state
(group 1's in next state map)

states that have common output behavior
(group 1's in output map)

State Assignment

Pencil and Paper Methods

Example: 3-bit Sequence Detector

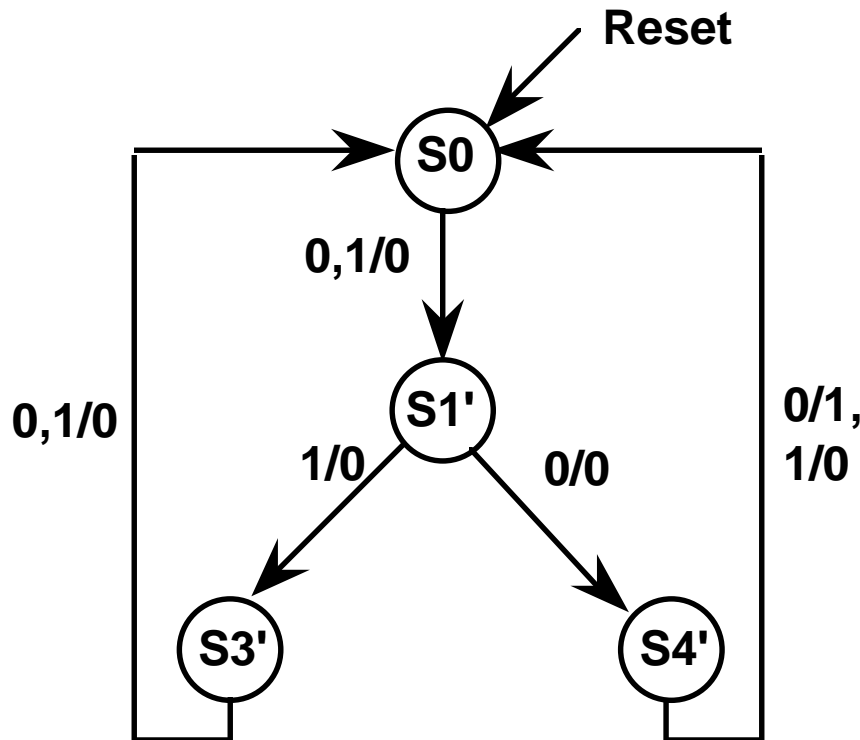

Highest Priority: (S3', S4')

Medium Priority: (S3', S4')

Lowest Priority:

0/0: (S0, S1', S3')

1/0: (S0, S1', S3', S4')

State Assignment

Paper and Pencil Methods

	Q0	
Q1 \	0	1
0	S0	S1'
1	S3'	S4'

Reset State = 00

Highest Priority Adjacency


	Q0	
Q1 \	0	1
0	S0	S3'
1	S1'	S4'

Not much difference in these two assignments

State Assignment

Paper & Pencil Methods

Another Example: 4 bit String Recognizer

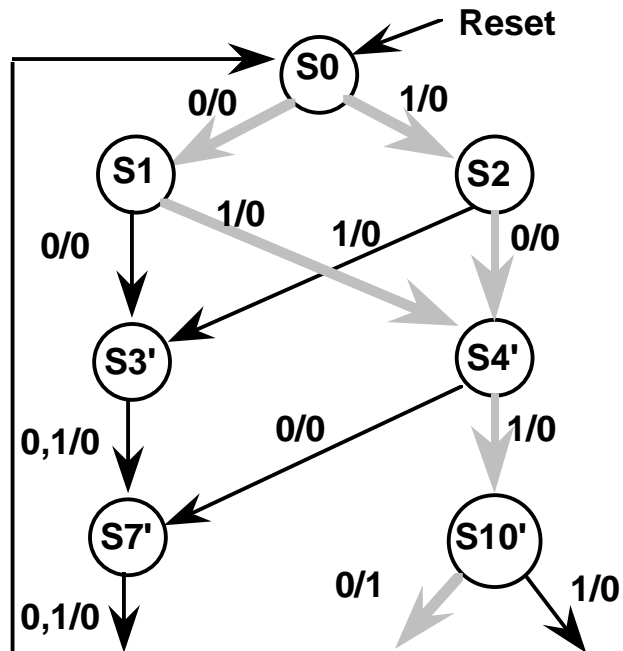

Highest Priority: (S3', S4'), (S7', S10')

Medium Priority:

(S1, S2), 2x(S3', S4'), (S7', S10')

Lowest Priority:

0/0: (S0, S1, S2, S3', S4', S7')

1/0: (S0, S1, S2, S3', S4', S7')

State Assignment

Paper & Pencil Methods

State Map

	Q1 Q0	00	01	11	10
Q2 \	0	S0			
	1				

	Q1 Q0	00	01	11	10
Q2 \	0	S0			
	1				

00 = Reset = S0

(S1, S2), (S3', S4'), (S7', S10')
placed adjacently

	Q1 Q0	00	01	11	10
Q2 \	0	S0		S3'	
	1			S4'	

	Q1 Q0	00	01	11	10
Q2 \	0	S0			
	1	S7'			S10'

	Q1 Q0	00	01	11	10
Q2 \	0	S0		S3'	S7'
	1			S4'	S10'

	Q1 Q0	00	01	11	10
Q2 \	0	S0		S3'	
	1	S7'		S4'	S10'

	Q1 Q0	00	01	11	10
Q2 \	0	S0	S1	S3'	S7'
	1		S2	S4'	S10'

	Q1 Q0	00	01	11	10
Q2 \	0	S0	S1	S3'	
	1	S7'	S2	S4'	S10'




(a)

(b)




State Assignment

Effect of Adjacencies on Next State Map

Current State	Next State	
	X = 0	X = 1
(S ₀) 000	001	101
(S ₁) 001	011	111
(S ₂) 101	111	011
(S ₃) 011	010	010
(S ₄) 111	010	110
(S ₇) 010	000	000
(S ₁₀) 110	000	000

   

Current State	Next State	
	X = 0	X = 1
(S ₀) 000	001	010
(S ₁) 001	011	100
(S ₂) 010	100	011
(S ₃) 011	101	101
(S ₄) 100	101	110
(S ₇) 101	000	000
(S ₁₀) 110	000	000

  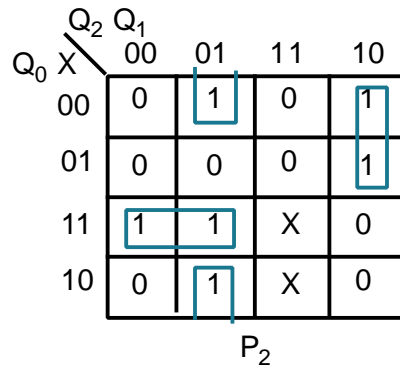

First encoding exhibits a better clustering of 1's in the next state map