

EECS150 - Digital Design

Lecture 3 - Verilog Introduction

Jan 24, 2012


John Wawrzynek

Outline

- Background and History of Hardware Description
- Brief Introduction to Verilog Basics
- Lots of examples
 - structural, data-flow, behavioral
- Verilog in EECS150

Design Entry

- Schematic entry/editing used to be the standard method in industry and universities.
- Used in EECS150 until 2002
- ☺ Schematics are intuitive. They match our use of gate-level or block diagrams.
- ☺ Somewhat physical. They imply a physical implementation.
- ☹ Require a special tool (editor).
- ☹ Unless hierarchy is carefully designed, schematics can be confusing and difficult to follow on large designs.

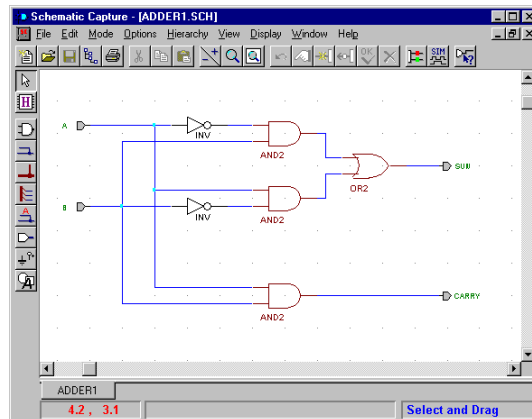

- Hardware Description Languages (HDLs) are the new standard
 - except for PC board design, where schematics are still used.

Spring 2012

EECS150 - Lec03-Verilog

Page 3

Hardware Description Languages

- **Basic Idea:**
 - Language constructs describe circuits with two basic forms:
 - **Structural descriptions:** connections of components. Nearly one-to-one correspondence to with schematic diagram.
 - **Behavioral descriptions:** use high-level constructs (similar to conventional programming) to describe the circuit function.
- Originally invented for simulation.
 - Now "logic synthesis" tools exist to automatically convert from HDL source to circuits.
 - High-level constructs greatly improves designer productivity.
 - However, this may lead you to falsely believe that hardware design can be reduced to writing programs!*

"Structural" example:

```
Decoder(output x0,x1,x2,x3;
         inputs a,b)
{
  wire abar, bbar;
  inv(bbar, b);
  inv(abar, a);
  and(x0, abar, bbar);
  and(x1, abar, b );
  and(x2, a, bbar);
  and(x3, a, b );
}
```

"Behavioral" example:

```
Decoder(output x0,x1,x2,x3;
         inputs a,b)
{
  case [a b]
    00: [x0 x1 x2 x3] = 0x1;
    01: [x0 x1 x2 x3] = 0x2;
    10: [x0 x1 x2 x3] = 0x4;
    11: [x0 x1 x2 x3] = 0x8;
  endcase;
}
```


Warning: this is a fake HDL!

Lec03-Verilog

Page 4

*Describing hardware with a language is similar, however, to writing a parallel program.

Sample Design Methodology

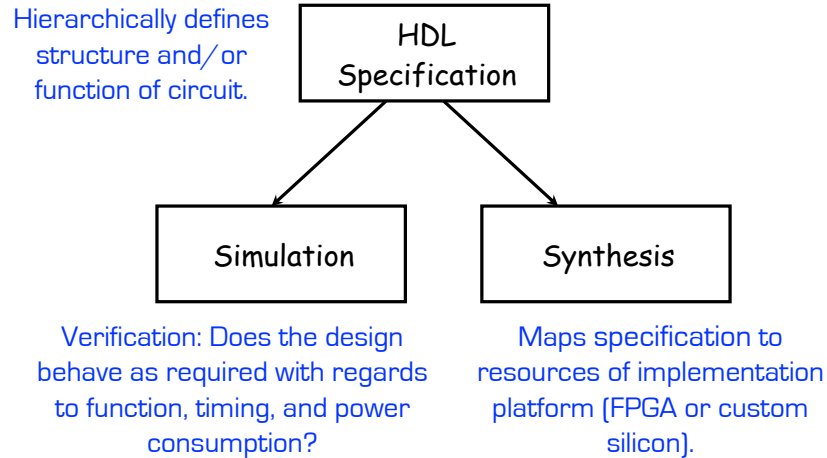

Note: This is not the entire story. Other tools are useful for analyzing HDL specifications. More on this later.

Verilog


- A brief history:
 - Originated at Automated Integrated Design Systems (renamed Gateway) in 1985. Acquired by Cadence in 1989.
 - Invented as simulation language. Synthesis was an afterthought. Many of the basic techniques for synthesis were developed at Berkeley in the 80's and applied commercially in the 90's.
 - Around the same time as the origin of Verilog, the US Department of Defense developed VHDL (A double acronym! VSIC (Very High-Speed Integrated Circuit) HDL). Because it was in the public domain it began to grow in popularity.
 - Afraid of losing market share, Cadence opened Verilog to the public in 1990.
 - An IEEE working group was established in 1993, and ratified IEEE Standard 1394 (Verilog) in 1995. We use IEEE Std 1364-2001.
 - Verilog is the language of choice of Silicon Valley companies, initially because of high-quality tool support and its similarity to C-language syntax.
 - VHDL is still popular within the government, in Europe and Japan, and some Universities.
 - Most major CAD frameworks now support both.
 - Latest Verilog version is “system Verilog” .
 - Latest HDL: C++ based. OSCI (Open System C Initiative).

Verilog Introduction

- A **module** definition describes a component in a circuit
- Two ways to describe module contents:
 - Structural Verilog
 - List of sub-components and how they are connected
 - Just like schematics, but using text
 - tedious to write, hard to decode
 - You get precise control over circuit details
 - May be necessary to map to special resources of the FPGA
 - Behavioral Verilog
 - Describe what a component does, not how it does it
 - Synthesized into a circuit that has this behavior
 - Result is only as good as the tools
- Build up a hierarchy of modules. Top-level module is your entire design (or the environment to test your design).

Verilog Modules and Instantiation

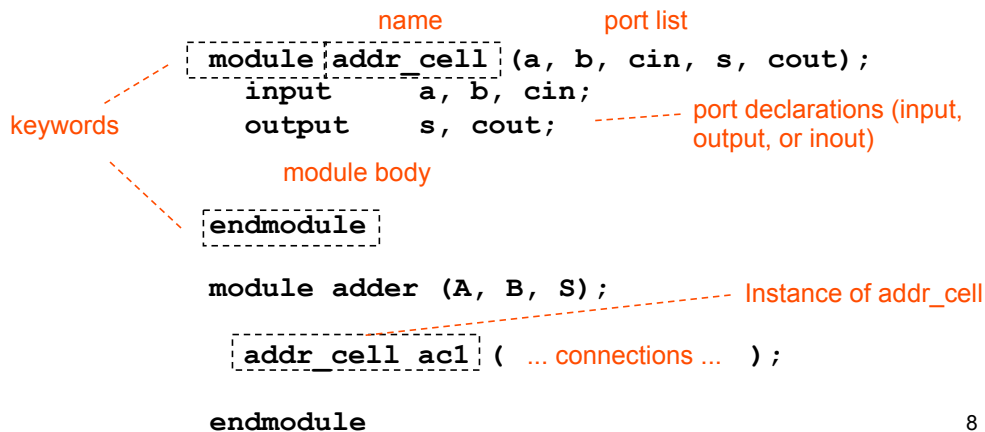- Modules define circuit components.
- Instantiation defines hierarchy of the design.



Note: A module is not a function in the C sense. There is no call and return mechanism. Think of it more like a hierarchical data structure.

Structural Model - XOR example

```

module xor_gate ( out, a, b );
  input  a, b;
  output out;
  wire  aBar, bBar, t1, t2;
  not invA (aBar, a);
  not invB (bBar, b);
  and and1 (t1, a, bBar);
  and and2 (t2, b, aBar);
  or  or1 (out, t1, t2);
endmodule

```

module name: xor_gate
port list: (out, a, b)
port declarations: input a, b; output out;
internal signal declarations: wire aBar, bBar, t1, t2;
Built-in gates: not, and, or
instances: invA, invB, and1, and2, or1
Interconnections (note output is first): or1 (out, t1, t2);


- Notes:

- The instantiated gates are not "executed". They are active always.
- xor_gate already exists as a built-in (so really no need to define it).
- Undeclared variables assumed to be wires. Don't let this happen to you!

Structural Example: 2-to1 mux



a) 2-input mux symbol

 

b) 2-input mux gate-level circuit diagram


```

/* 2-input multiplexor in gates */
module mux2 (in0, in1, select, out);
  input in0,in1,select;
  output out;
  wire s0,w0,w1;
  not (s0, select);
  and (w0, s0, in0),
      (w1, select, in1);
  or  (out, w0, w1);
endmodule // mux2

```

C++ style comments: /* 2-input multiplexor in gates */
Built-ins don't need Instance names: not (s0, select);
Multiple instances can share the same "master" name.: mux2
Built-ins gates can have > 2 inputs. Ex: and (w0, a, b, c, d);

Instantiation, Signal Array, Named ports

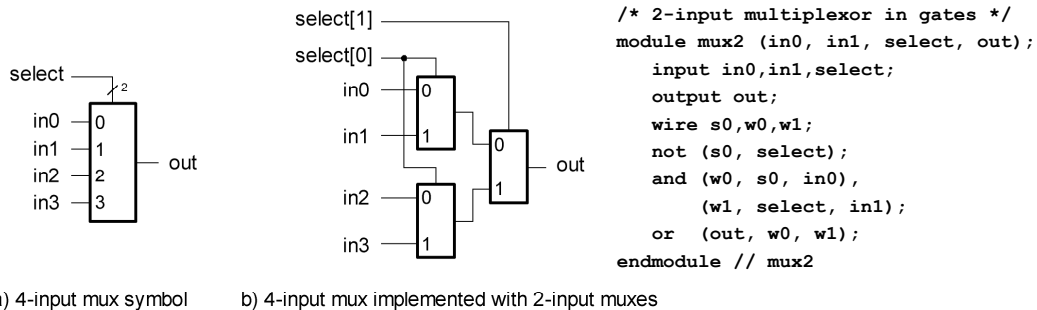

```

module mux4 (in0, in1, in2, in3, select, out);
  input in0,in1,in2,in3;
  input [1:0] select;
  output out;
  wire w0,w1;
  mux2
    m0 (.select(select[0]), .in0(in0), .in1(in1), .out(w0)),
    m1 (.select(select[0]), .in0(in2), .in1(in3), .out(w1)),
    m3 (.select(select[1]), .in0(w0), .in1(w1), .out(out));
endmodule // mux4

```

Signal array. Declares select[1], select[0]

Named ports. Highly recommended.

Simple Behavioral Model

```

module foo (out, in1, in2);
  input      in1, in2;
  output     out;
  assign out = in1 & in2;
endmodule

```

“continuous assignment”

Connects out to be the “and” of in1 and in2.

Shorthand for explicit instantiation of “and” gate (in this case).

The assignment continuously happens, therefore any change on the rhs is reflected in out immediately (except for the small delay associated with the implementation of the &).

Not like an assignment in C that takes place when the program counter gets to that place in the program.

Example - Ripple Adder


```

module FullAdder(a, b, ci, r, co);
  input a, b, ci;
  output r, co;

  assign r = a ^ b ^ ci;
  assign co = a&ci + a&b + b&cin;

endmodule

```

 


```

module Adder(A, B, R);
  input [3:0] A;
  input [3:0] B;
  output [4:0] R;

  wire c1, c2, c3;
  FullAdder
    add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),
    add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),
    add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),
    add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );
endmodule

```

 

Continuous Assignment Examples

```

wire [3:0] X,Y,R;
wire [7:0] P;
wire r, a, cout, cin;

```

- `assign R = X | (Y & ~Z);` ← use of bit-wise Boolean operators
- `assign r = &X;` ← example reduction operator
- `assign R = (a == 1'b0) ? X : Y;` ← conditional operator
- `assign P = 8'hff;` ← example constants
- `assign P = X * Y;` ← arithmetic operators (use with care!)
- `assign P[7:0] = {4{X[3]}, X[3:0]};` ← (ex: sign-extension)
- `assign {cout, R} = X + Y + cin;` ← bit field concatenation
- `assign Y = A << 2;` ← bit shift operator
- `assign Y = {A[1], A[0], 1'b0, 1'b0};` ← equivalent bit shift

Verilog Operators

Verilog Operator	Name	Functional Group			
()	bit-select or part-select		>	greater than	Relational
			>=	greater than or equal to	Relational
			<	less than	Relational
			<=	less than or equal to	Relational
	parenthesis		==	logical equality	Equality
!	logical negation	Logical	!=	logical inequality	Equality
~	negation	Bit-wise	===	case equality	Equality
&	reduction AND	Reduction	!==	case inequality	Equality
	reduction OR	Reduction	&	bit-wise AND	Bit-wise
~&	reduction NAND	Reduction	^	bit-wise XOR	Bit-wise
~	reduction NOR	Reduction	^~ or ~^	bit-wise XNOR	Bit-wise
^	reduction XOR	Reduction		bit-wise OR	Bit-wise
~^ or ^~	reduction XNOR	Reduction	&&	logical AND	Logical
+	unary (sign) plus	Arithmetic		logical OR	Logical
-	unary (sign) minus	Arithmetic	?:	conditional	Conditional
{}	concatenation	Concatenation			
{{}}	replication	Replication			
*	multiply	Arithmetic			
/	divide	Arithmetic			
%	modulus	Arithmetic			
+	binary plus	Arithmetic			
-	binary minus	Arithmetic			
<<	shift left	Shift			
>>	shift right	Shift			

Verilog Numbers

Constants:

- 14** ordinary decimal number
- 14** 2's complement representation
- 12'b0000_0100_0110** binary number ("_" is ignored)
- 12'h046** hexadecimal number with 12 bits

Signal Values:

By default, Values are unsigned

e.g., **C[4:0] = A[3:0] + B[3:0];**

if A = 0110 (6) and B = 1010(-6)

C = 10000 not 00000

i.e., B is zero-padded, not sign-extended

wire signed [31:0] x;

Declares a signed (2's complement) signal array.

Non-continuous Assignments

A bit strange from a hardware specification point of view.
Shows off Verilog roots as a simulation language.

"always" block example:

```
module and_or_gate (out, in1, in2, in3);
  input  in1, in2, in3;
  output out;
  reg    out;
  always @(in1 or in2 or in3) begin
    out = (in1 & in2) | in3;
  end
endmodule
```

reg type declaration. Not really a register in this case. Just a Verilog rule.

always keyword

@{in1 or in2 or in3} "sensitivity" list, triggers the action in the body.

begin brackets multiple statements (not necessary in this example).

Isn't this just: `assign out = (in1 & in2) | in3;`?

Why bother?

Always Blocks

Always blocks give us some constructs that are impossible or awkward in continuous assignments.

case statement example:

```
module mux4 (in0, in1, in2, in3, select, out);
  input in0, in1, in2, in3;
  input [1:0] select;
  output out;
  reg out;

  always @ (in0 in1 in2 in3 select)
    case (select)
      2'b00: out=in0;
      2'b01: out=in1;
      2'b10: out=in2;
      2'b11: out=in3;
    endcase
endmodule // mux4
```

case keyword

The statement(s) corresponding to whichever constant matches "select" get applied.

Couldn't we just do this with nested "if"s?

Well yes and no!

Always Blocks

Nested if-else example:

```
module mux4 (in0, in1, in2, in3, select, out);
  input in0,in1,in2,in3;
  input [1:0] select;
  output      out;
  reg        out;


  always @ (in0 in1 in2 in3 select)
    if (select == 2'b00) out=in0;
    else if (select == 2'b01) out=in1;
    else if (select == 2'b10) out=in2;
    else out=in3;
endmodule // mux4
```

Nested if structure leads to "priority logic" structure, with different delays for different inputs (in3 to out delay > than in0 to out delay). Case version treats all inputs the same.

Review - Ripple Adder Example


```
module FullAdder(a, b, ci, r, co);
  input a, b, ci;
  output r, co;

   assign r = a ^ b ^ ci;
  assign co = a&ci + a&b + b&cin;
endmodule
```



```
module Adder(A, B, R);
  input [3:0] A;
  input [3:0] B;
  output [4:0] R;

   wire c1, c2, c3;
  FullAdder
    add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),
    add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),
    add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),
    add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );
endmodule
```



Example - Ripple Adder Generator

Parameters give us a way to generalize our designs. A module becomes a "generator" for different variations. Enables design/module reuse. Can simplify testing.

```
module Adder(A, B, R);
  parameter N = 4;
  input [N-1:0] A;
  input [N-1:0] B;
  output [N:0] R;
  wire [N:0] C;

  genvar i;
  generate
    for (i=0; i<N; i=i+1) begin:bit
      FullAdder add(.a(A[i], .b(B[i]), .ci(C[i]), .co(C[i+1]), .r(R[i]));
    end
  endgenerate

  assign C[0] = 1'b0;
  assign R[N] = C[N];
endmodule
```

Declare a parameter with default value.
Note: this is not a port. Acts like a "synthesis-time" constant.
Replace all occurrences of "4" with "N".
variable exists only in the specification - not in the final circuit.
Keyword that denotes synthesis-time operations
For-loop creates instances (with unique names)

```
Adder adder4 ( ... );
Adder #(.N(64))
  adder64 ( ... );
```

Overwrite parameter N at instantiation.

More on Generate Loop

Permits variable declarations, modules, user defined primitives, gate primitives, continuous assignments, initial blocks and always blocks to be instantiated multiple times using a for-loop.

```
// Gray-code to binary-code converter
module gray2bin1 (bin, gray);
  parameter SIZE = 8;
  output [SIZE-1:0] bin;
  input [SIZE-1:0] gray;

  genvar i;
  generate for (i=0; i<SIZE; i=i+1) begin:bit
    assign bin[i] = ^gray[SIZE-1:i];
  end endgenerate
endmodule
```

variable exists only in the specification - not in the final circuit.
Keywords that denotes synthesis-time operations
For-loop creates instances of assignments
Loop must have constant bounds

generate if-else-if based on an expression that is deterministic at the time the design is synthesized.

generate case : selecting case expression must be deterministic at the time the design is synthesized.

Verilog in EECS150

- We will primarily use **behavioral modeling** along with **instantiation** to 1) build hierarchy and, 2) map to FPGA resources not supported by synthesis.
- Favor continuous assign and avoid always blocks unless:
 - no other alternative: ex: state elements, case
 - helps readability and clarity of code: ex: large nested if else
- Use named ports.
- Verilog is a big language. This is only an introduction.
 - Our text book is a good source. Read and use chapter 4.
 - Be careful of what you read on the web. Many bad examples out there.
 - We will be introducing more useful constructs throughout the semester. Stay tuned!

Final thoughts on Verilog Examples

Verilog looks like C, but it describes hardware

Multiple physical elements with parallel activities and temporal relationships.

A large part of digital design is knowing how to write Verilog that gets you the desired circuit. First understand the circuit you want then figure out how to code it in Verilog. If you do one of these activities without the other, you will struggle. These two activities will merge at some point for you.

Be suspicious of the synthesis tools! Check the output of the tools to make sure you get what you want.