

CS 61C: Great Ideas in Computer Architecture (Machine Structures) *Muxes, Adders, and ALUs*

Instructors:

Randy H. Katz

David A. Patterson

<http://inst.eecs.Berkeley.edu/~cs61c/fa10>

10/25/10

Fall 2010 -- Lecture #24

1

Agenda

- Multiplexer
- Administrivia
- Technology Break
- ALU Design

10/25/10

Fall 2010 -- Lecture #24

2

Agenda


- Multiplexer
- Administrivia
- Technology Break
- ALU Design

10/25/10

Fall 2010 -- Lecture #24

3

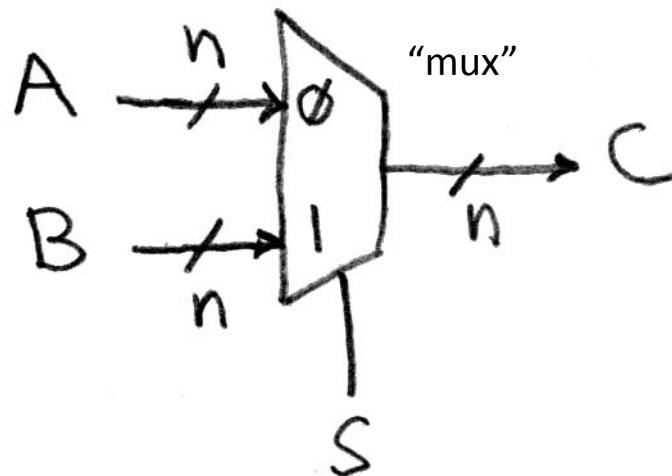Data Multiplexer (e.g., 2-to-1 x n-bit-wide)




10/25/10

Fall 2010 -- Lecture #24

4

N Instances of 1-bit-Wide Mux

 

How many rows in TT?

$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$




10/25/10

Fall 2010 -- Lecture #24

5

How Do We Build a 1-bit-Wide Mux?

 


10/25/10

Fall 2010 -- Lecture #24

6

4-to-1 Multiplexer

 


$$e = \bar{s}_1\bar{s}_0a + \bar{s}_1s_0b + s_1\bar{s}_0c + s_1s_0d$$

10/25/10

Fall 2010 -- Lecture #24

7

Alternative Hierarchical Approach

 


10/25/10

Fall 2010 -- Lecture #24

8

Arithmetic and Logic Unit

 - Most processors contain a special logic block called “Arithmetic and Logic Unit” (ALU)
- We’ll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR




when $S=00$, $R=A+B$
 when $S=01$, $R=A-B$
 when $S=10$, $R=A \text{ AND } B$
 when $S=11$, $R=A \text{ OR } B$

10/25/10

Fall 2010 -- Lecture #24

9

Simple ALU

 

10/25/10

Fall 2010 -- Lecture #24

10

Agenda

- Mutiplexers
- **Administrivia**
- Technology Break
- ALU

Agenda

- Mux + Adder Design
- Administrivia
- **Technology Break**
- ALU Design

Agenda

- Multiplexer
- Administrivia
- Technology Break
- ALU Design

10/25/10

Fall 2010 -- Lecture #24

13

Adder/Subtractor: One-bit adder Least Significant Bit

+	a_3	a_2	a_1	a_0	a_0	b_0	s_0	c_1
	b_3	b_2	b_1	b_0	0	1	1	0
	s_3	s_2	s_1	s_0	1	0	1	0
					1	1	0	1

$$s_0 = a_0$$

$$c_1 = a_0$$

10/25/10

Fall 2010 -- Lecture #24

14

Adder/Subtractor: One-bit adder

(1/2) ...

a_3	a_2	a_1	a_0	b_3	b_2	b_1	b_0	s_3	s_2	s_1	s_0
$+$											



a_i	b_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i =$$

$$c_{i+1} =$$

Adder/Subtractor: One-bit Adder

(2/2) ...

  


$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

N x 1-bit Adders \Rightarrow 1 N-bit Adder

Connect Carry Out $i-1$ to Carry in i :

 

10/25/10


Fall 2010 -- Lecture #24

17

Overflow Conditions

Add two positive numbers to get a negative number

 or two negative numbers to get a positive number



10/25/10

Fall 2010 -- Lecture #24

18

Overflow Conditions

$$\begin{array}{r} 5 \quad 0111 \\ 3 \quad 0101 \\ \hline -8 \quad 1000 \end{array}$$

Overflow

$$\begin{array}{r} 5 \quad 0000 \\ 2 \quad 0101 \\ \hline 7 \quad 0111 \end{array}$$

No overflow

$$\begin{array}{r} -7 \quad 1000 \\ -2 \quad 1001 \\ \hline 7 \quad 10111 \end{array}$$


Overflow

$$\begin{array}{r} -3 \quad 1111 \\ -5 \quad 1101 \\ \hline -8 \quad 11000 \end{array}$$


No overflow

Overflow when carry in to sign does not equal carry out: $C_n \text{ xor } C_{n-1}$

Twos Complement Adder/ Subtractor

 

Design Hierarchy

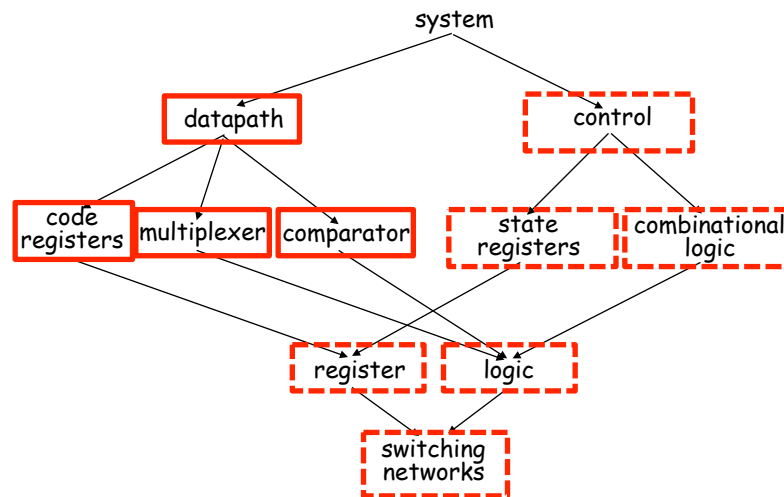

10/25/10

Fall 2010 -- Lecture #24

21

Summary

- Use muxes to select among input
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, indep of S
- Can implement muxes hierarchically
- ALU can be implemented using a mux
 - Coupled with basic block elements
- N-bit adder-subtractor done using N 1-bit adders with XOR gates on input
 - XOR serves as conditional inverter

10/25/10

Fall 2010 -- Lecture #24

22