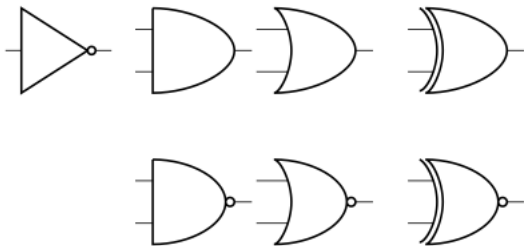


# CS61c Summer 2014 Discussion 10 – Synchronous Digital Systems and Boolean Algebra

July 23, 2014

## 1 Logic Gates

1. Label the following logic gates:



not, and, or, xor, nand, nor, xnor


2. Convert the following to boolean expressions:

(a) NAND  $\bar{A}\bar{B} + \bar{A}B + A\bar{B}$

(b) XOR  $\bar{A}B + A\bar{B}$

(c) XNOR  $\bar{A}\bar{B} + AB$

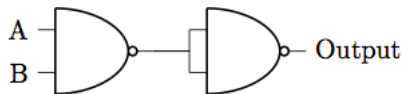3. Create an AND gate using only NAND gates.




4. How many different two-input logic gates can there be? How many n-input logic gates?


A truth table with  $n$  inputs has  $2^n$  rows. Each logic gate has a 0 or a 1 at each of these rows. Imagining a function as a  $2^n$ -bit number, we count  $2^{2^n}$  total functions, 04 16 in the case of  $n = 2$

## 2 State

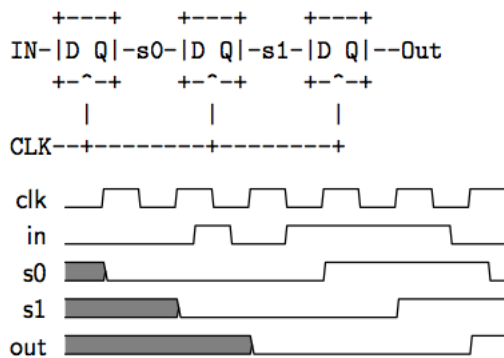1. Fill out the timing diagram for the circuit below:



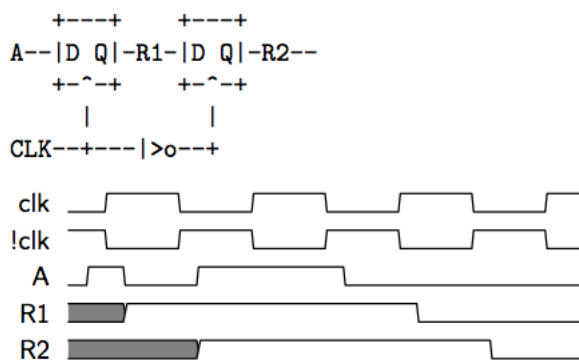2. Fill out the timing diagram for the circuit below:



## 3 Boolean Logic

- $A + \bar{A} = 1$
- $0B = 0$
- $(A + B)(A + C) = A + BC$
- $1 + A = 1$
- $B\bar{B} = 0$
- $\overline{AB} = \bar{A} + \bar{B}$
- $A + AB = A$
- $A + \bar{A}B = A + B$
- $\overline{A+B} = \bar{A}\bar{B}$

1. Minimize the following boolean expressions:

(a) Standard:  $(A + B)(A + \bar{B})C$

$$(AA + A\bar{B} + AB + B\bar{B})C = (A + A(\bar{B} + B))C = AC$$

(b) Grouping & Extra Terms:  $\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC + A\bar{B}C$

$$\begin{aligned} \bar{A}\bar{C}(\bar{B} + B) + A\bar{C}(\bar{B} + B) + AC(\bar{B} + B) &= \bar{A}\bar{C} + A\bar{C} + AC \\ &= \bar{A}\bar{C} + A\bar{C} + A\bar{C} + AC \\ &= (\bar{A} + A)C + A(\bar{C} + C) \\ &= A + \bar{C} \end{aligned}$$

(c) DeMorgan's:  $\overline{A(\overline{B\overline{C}} + BC)}$

$$\begin{aligned}\overline{A(\overline{B\overline{C}} + BC)} &= \overline{A} + \overline{\overline{B\overline{C}} + BC} \\ &= \overline{A} + \overline{B\overline{C}}\overline{BC} \\ &= \overline{A} + (B + C)(\overline{B} + \overline{C}) \\ &= \overline{A} + B\overline{C} + \overline{B}C\end{aligned}$$