

Lecture #11

ANNOUNCEMENTS

- Homework Assignment #4 will be posted today
- **Midterm #1: Monday Sept. 29th** (11:10AM-12:00PM)
 - closed book; one page (8.5"x11") of notes & calculator allowed
 - covers Chapters 1-5 in textbook (HW#1-4)
- Midterm Review Session: Friday 9/26 7-9PM, 277 Cory
- Extra office hours:
 - Steve: 9/26 from 12-2PM
 - Farhana: 9/27 from 1-3PM, 9/28 from 9-11AM
- Practice problems and old exam are posted online


OUTLINE

- Review: op amp circuit analysis
- The capacitor (Chapter 6.2 in text)

Review: Op Amp Circuit Analysis

Procedure:

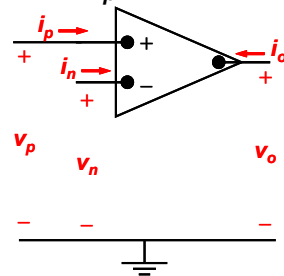
1. Assume that the op amp is ideal
 - a) Apply KCL at (+) and (-) terminals, noting $i_p = 0$ & $i_n = 0$
 - b) Note that $v_n = v_p$
 - c) Write an expression for v_o
2. Calculate v_o



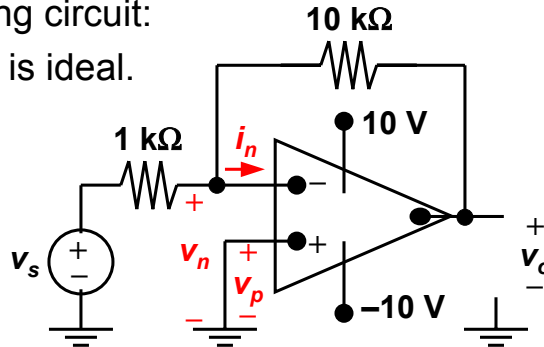3. Check: Is the op-amp operating in its linear region?
 - If $V^- \leq v_o \leq V^+$, then the assumption is valid.
 - If calculated $v_o > V^+$, then v_o is saturated at V^+
 - If calculated $v_o < V^-$, then v_o is saturated at V^-

Op Amp Circuit Analysis Example

Consider the following circuit:
Assume the op amp is ideal.



- Calculate v_o if $v_s = 100$ mV
- What is the **voltage gain** v_o/v_s of this amplifier?
- Specify the range of values of v_s for which the op amp operates in a linear mode


Op Amp Circuit Analysis Example cont'd.

What if the op amp is not ideal?


$$R_i = 10 \text{ k}\Omega$$

$$R_o = 1 \text{ k}\Omega$$

$$A = 10^3$$

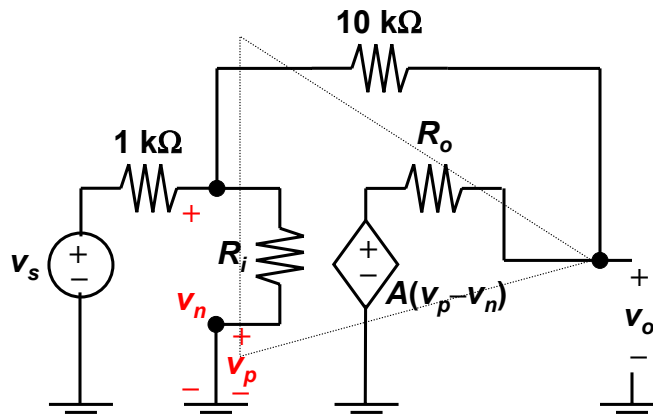

Re-draw the circuit
& analyze:

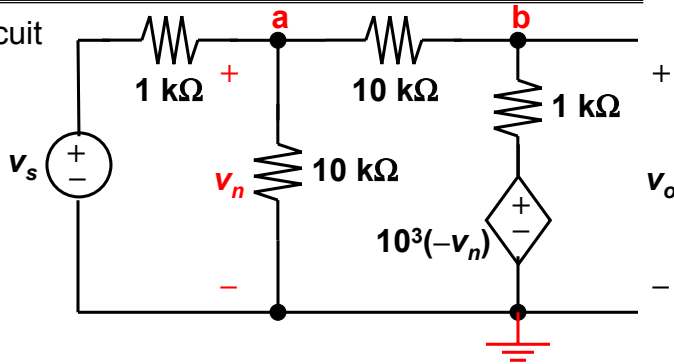


KCL @ node a:

KCL @ node b:

$$-\frac{v_o}{v_s} \cong 9.87 < 10$$

Effect of Load Resistance R_L

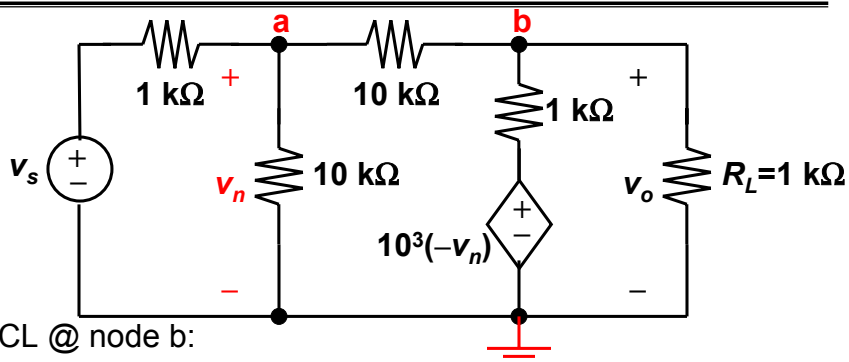

KCL @ node b:

$$-\frac{v_o}{v_s} \cong 9.75 < 9.87$$

- For an ideal op amp ($R_o = 0 \Omega$), v_o does not depend on the "load". However, for a realistic op amp, it does.

The Capacitor

Two conductors (a,b) separated by an insulator:

difference in potential = V_{ab}

=> equal & opposite charge Q on conductors

$$Q = CV_{ab}$$

(stored charge in terms of voltage)


where C is the **capacitance** of the structure,

➤ positive (+) charge is on the conductor at higher potential


Parallel-plate capacitor:

- area of the plates = A
- separation between plates = d
- **dielectric permittivity** of insulator = ϵ

=> capacitance $C = \frac{A\epsilon}{d}$

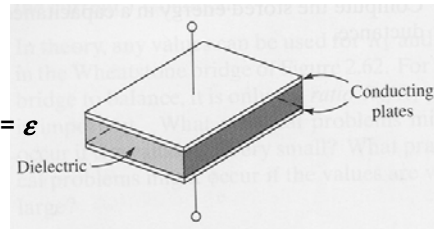

Symbol:

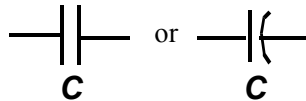


Units: Farads (Coulombs/Volt)

(typical range of values: 1 pF to 1 μF)

Current-Voltage relationship:
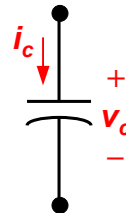
$$i_c = \frac{dQ}{dt} = C \frac{dv_c}{dt} + v_c \frac{dC}{dt}$$



Note: v_c must be a continuous function of time

Voltage in Terms of Current

$$Q(t) = \int_0^t i_c(t) dt + Q(0)$$

$$v_c(t) = \frac{1}{C} \int_0^t i_c(t) dt + \frac{Q(0)}{C} = \frac{1}{C} \int_0^t i_c(t) dt + v_c(0)$$


Stored Energy

You might think the energy stored on a capacitor is QV , which has the dimension of Joules. But during charging, the average voltage across the capacitor was only half the final value of V .

Thus, energy is $\frac{1}{2}QV = \frac{1}{2}CV^2$.

Example: A 1 pF capacitance charged to 5 Volts
has $\frac{1}{2}(5V)^2 (1pF) = 12.5 \text{ pJ}$

A more rigorous derivation

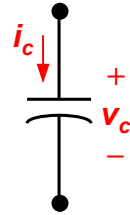

$$w = \int_{t = t_{\text{Initial}}}^{t = t_{\text{Final}}} v_c \cdot i_c dt = \int_{v = V_{\text{Initial}}}^{v = V_{\text{Final}}} \frac{dQ}{dt} dt = \int_{v = V_{\text{Initial}}}^{v = V_{\text{Final}}} v_c dQ$$

$$w = \int_{v = V_{\text{Initial}}}^{v = V_{\text{Final}}} C v_c dv_c = \frac{1}{2} C V_{\text{Final}}^2 - \frac{1}{2} C V_{\text{Initial}}^2$$

Integrating Amplifier

$$v_o(t) = -\frac{1}{RC} \int_0^t v_{IN}(t) dt + v_c(0)$$

