

Lecture #31

ANNOUNCEMENTS

- Prof. King's office hours this week are cancelled

OUTLINE


- » Fan-out
- » Propagation delay
- » CMOS power consumption
- » Timing diagrams

Reading (Rabaey *et al.*)

- Chapter 1.3, pp. 21-22 & 24-28
- Chapter 5.2 & 5.5, pp. 148-149 & 173-184
- Chapter 6.2.1, pp. 204-207, 215-216

Fan-Out

 
- Typically, the output of a logic gate is connected to the input(s) of one or more logic gates
- The **fan-out** is the number of gates that are connected to the output of the driving gate:



- Fanout leads to increased capacitive load on the driving gate, and therefore longer propagation delay
 - The input capacitances of the driven gates sum, and must be charged through the equivalent resistance of the driver

Effect of Capacitive Loading

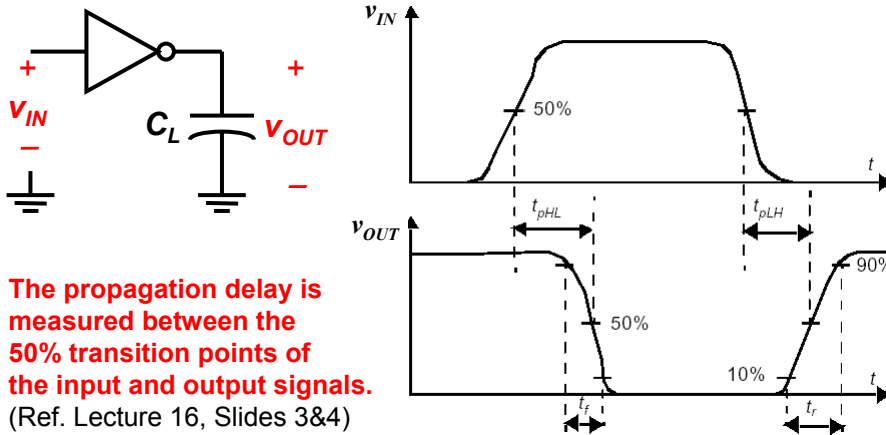- When an input signal of a logic gate is changed, there is a **propagation delay** before the output of the logic gate changes. This is due to capacitive loading at the output.



Calculating the Propagation Delay

Model the MOSFET in the ON state as a resistive switch:


Case 1: V_{out} changing from High to Low
(input signal changed from Low to High)

- NMOSFET(s) connect V_{out} to GND

$$t_{pHL} = 0.69 \times R_n C_L$$

Pull-up network is modeled as an open switch →

 Pull-down network is modeled as a resistor →




Calculating the Propagation Delay (cont'd)

Case 2: V_{out} changing from Low to High
(input signal changed from High to Low)

- PMOSFET(s) connect V_{out} to V_{DD}

$$t_{pLH} = 0.69 \times R_p C_L$$

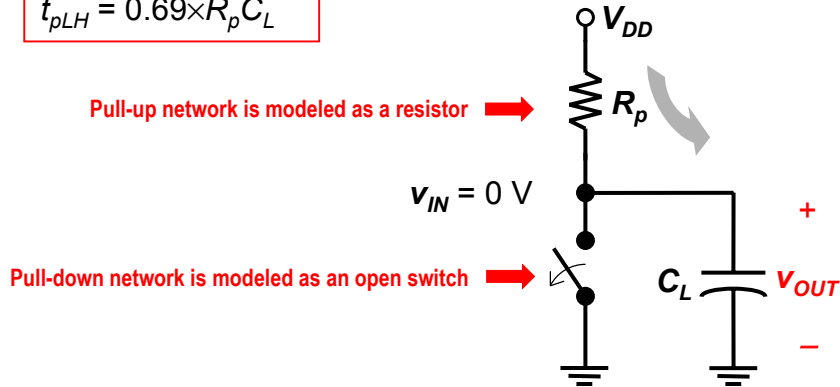

Output Capacitance of a Logic Gate

- The output capacitance of a logic gate is comprised of several components:

“intrinsic capacitance” \rightarrow • pn-junction and gate-drain capacitance
– both NMOS and PMOS transistors

“extrinsic capacitance” $\left\{ \begin{array}{l} \bullet \text{ capacitance of connecting wires} \\ \bullet \text{ input capacitances of the fan-out gates} \end{array} \right.$


 


Figure 5.14 The Miller effect—A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.

Minimizing Propagation Delay

- A fast gate is built by
 1. **Keeping the output capacitance C_L small**
 - Minimize the area of drain pn junctions.
 - Lay out devices to minimize interconnect capacitance.
 - Avoid large fan-out.
 2. **Decreasing the equivalent resistance of the transistors**
 - Decrease L
 - Increase W
 - ... but this increases pn junction area and hence C_L
 3. **Increasing V_{DD}**
 - trade-off with power consumption & reliability


Transistor Sizing for Performance

 

- Widening the transistors reduces resistance, but increases capacitance
- In order to have the on-state resistance of the PMOS transistor match that of the NMOS transistor (e.g. to achieve a symmetric voltage transfer curve), its W/L ratio must be larger by a factor of ~ 3 . To achieve minimum propagation delay, however, **the optimum factor is ~ 2 .**

CMOS Energy Consumption (Review)

 - The energy delivered by the voltage source in charging the load capacitance is $C_L V_{DD}^2$
 - Half of this is stored in C_L ; the other half is absorbed by the resistance through which C_L is charged.
- In one complete cycle (charging and discharging), the total energy delivered by the voltage source is $C_L V_{DD}^2$



CMOS Power Consumption

- The total power consumed by a CMOS circuit is comprised of several components:
 1. **Dynamic power consumption due to charging and discharging capacitances***:

$$P_{dyn} = C_L V_{DD}^2 f_{0 \rightarrow 1} = C_{EFF} V_{DD}^2 f$$

$f_{0 \rightarrow 1}$ = frequency of 0→1 transitions (“switching activity”)

f = clock rate (maximum possible event rate)

Effective capacitance C_{EFF} = average capacitance charged every clock cycle

*** This is typically by far the dominant component!**

CMOS Power Consumption (cont'd)

2. **Dynamic power consumption due to direct-path currents during switching** (Ref. Lecture 27, Slides 3&4)


$$P_{dp} = C_{sc} V_{DD}^2 f$$

$C_{sc} = t_{sc} I_{peak} / V_{DD}$ is the equivalent capacitance charged every clock cycle due to "short-circuits" between V_{DD} & GND

(typically <10% of total power consumption)

3. **Static power consumption due to transistor leakage and pn-junction leakage**

$$P_{stat} = I_{stat} V_{DD}$$

 

Low-Power Design Techniques

1. **Reduce V_{DD}**

→ quadratic effect on P_{dyn}

Example: Reducing V_{DD} from 2.5 V to 1.25 V
reduces power dissipation by factor of 4

- Lower bound is set by V_T : V_{DD} should be $>2V_T$

2. **Reduce load capacitance**

→ Use minimum-sized transistors whenever possible

3. **Reduce the switching activity**


– involves design considerations at the architecture level (beyond the scope of this class!)

NAND Gates vs. NOR Gates

- In order for a 2-input NAND gate to have the same pull-down delay (t_{pHL}) as an inverter, the NMOS devices in the NAND gate must be made twice as wide.
 - This first-order analysis neglects the increase in capacitance which results from widening the transistors.
 - Note: The delay depends on the input signal pattern.
 - In order for a 2-input NOR gate to have the same pull-up delay (t_{pLH}) as an inverter, the PMOS devices in the NOR gate must be made twice as wide.
 - Since hole mobility is lower than electron mobility (so that larger W/L ratios are needed for PMOS devices as compared with NMOS devices), stacking PMOS devices in series (as is done in a NOR gate) should be avoided as much as possible.
- **NAND gates are preferred for implementing logic!**

Propagation Delay in Timing Diagrams


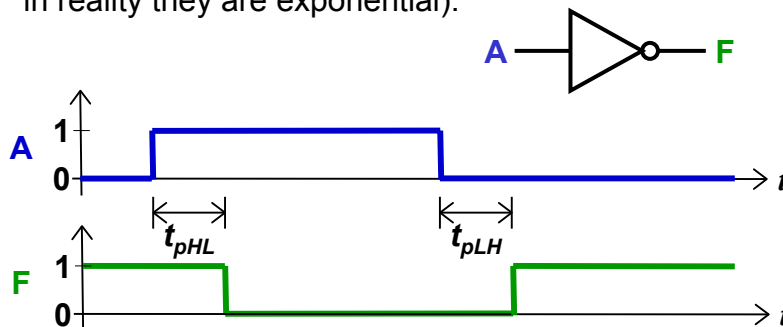
- To simplify the drawing of timing diagrams, we can **approximate the signal transitions to be abrupt** (though in reality they are exponential).



To further simplify timing analysis, we can define the propagation delay as $t_p = (t_{pHL} + t_{pLH}) / 2$

Glitching Transitions

  The propagation delay from one logic gate to the next can cause spurious transitions, called **glitches**, to occur. (A node can exhibit multiple transitions before settling to the correct logic level.)




Glitch Reduction

- Spurious transitions can be minimized by balancing signal paths

Example: $F = A \cdot B \cdot C \cdot D$



Chain structure

 

Tree structure