


## Outline

- Last time:
  - Race-free State Assignment
  - Excitation Equations
  - Design Example: Implementation
  - Summary of Asynchronous Design Process
- This lecture:
  - Asynchronous Examples
  - State Assignment in Asynchronous
  - Error Detection & Correction
  - Review: Bandwidth and Latency
  - Binary Decision Diagrams

CS150 Newton/Pister

14.1.1

## Race Conditions and Cycles

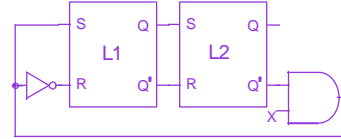

	X	
	0	1
Q <sub>1</sub> Q <sub>2</sub>	00	10
01	00	00
11	01	01
10	01	11

	X	
	0	1
Q <sub>1</sub> Q <sub>2</sub>	00	
01	00	
11	01	
10	01	11

CS150 Newton/Pister

14.1.2

## Race Conditions


	X	
	0	1
Q <sub>1</sub> Q <sub>2</sub>	00	11
01	00	01
11	01	11
10	10	10

CS150 Newton/Pister

14.1.3

## Example 3: Asynchronous Analysis

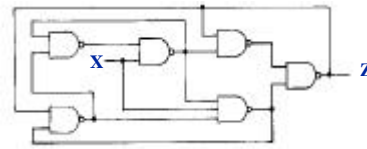- (a) Analyze the following asynchronous network using a flow table. Starting in the stable total state for which  $X=Z=0$ , determine the state and the output sequences when the input sequence is  $X=0, 1, 0, 1, 0, \dots$
- (b) Find any critical races which are present in the table.



CS150 Newton/Pister

14.1.4

## Race-Free State Assignment

- A race-free state assignment for any 4-row table can be found using three state variables
- Example:




column 00  $b \rightarrow a, c \rightarrow d$   
 column 01  $a \rightarrow c, b \rightarrow d$   
 column 11  $a \rightarrow d, c \rightarrow b$   
 column 10  $c \rightarrow a, d \rightarrow b$

CS150 Newton/Pister

14.1.5
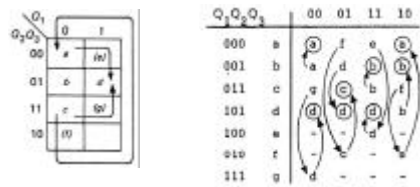
## Race-Free State Assignment

- The assignment below is a universal state-assignment map that will work for any 4-row table
- The example can then be expanded as shown, with the additional rows added




CS150 Newton/Pister

14.1.6
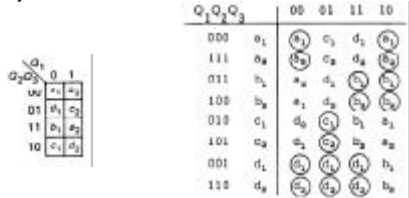
### Race-Free State Assignment

- Another universal assignment for 4-row tables is shown below (M. Mano, *Logic and Computer Design*, Prentice Hall)
- Using this approach, the expanded example from before becomes as shown below right
- This approach faster than previous general approach above. Why?




CS150 Newton/Pister

14.1.7
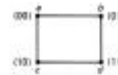
### Race-Free State Assignment

- Don't cares can be used to make race-free assignment
- In example below-left, we need:  $col_{00} d \rightarrow a$ ;  $col_{01} a \rightarrow b, c \rightarrow d$ ;  $col_{11} b \rightarrow c$ ;  $col_{10} a \rightarrow c, b \rightarrow d$



- Looks like we need extra rows, but use the don't cares:



CS150 Newton/Pister

14.1.8

### Shared-Row Assignments

	00	01	11	10
a	1	2	5	4
b	7	2	3	12
c	1	8	13	4
d	7	10	5	4
e	1	9	5	6
f	11	8	3	6

column 00:  $e, c \rightarrow a$   $d \rightarrow b$   
 column 01:  $a \rightarrow b$   $c, f \rightarrow d$   
 column 11:  $b, f \rightarrow c$   $a, d \rightarrow e$   
 column 10:  $a, c \rightarrow d$   $e \rightarrow f$

Consider the example above. We need at least three state variables and maybe even four.


$e \rightarrow a, c \rightarrow a$ ;  $e \rightarrow c \rightarrow a$ ;  $c \rightarrow c \rightarrow a$   
 or any of these going through an intermediate state

CS150 Newton/Pister

14.1.9
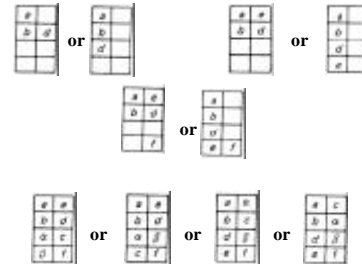
### Shared-Row Assignment

- How do we get there? Trial and error...




CS150 Newton/Pister

14.1.10
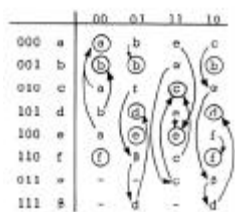
### Shared-Row Assignment

- Result of using second option from previous slide:



CS150 Newton/Pister

14.1.11

### Error Detection & Correction

- As transistors & wires become smaller, the number of electrons used to represent a stored 1 or 0 decreases
- The probability that a cosmic ray, alpha particle, local electric field (crosstalk) or some other disturbance will change a stored value (or even the value on a wire) increases
- Two aspects:
  - Error detection (e.g. parity)
  - Error correction (e.g. Hamming Codes)
    - 2-bit detect, 1-bit correct

CS150 Newton/Pister

14.1.12

### Hamming Codes

- Most common types of error-correcting codes used in RAM
- Based on work of R. W. Hamming
- k parity bits are added to an n-bit word, forming a new n+k bit word
- The positions numbered with powers of two are reserved for the parity bits
- Can be used with words of any length
- Example: 8-bit data word 11000100

1	2	3	4	5	6	7	8	9	10	11	12
P <sub>1</sub>	P <sub>2</sub>	1	P <sub>4</sub>	1	0	0	P <sub>8</sub>	0	1	0	0

CS150 Newton/Pister

14.1.13

### Hamming Codes

- Calculate parity bits as follows:  
 $P_1 = \text{xor}(3,5,7,9,11) = 1 \oplus 1 \oplus 0 \oplus 0 \oplus 0 = 0$   
 $P_2 = \text{xor}(3,6,7,10,11) = 0$   
 $P_4 = \text{xor}(5,6,7,12) = 1$   
 $P_8 = \text{xor}(9,10,11,12) = 1$

1	2	3	4	5	6	7	8	9	10	11	12
0	0	1	1	1	0	0	1	0	1	0	0

- When bits are read from memory, compute check bits:  
 $C_1 = \text{xor}(1,3,5,7,9,11)$   
 $C_2 = \text{xor}(2,3,6,7,10,11)$   
 $C_4 = \text{xor}(4,5,6,7,12)$   
 $C_8 = \text{xor}(8,9,10,11,12)$

CS150 Newton/Pister

14.1.14

### Hamming Codes

- $C_8 C_4 C_2 C_1 = 0000$  indicates no error has occurred
- Examples:

1	2	3	4	5	6	7	8	9	10	11	12	
0	0	1	1	1	0	0	1	0	1	0	0	no error
1	0	1	1	1	0	0	1	0	1	0	0	error in bit 1
0	0	1	1	0	0	0	1	0	1	0	0	error in bit 5

C <sub>8</sub>	C <sub>4</sub>	C <sub>2</sub>	C <sub>1</sub>	
0	0	0	0	no error
0	0	0	1	error bit 1
0	1	0	1	error bit 5

CS150 Newton/Pister

14.1.15

### Hamming Codes

- For n data bits and k check bits,  $n+k \leq 2^k-1$
- Grouping of bits for parity generation can be observed from listing of binary numbers:

B <sub>1</sub>	B <sub>2</sub>	B <sub>3</sub>	
0	0	0	0
1	1	0	0
2	0	1	0
3	1	1	0
4	0	0	1
5	1	0	1
6	0	1	1
7	1	1	1

**B<sub>1</sub>=1 for (1,3,5,7)**  
**B<sub>2</sub>=1 for (2,3,6,7)**  
**B<sub>3</sub>=1 for (4,5,6,7)**

CS150 Newton/Pister

14.1.16

### Hamming Codes

- Add P<sub>13</sub> as an overall parity bit: 001110010100P<sub>13</sub>
- Detect/Correct Rules as follows:


If C=0, P=0 no error  
 If C≠0, P=1 single error, correctable  
 If C≠0, P=0 double error, uncorrectable  
 If C=0, P=1 error occurred in P<sub>13</sub>

- Can also have far more sophisticated schemes
- Covered in detail in communication & information theory courses

CS150 Newton/Pister


14.1.17

### NMM: Combinational Implementation

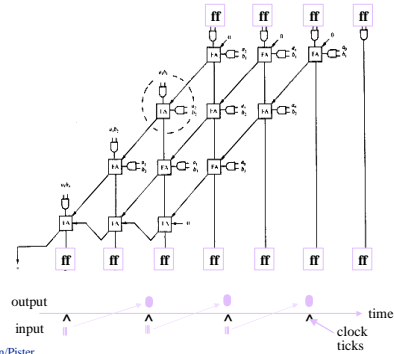

CS150 Newton/Pister


14.1.18

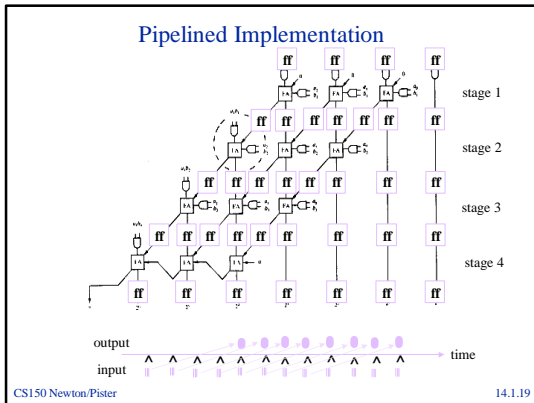

### Bandwidth and Latency

- **Latency:** The minimum time to get the first result (sec.) - the one-time cost.
- **Bandwidth:** The maximum rate at which results can be produced in the steady-state (values/sec.) - the incremental cost
- For example, disc drives, RAM (normal, video), networks, signal-processors (e.g. HDTV, radar)



CS150 Newton/Pister 14.1.20






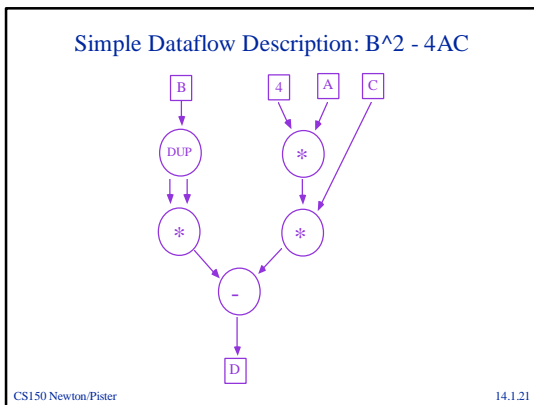


### Scheduling of Functional Units


- Given a certain number of functional units (e.g. ALU's, RAM's), schedule a particular computation (from the HDL or software) onto a particular functional unit at a particular time relative to other operations.
- Analogous problem scheduling "wires"
- What about the values on the wires?

CS150 Newton/Pister 14.1.22

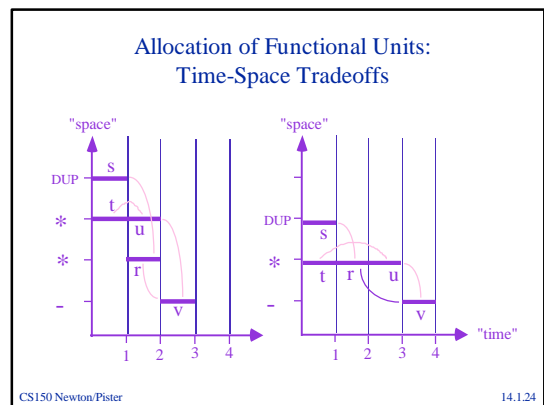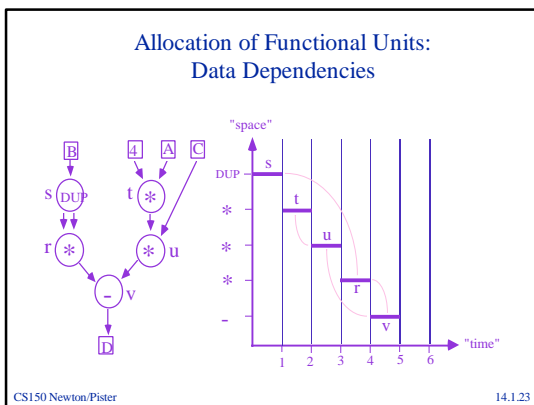

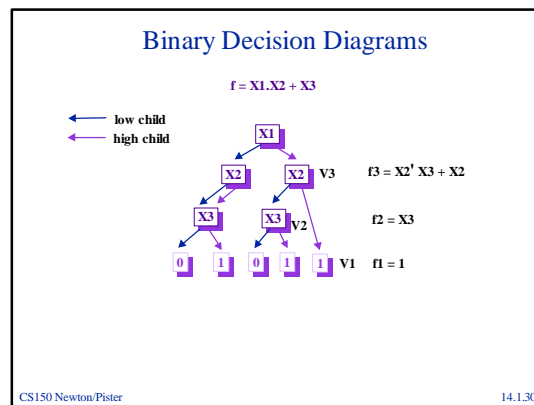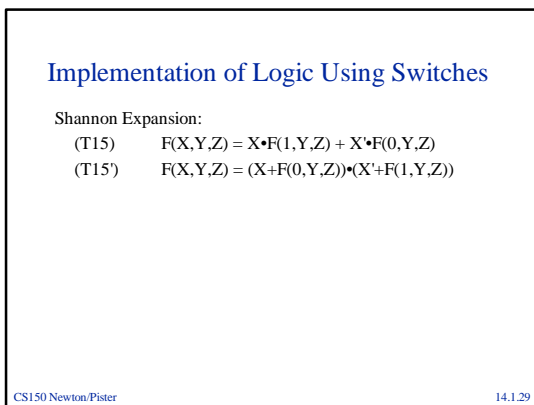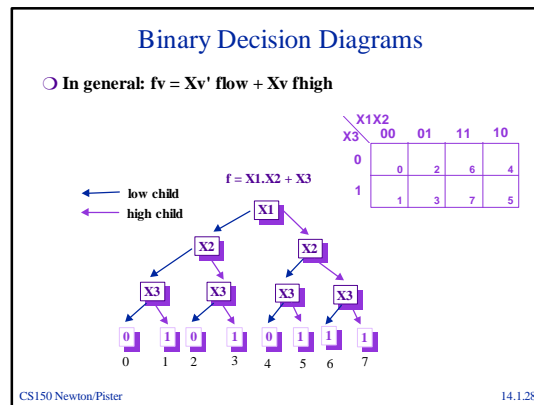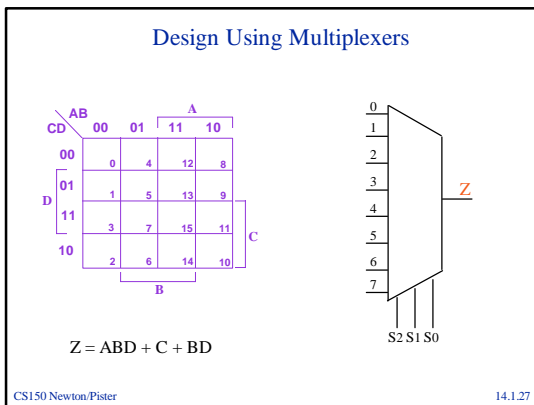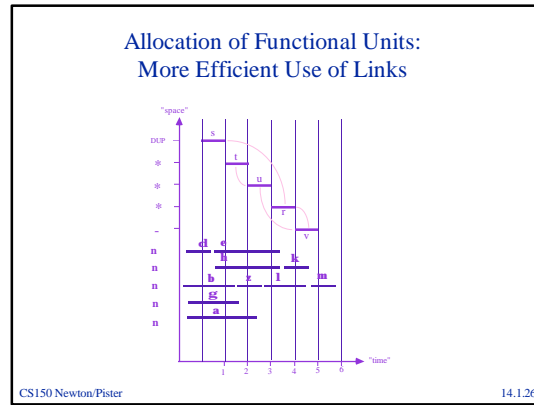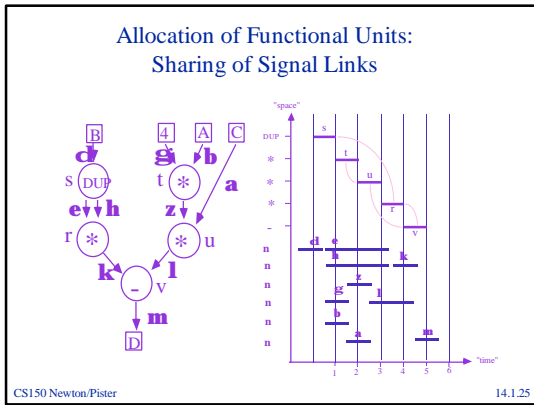

### Use of BDDs for Verification

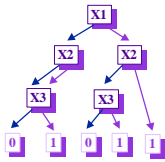


- Condition on edges forces order on variables.
- Order must be consistent with all edges.
- For each edge, parent before child in the order.  
→ X1 X2 X3

CS150 Newton/Pister

14.1.31
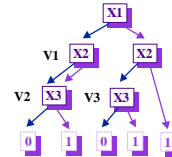
### Use of BDDs for Verification

- V1 is a redundant vertex
- V2, V3 represent the same function
- A BDD is a reduced binary decision graph  
→ Reduction is  $O(N^2 \log(N))$  for N vertices




CS150 Newton/Pister

14.1.32
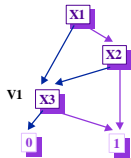
### Use of BDDs for Verification


- Each vertex corresponds to a partial assignment of inputs.  
→ V1: 0-, 10
- Result of reduction is a canonical form.



CS150 Newton/Pister

14.1.33

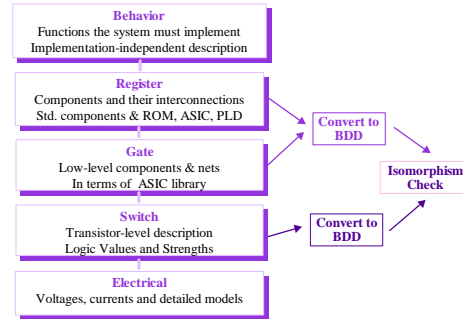
### Combinational Verification Using Canonical Form



CS150 Newton/Pister

14.1.34

### Connectivity Verification

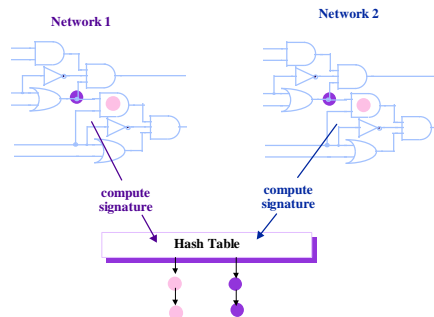

CS150 Newton/Pister

14.1.35

### Connectivity Verification

- (1) Read Network1 and Network2 into separate graph data structures (usually, node = transistor or gate, edge = connection).
- (2) Compute signatures for nodes or edges or both.  
→ Type-specific: Gate type, #inputs, #outputs  
→ Network-specific (local): Fanin types, #fanouts, fanout types  
→ Network-specific (global): Distance from primary inputs, primary outputs, nodes that are known to be the same in each network (e.g. named, primary inputs or outputs ("seeds")).
- (3) Hash signatures from both networks into single hash table.
- (4) If a hash table cell has:  
→ > 2 nodes: ignore for now  
→ = 2 nodes: a match has been found  
→ = 1 node: an (easy!) error has been found
- (5) Add links between networks for nodes that have been matched.
- (6) Recompute hash functions for un-bound nodes and repeat until done or no change.

CS150 Newton/Pister

14.1.36