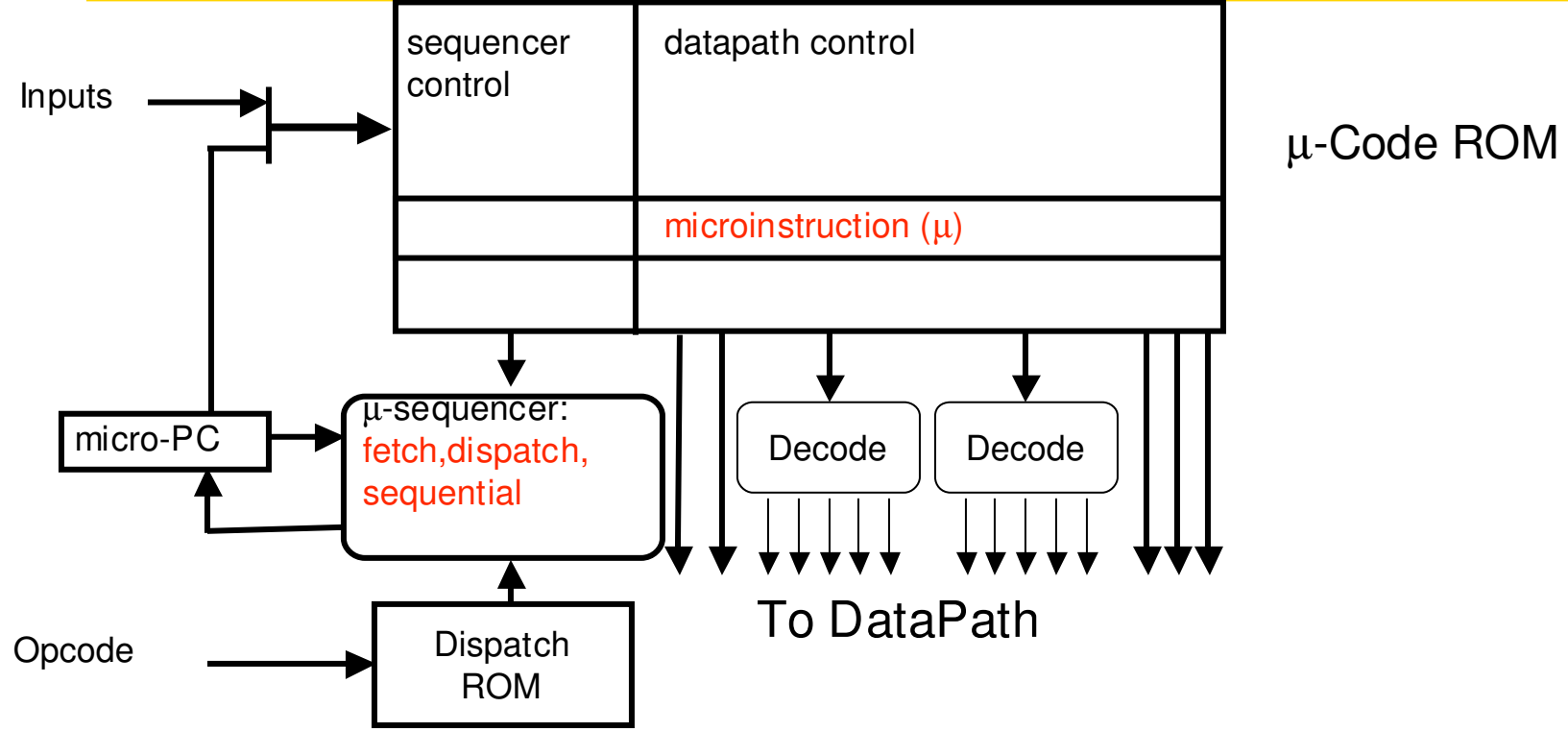
sequencer control
datapath control
Inputs
μ-Code ROM
microinstruction (μ)
micro-PC
μ-sequencer:
fetch,dispatch,
sequential
Decode
Decode
To DataPath
Opcode
Dispatch ROM