

University of California at Berkeley
College of Engineering
Dept. of Electrical Engineering and Computer Sciences

EE 105 Midterm I

Spring 2007

Prof. Ming C. Wu

Feb. 22, 2007


Guidelines

- Open book and notes.
- The values of common parameters are listed at the beginning of next page.

Please use the following parameters for all problems unless specified otherwise:

$$\begin{aligned} \phi_{n+} &= 550 \text{ mV}, & \phi_{p+} &= -550 \text{ mV}, & V_{th} &= 26 \text{ mV} \\ \epsilon_{Si} &= 11.7, & \epsilon_{SiO_2} &= 3.9, & \epsilon_0 &= 8.854 \times 10^{-14} \text{ F/cm} \\ q &= 1.6 \times 10^{-19} \text{ C}, & n_i &= 10^{10} \text{ cm}^{-3}. \end{aligned}$$

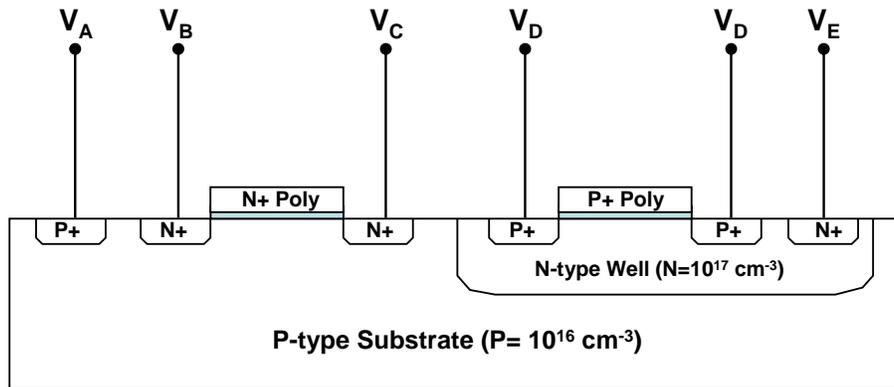- (1) The figure below shows the schematic cross section of a CMOS device.
- [5 pt] Please circle all the PN junctions in this CMOS device directly on the cross-sectional diagram in your answer sheets. How many PN junctions are there?
 - [5 pt] If the power supply voltages available for this CMOS are +2V and -2V, what voltage should be applied to V_A and V_E ? Why?



- (2) Consider a PN junction with both N and P doping concentration of 10^{16} cm^{-3} .
- [5 pt] Find the built-in potential.
 - [5 pt] What is the depletion width at zero bias?
 - [5 pt] What is the maximum electric field at zero bias?
 - [5 pt] The PN junction is used as a varactor. If the bias voltage is varied from zero to 10V reverse bias, what is the capacitance tuning ratio (i.e., the ratio of maximum and minimum capacitance)
- (3) Consider a PMOS capacitor with a p+ poly gate and a 1-nm-thick high-k gate dielectric whose relative dielectric constant is 20. The substrate doping is 10^{16} cm^{-3} .
- [5 pt] Find the flat-band voltage.
 - [5 pt] Find the threshold voltage.
 - [10 pt] Find the charge distribution of the MOS capacitor (i.e., $\rho(x)$ vs x) when the gate is biased at 0V. Please be quantitative.
 - [5 pt] What is the total gate charge per unit area at the gate, channel, and body, respectively, when the gate is biased at 0V.
 - [5 pt] What is the total capacitance per unit area when the gate is biased at 0V?
- (4) For the circuit shown below, $W/L = 10$ for both M_1 and M_2 ,
 $\mu_n C_{ox} = 100 \mu\text{A/V}^2$, $\mu_p C_{ox} = 50 \mu\text{A/V}^2$, $\lambda = 0.05 \text{ V}^{-1}$ for NMOS and 0.01 V^{-1} for PMOS, $V_{TH} = 1\text{V}$ for NMOS and -1V for PMOS, $V_{DD} = 5\text{V}$.

- [10 pt] Find the DC bias voltages, V_b and V_G , such that the bias current is $100 \mu\text{A}$. Use $\lambda = 0$ for this part.
- [5 pt] Find the small-signal parameters (i.e., g_m , r_0) corresponding to the condition in a).
- [5 pt] What is the voltage gain of this amplifier, both symbolically and numerically?
- [5 pt] What is the input and output resistance of this amplifier (both symbolically and numerically)?
- [5 pt] What determines the output voltage swing? Find the maximum and the minimum output voltages.
- [5 pt] How does the voltage gain and the output resistance change if the gate of M_1 is connected to the output directly (no V_b is applied)?
- [5 pt] What is the DC value of the output voltage?

